

Engineering 1620 – Spring 2020
Answers to Homework 3: Diode Applications and Bipolar Transistors

1.) First one has to convert the problem to an appropriate linear model. The zener diode model voltage parameter is $V_Z = V_{ZT} - R_Z I_{ZT} = 7.5 - 12 \cdot 0.01 = 7.38$ volts. At 15ma, the forward biased diode has parameters $r_d = \frac{nkT}{qI_D} = \frac{1.8 \cdot 0.0256}{0.015} = 3.07$ ohms and


$V_F = V_D - \frac{mkT}{q} = .65 - 1.8 \cdot 0.0256 = .604$ volts. The equivalent circuit is shown below and is the basis of our calculations.

1.1) The resistor shown in series with the two diodes is simply the value needed to get 15ma DC in the diode loop or $\frac{V_{IN} - V_F - V_Z}{0.015} = \frac{24 - .614 - 7.38}{0.015} = 1068$ ohms.

1.2) The output voltage is $V_{OUT} = .614 + 7.38 + 0.015 \cdot (2.4 + 12) = 8.21$ volts and the ripple is $v_{out} = v_{in} \frac{3.0 + 12}{14.4 + 1067} = 0.0069$ volts.

1.3) For a 10 degree C increase in temperature, the diode voltage decreases by 22 mv and the zener increases by $10 \cdot .027\%$ of the DC voltage across the zener. That voltage is $7.38 + .015 \cdot 12 = 7.56$ volts. This implies a change of $10 \cdot .00027 \cdot 7.56 = 20.4$ mv for a net change of -1.6 mV or -0.019 %.

 1.4) The amplifier makes the output independent of the amount of current drawn by the load RL. The input of the amplifier draws no current and the current through the load, RL, is supplied by the power supply through the opamp.



2.) To find the optimal collector current, one has to begin by computing the impedance of the shaker. The reactance of the coil at 60 Hz is 22.6 ohms. The phase angle is

$$\varphi = \tan^{-1}\left(\frac{22.6}{10}\right) = 66.1 \text{ deg. The magnitude of the impedance } |Z_c| \text{ is } \boxed{}$$

$\sqrt{11.5^2 + 22.6^2} = 25.4$ ohms. Then the optimal collector current is

$$I_{Copt} = \frac{V_{CC} - V_{CESAT}}{R_{DC} + (1 - \alpha)|Z_{AC}|} = \frac{40 - 1.3}{11.5 + .9 \cdot 25.4} = 1.12 \text{ amperes.}$$

We next want to select values for the two biasing resistors. The complicating factor is that h_{FE} varies from 750 to 20,000 and that is a 27:1 range. To maintain fairly tight control of the quiescent current, R_{BB} will probably have to be low, much lower than the minimum of $(1 + h_{FE})R_E = 751 \cdot 1.5 = 1125$ ohms. I tried using a lower resistor $R_1 = 220$ ohms (a standard resistance about 20 % of 1125) and R_{BB} will be a little lower than that. By using the nominal conditions ($h_{FE} = 4000$, $V_{BE} = 1.35$) and KCL at the base node, this gives $R_2 = 2.66 \text{ K}$. With these values, $V_{BB} = 3.06$ volts and $R_{BB} = 203$ ohms. The range of base-emitter voltage is the temperature change times twice the temperature coefficient of one emitter-base junction or $70 \cdot 2 \cdot .0022 = .308$ volts. Then one tests the two cases: 1.) for $h_{FE} = 750$, $V_{BE} = 1.504$ volts ($1.35 + .154$) one gets $I_C = .88$ Amps which is 80 % of the nominal value – just enough! 2.) for $h_{FE} = 20000$, $V_{BE} = 1.20$ volts ($1.35 - .154$) one gets $I_C = 1.23$ amps or 112 % of nominal - a comfortable margin. There are certainly other solutions near these values.

For the input capacitor calculation, we need the input impedance of $R_{BB} || Z_{tr}$ at nominal conditions or $2660 || 220 || (4000 \cdot 1.53) = 197$ ohms. One DB loss is a factor of .89 and the ratio of 60 Hz to cutoff must be 1.95 for a single pole circuit like this one.

$$(0.89 = \frac{(60 / f_{3DB})^2}{\sqrt{1 + (60 / f_{3DB})^2}}) \text{ That places the 3 DB cutoff at 30.5 Hz and}$$

$$C_{IN} = \frac{1}{2\pi R_{in} f_c} = \frac{1}{2\pi 196 \cdot 30.5} = 26.6 \mu f.$$

3.) Since the circuit is very simple, I just wrote the deck in a text editor. I ran the simulation in LTSpice on my home computer. Here is the deck and the principal results.

```
* Q&D Simulation of PNP CE stage
.lib "C:\EDA\En162\SPICES\ENGN1620LabComponents.lib"
*
```

```
VDD 1 0 DC 12
RA 1 2 71
CE 1 2 220U
RB 2 3 29
Q1 4 5 3 3 2N3906
RC 4 0 1K
```

Property	Target Value	Value in SPICE
ICQ	6.6 mA	7.25 mA
Gain	30 (30 dB)	30.03 (29.55 dB)
LF cutoff	50 Hz (-3dB)	54.4 Hz (29.55 – 26.54)

```

R1 1 5 2.3K
R2 5 0 16K
CIN 5 6 2.8U
VIN 6 0 AC 1.0
.OP
.AC DEC 20 10 100K
.PROBE
.end

```

4.1) The first stage is common base CB and the second common collector CC.

4.2) With no base current in Q1, the voltage across the 3 K biasing resistor will be $3 \cdot 12 / 13 = 2.77$ volts. With a base current of 0.01 mA, this voltage difference decreases to 2.75 volts. (The effect of base current might have been neglected altogether given this value.) So $RE1 = (2.75 - 0.7) / 5e-3 = 410$ ohms.

4.3) The output impedance of the Q1 stage is 1 K and that is the source impedance for the CC stage. The output impedance of that stage is $RE2 \parallel (1K/101 + re2) = 18$ ohms. Very likely RE2 will have little effect so $re2 = 8$ ohms and $IE2 = 3.21$ mA. The base current of Q2 = .032 mA and the emitter voltage is $(5 - .032 - 0.7)$ for $RE2 = 4.27 / 3.21 = 1.33$ K.

4.4) The midband gain is $.99 \cdot (1K \parallel 101 \cdot 2.7K) / (180 + re1) = 4.81$ (13.6 DB).

4.5) The midband input impedance is $re1 + 180 = 185$ ohms.

$$c_{IN} = \frac{1}{2\pi f R_{in}} = \frac{1}{2\pi \cdot 10^4 \cdot 185} \text{ which is } 0.083 \text{ ufd.}$$

4.6) The input capacitor prevents the signal source from changing the bias conditions of the amplifier itself.

5.) The starting point for the problem is to see what the quiescent current would be if the transistor operates so that it is not in saturation. We try to apply the simple formula for a

circuit with three-resistor biasing, namely $I_C = \frac{h_{FE}(V_{BB} - V_{BE})}{R_{BB} + (1 + h_{FE})R_E}$. To estimate V_{BE} , we

estimate first the collector current as the expected voltage across R3 divided by the value of R3 or $(9 - 5) / 33 = 0.12$ mA. Then $V_{BE} = \frac{kT}{q} \ln(1.2 \cdot 10^{-4} / 1.2 \cdot 10^{-14}) = 0.59$ volts. For

this circuit: $V_{BB} = 9 \frac{270}{270 + 330} = 4.05$ volts; $R_{BB} = \frac{270 \cdot 330}{270 + 330} = 149$ Kohm. Evaluating the

formula gives: $I_C = \frac{120(4.05 - .58)}{149 + 121 \cdot 3.3} = .71$ mA. This is obviously ridiculous because the

collector voltage would have to be $9 - .71 \cdot 33 = -14.3$ volts. That is not physically possible so the transistor must be in saturation.

Under that condition the collector-emitter voltage will be $V_{CE} = V_{CESAT} = 0.2$ volts and the current gain will be small.


To find the real conditions of the circuit in saturation, just do KCL at the emitter using the emitter voltage, V_{EG} , as the unknown. Then $I_E = I_C + I_B$ and

$$\frac{V_{EG}}{3.3} = \frac{9 - 0.2 - V_{EG}}{33} + \frac{4.05 - 0.59 - V_{EG}}{148}$$

for which the solution is $V_{EG} = 0.861$ volts; $I_C = .260$ mA; $I_B = .021$ mA; $h_{FE} = 12$; $V_{CG} = 1.06$ volts; and $V_{BG} = 1.46$ volts. I am willing to accept a simpler solution - neglect the base current and calculate I_C based simply on $V_{CE} = V_{CESAT} = 0.2$ volts.

The problem is that there is too much base current and V_{BB} must be reduced or R_4 increased or R_3 reduced. You are told to make a change without lowering the input impedance or changing gain or output impedance. The only remaining choice is to raise the value of R_1 . The easy way to select a new value for R_1 is to use KCL at the base terminal. The desired collector current is $I_C = \frac{9 - 5}{33} = .121$ ma. The emitter current is to be 122

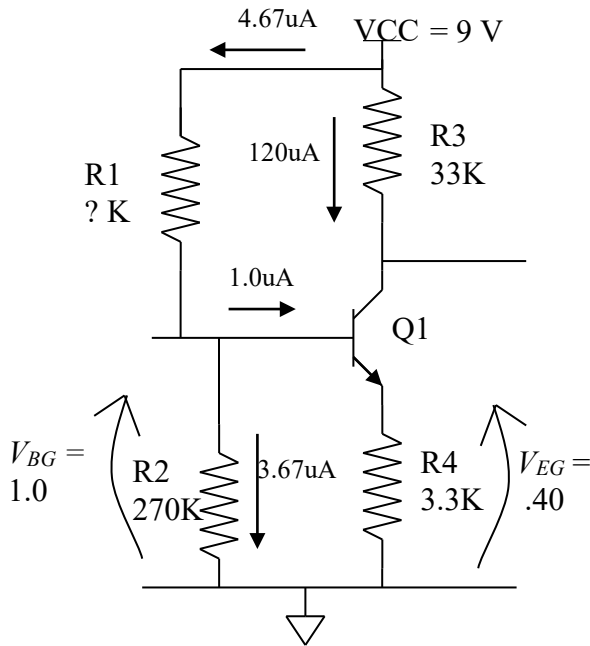uA for an emitter voltage of 0.4 volts. The base node voltage is just about 1.0 volts and the base current 1 uA. Current through R_2 is 3.67 uA and through R_1 4.67 uA. R_1 is then 1.72 Megohms. With the new value of R_1 , $V_{BB} = 1.23$ volts and $R_{BB} = 233$ K.




For a current gain of 80,

$$I_C = \frac{80(1.23 - .59)}{233 + 81 \cdot 3.3} = 0.102 \text{ uA.}$$

Like-wise for a gain of 160, $I_C = 134 \text{ uA.}$

 6.) Here is the circuit for this problem again. It should be obvious that the base-emitter voltage of Q_2 , V_{BE2} , is smaller than that of Q_1 because of the voltage drop across resistor R_E . For that reason, its collector and base currents will be less than those of Q_1 and so we can very likely neglect at least the base current of Q_2 .



6.1) Applying KCL at the collector of Q1 implies:

$$I_{BI} = I_{B1} + I_{C1} = (1 + \beta) I_{B1}$$

Solve for the base current of Q1 and calculate the collector current from that: $I_{C1} = \frac{\beta I_{BI}}{1 + \beta} = \alpha I_{BI}$

6.2) The same equation for collector current holds for each transistor, namely:

$i_{C1} = I_{SCE} \exp\left(\frac{qV_{BE1}}{nkT}\right)$ and $i_{C2} = I_{SCE} \exp\left(\frac{qV_{BE2}}{nkT}\right)$. Apply a Kirchoff voltage loop around the base to emitter of Q1, up across R_E , and across emitter to base of Q2 back to the starting point to get: $v_{BE1} = v_{BE2} + i_{C2} R_E$. Use this result to substitute for v_{BE2} in the exponential equation to get: $i_{C2} = I_{SCE} \exp\left(\frac{q(v_{BE1} - i_{C2} R_E)}{nkT}\right) = i_{C1} \exp\left(\frac{-qi_{C2} R_E}{nkT}\right)$. Now use the result of part 1 to eliminate Q1 and arrive at a transcendental equation with i_{C2} as the only unknown: $i_{C2} = \alpha I_{BI} \exp\left(\frac{-qi_{C2} R_E}{nkT}\right)$. An alternate form of this would be:

$$i_{C2} = \frac{nkT}{qR_E} \ln\left(\frac{\alpha I_{BI}}{i_{C2}}\right)$$

6.3) For a current gain of 100, alpha is .99 and the ratio $\frac{i_{C2}}{\alpha I_{BI}} = \frac{.05}{.99} = .0505$. The natural

$$\log \text{ of } 0.0505 \text{ is } -2.986 \text{ so } R_E = \frac{nkT}{qi_{C2}} \ln\left(\frac{\alpha I_{BI}}{i_{C2}}\right) = \frac{1.05 \cdot .0256 \cdot 2.986}{5.05 \cdot 10^{-5}} = 1460 \text{ ohms.}$$


7.1) The two transistor have the same collector currents because their base to ground connections are identical. The KCL node at the collector of Q1 implies that $I_{C1} = I_{BIAS} - 2I_{B1}$ and substituting the collector current divided by the current gain for the

base current gives $I_{C1} = \frac{h_{FE} I_{BIAS}}{h_{FE} + 2}$. This gives 490 uamp for the given conditions.

7.2) If you short the collector to base of the common base model, you are left with just a resistor r_e from Q1 and the emitter resistor R_E . For 490 uamp and 27 deg. C temperature

that is $r_e = \frac{kT}{qI_{EQ}} = \frac{0.0256}{4.9e-4} = 53 \text{ ohms}$ and the sum becomes 753 ohms.

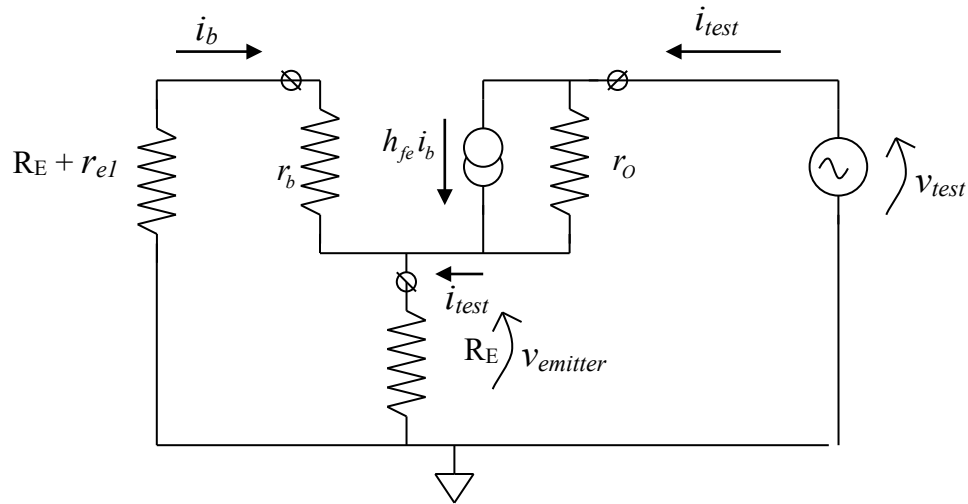7.3) For this part of the problem, you need to make a small signal model first. You want the output impedance of the current source Q2 so you attach a small voltage source to the drain and calculate the resultant current or vice versa. The voltage source is a little easier. Similarly, both the CCCS and CVCS models work – they model the same thing. Here is the circuit model with the CCCS version:



The resistor on the left is the result of part 7.1. The circuit has two nodes where KCL is easy to apply, one at the collector and one at the emitter. The base current is just minus the emitter voltage divided by the resistance of that branch of the circuit. One important thing to notice is that the test current enters the emitter node directly – you don't have to sum the current source and the current through r_o separately at the emitter node. The resultant equations are:

$$\text{At collector: } i_{test} = h_{fe} i_b + \frac{v_{test} - v_{emitter}}{r_o}$$

$$\text{At emitter: } v_{emitter} = i_{test} [R_E \parallel R_E + r_b + r_{e1}] = i_{test} \frac{R_E (R_E + r_b + r_{e1})}{2R_E + r_b + r_{e1}}$$

$$\text{For base current: } i_b = -\frac{v_{emitter}}{r_b + r_{e1} + R_E} \quad (\text{This minus sign is the tricky part.})$$

These are 3 equations in 3 unknowns, but they are straightforward to solve. Eliminate the base current

$$\text{first: } i_{test} = \frac{v_{test}}{r_o} - v_{emitter} \left(\frac{1}{r_o} + \frac{h_{fe}}{r_b + r_{e1} + R_E} \right)$$

You have the emitter voltage in terms of the test current so move its terms to the left side and factor out the test current to get:

$$i_{test} \left[1 + \frac{R_E (R_E + r_b + r_{e1})}{2R_E + r_b + r_{e1}} \cdot \left(\frac{1}{r_o} + \frac{h_{fe}}{r_b + r_{e1} + R_E} \right) \right] = \frac{v_{test}}{r_o}$$

That looks really ugly but it actually isn't. Notice that what you are looking for, the output impedance of the current source is the test voltage divided by the test current. Swap the positions of the test current on the left with the r_o term on the right to get the answer:

$$z_{out} = \frac{v_{test}}{i_{test}} = r_0 \left[1 + \frac{R_E (R_E + r_b + r_{e1})}{2R_E + r_b + r_{e1}} \cdot \left(\frac{1}{r_0} + \frac{h_{fe}}{r_b + r_{e1} + R_E} \right) \right] = r_0 \left[1 + \frac{R_E h_{fe}}{2R_E + r_b + r_{e1}} \right] + [R_E \parallel R_E + r_b + r_{e1}]$$

The physical interpretation is that the output impedance is the sum of the impedance emitter to ground (small) with r_0 multiplied by a large factor. That factor is from the way current through r_0 increases the emitter voltage. That increase reduces the base current and therefore reduces the collector current resulting in an apparently higher impedance. The effect can be substantial so this type of circuit is widely used to make high impedance current sources.

$$7.4) r_0 = \frac{V_A + V_{CE}}{I_C} = \frac{83}{4.9e-4} = 169 \text{ K}. \quad r_b = \frac{kT}{qI_{BQ}} = \frac{.0256\beta}{I_{CQ}} = 5.22 \text{ K ohms.}$$

The resistance from emitter to ground is 700 ohms in parallel with 6 K and that is too low to matter. The terms with the Early resistance are:

$$z_{out} = 1.69 \cdot 10^5 \left[1 + \frac{7 \cdot 10^4}{1400 + 5220 + 53} \right] = 11.5 \cdot 1.69 \cdot 10^5 = 1.94 \text{ Megohms.}$$


This is an order of magnitude higher than just the Early resistance. This multiplication of r_0 in circuit is an additional reason why I could forget that resistance when analyzing the primitive circuits we started with.

8.1) The two transistors have the same base-emitter voltages because they carry the same emitter currents. The Thevenin equivalent circuit for the two biasing resistors is a 1.6 volt source and 5.76 K resistor. From KVL using the equation for IC in terms of IS, VT and

VBE we have $V_{BB} - R_{BB}I_B - 2V_T \ln \left(\frac{(\beta+1)I_B}{I_S} \right) = 0$. You can solve this several ways: take


a guess (the numbers were dummed up to give a nice round answer), iterate, or use a standard tool such as MATLAB, Mathematica, Excel, etc. I used Excel and got $I_B = 1.79e-5$ and $I_C = 1.79 \text{ mA}$. VBE was 0.75 volts.

 8.2) The lower transistor is diode connected so its small signal model is just a resistor with value V_T/I_E or 14.4 ohms. The small signal model of the upper transistor has $g_m = 69.6 \text{ mA/volt}$ and $r_{\pi} = 1.45 \cdot 10^3$ ohms. In the circuit, the output resistance of the transistor from the early effect is infinite.



9.a) Neither transistor is saturated so the total emitter current of both transistors is equivalent to a single transistor with $I_S = 7.5e-16$. The Thevenin equivalent of the bias network is 1.2 volts and 6.24 K. This can be solved the same way as the last problem but just a little guessing gives a good answer. The total collector current of both together is 1 mA. Transistor Q1 is twice the size of Q2 and they have the same V_{BE} so the current will be distributed as .667 mA through Q1 and .333 mA through Q2. $V_{BE} = 0.718$ volts and the Kirchoff loop equation is balanced within 0.016 volt in 1.2 volts.

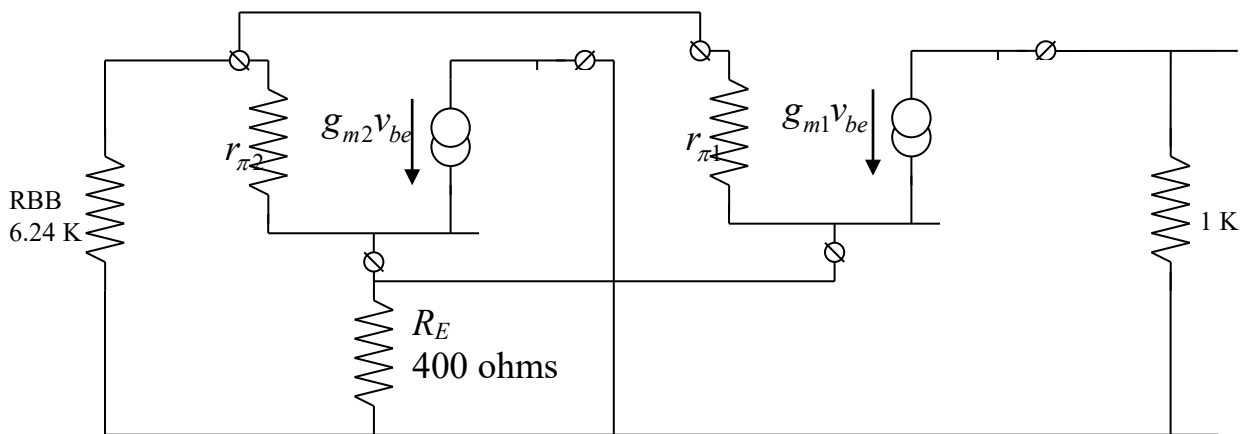9.b) The small signal model has different values of transconductance and base-emitter resistance for the two devices. In the circuit I have swapped the order of Q1 and Q2 to make the circuit easier to read. Q1 has $g_{m1} = 26$ mA/volt and $r_{\pi1} = 3876$ ohms. For Q2, the transconductance is half that and the resistance is twice that.



10) The base-emitter voltage is 0.741 volts for 1.0 mA collector current. The base current is 10 uA and the voltage at the node where RB ties to the other two resistors is $2.5 - 1e3 * 1.01e-3 = 1.49$ volts. Ohm's law gives $R_B = (1.49 - .741) / 1e-5 = 74.9$ K.