

## Engineering 1620 – Spring 2016

### Answers to the Practice Problems for Exam

1.1) Let the closed loop gain of the amplifier be  $G \equiv 1 + \frac{R2}{R1}$ . Let the voltage relative to ground at the node where C2 joins the two resistors, R, be  $v_1$ . Then the output voltage in terms of the voltage at  $v_1$  is by inspection:


$$v_{OUT} = \frac{G}{1 + s\tau_1} v_1 \text{ or } v_1 = \frac{1 + s\tau_1}{G} v_{OUT}$$

where  $\tau_1 = RC_1$ . The KCL current nodal equation at  $v_1$  is:

$$0 = v_1 \left[ \frac{1}{R} + \frac{sC_1}{1 + s\tau_1} + sC_2 \right] - \frac{v_{IN}}{R} - sC_2 v_{OUT}$$

$$Gv_{IN} = [1 + s\tau_1 + s\tau_1 + s\tau_2(1 + s\tau_1) - Gs\tau_2] v_{OUT}$$

 and  $H(s) = \frac{G}{s^2\tau_1\tau_2 + s(2\tau_1 + \tau_2 - G\tau_2) + 1}$  *qed.*



1.2) The easy part first: select an arbitrary value for R2, say 10 K, then R1 = 4 K. If R = 1 megohm, then the numerical values of the two time constants are simply the values of the capacitors expressed in microfarads. The second order Butterworth polynomial is  $s^2 + \sqrt{2}s + 1$  so by comparison we have:

$$C_1C_2 = 1 \text{ and } \sqrt{2} = 2C_1 + C_2 - 1.4C_2$$


Multiplying the second equation by  $C_2$  and eliminating  $C_1$  leaves  $0.4C_2^2 + \sqrt{2}C_2 - 2 = 0$ , the solution of which is  $C_2 = 1.083$  ufd.  $C_1 = 0.924$  ufd.

1.3) For operation with a bandwidth of 3.1 KHz, we need to divide the capacitors by

$2\pi \cdot 3.1 \cdot 10^3 = 1.948 \cdot 10^4$  but the scaling the resistor value from 1 megohm to 100 K increases the capacitors by a factor of 10. The net effect is that  $C_2 = \frac{1.08}{1.948 \cdot 10^3} = 555$  pf and  $C_1 = 474$  pf.

2.1) This is a (Wilson) current mirror with input on the left and output on the right. It might equally well be called a current source because the input side of the mirror has a fixed current rather than a time dependent signal. M3 and M1 are the matched pair that have the same  $V_{GS}$  and nearly the same  $V_{DS}$  that forces the current in M3 to be mirrored in M1. M2 increases the output impedance by cascoding the output drain current of M1. M3 provides the fixed gate voltage to the cascoding transistor but its primary purpose is to equalize the drain voltages of M1 and M3 to improve the current match.

 2.2) The output resistance of the circuit is the ratio of a change in output voltage to a consequent change in the output current. To calculate it, one needs the small signal equivalent circuit of the output side of the mirror. At low frequencies when the gate-drain capacitance of M2 can be neglected, the gate voltages of M1 and M2 are constant and hence at small signal ground. Because the small signal model has the gate of M1 grounded, the dependent current source in M1 is zero current; only the output resistance of M1 from channel length modulation is needed in the circuit model. Also add a test current,  $i_{test}$ , to drive the output of the model. The final model is simply



The current through  $r_{O1}$  is  $i_{test}$  so  $v_{gs2} = -i_{test} r_{O1}$ . The KCL equation at the drain is

$$i_{test} = -g_{m2} r_{O1} i_{test} + \frac{v_{test} - i_{test} r_{O1}}{r_{O2}}$$

Multiply through by  $r_{O2}$  and collect terms to get  $z_{out} = (1 + g_{m2} r_{O1}) r_{O2} + r_{O1}$ . This is the effect of source (or emitter degeneration) on output impedance and is one of the standard results a designer has to keep in mind all the time.

2.3) All four transistors have the same current,  $I_D = 20 \text{ uamp}$ . The transconductance is

$g_m \approx \frac{2I_D}{V_{ov}} = 1.2 \cdot 10^{-4} \text{ sie}$ . Since  $\lambda$  is small and  $V_{DS}$  is low (on M1 it is about 1 volt) we can write

$r_o \approx \frac{1}{\lambda I_D} = 2 \cdot 10^6$  and then the output resistance is  $242r_o = 4.84 \cdot 10^8 \text{ ohms}$ .

3) The starting point is to write out the gain of the amplifier. It has a single dominant pole at  $f_d = \frac{f_{GBW}}{A_{OL}}$

where  $f_{GBW}$  is the gain-bandwidth product and  $A_{OL}$  is the low frequency open-loop gain. With this:

$$A(s) = \frac{A_{OL}}{1 + j \frac{f}{f_d}} \text{ and } 1 + A(s) = A_{OL} \frac{1 + j \frac{f}{f_{GBW}}}{1 + j \frac{f}{f_d}}$$

where this assumes that  $A_{OL} \gg 1$ . In this problem  $A_{OL} = 4 \cdot 10^5$  ohms and  $f_d = \frac{2.4 \cdot 10^7}{4 \cdot 10^5} = 60 \text{ Hz}$ .

3.1) By Miller's theorem, the input should appear to have an impedance equivalent to  $C_{INT}$  scaled by the factor  $1 + A(s)$ . From the impedance of a capacitor this is

$$z = \frac{1}{j2\pi f A_{OL} C_{INT}} \left[ \frac{1 + j \frac{f}{f_d}}{1 + j \frac{f}{f_{GBW}}} \right]$$

3.2) At 1 Hz, the phase angle of the pole-zero ratio in the brackets is negligible (or to be more exact 0.94 degrees). So the impedance has a  $-89.1$  degree phase, and is essentially a 60 ufd capacitor with reactance of 2.75 K ohms.

3.3) At 1 KHz, the phase angle in the bracket is  $\tan^{-1}\left(\frac{1000}{60}\right) = 86.6$  degrees. (The denominator still has negligible imaginary part.) This moves the phase of the impedance to 3.4 degrees making it essentially a resistor. The magnitude is  $|z| \approx \frac{1}{2\pi f_d A_{OL} C_{INT}} = 44.2 \text{ ohms}$ , essentially a 44 ohm resistor.

3.4) The reactance of the 15 pf capacitance of the amplifier input impedance is 9.8 megohms so that is negligible in comparison to the 44 ohm resistor.

3.5) At 1 MHz, the phase angle of the numerator of  $z$  is 90 degrees since the imaginary part of the numerator is 16,000 times bigger than the real part. The denominator contributes a phase of -2.4 degrees so the impedance is still essentially a resistor. The magnitude is still 44.2 ohms.

In the frequency range from somewhat above the dominant pole frequency until nearly the unity gain frequency, the input impedance stays constant and resistive. The decrease in reactance of  $C_{INT}$  is offset because the amplification from the opamp is decreasing above the dominant pole frequency. The two effects have inverse dependence on frequency and so cancel. Similarly  $C_{INT}$  and the amplifier have offsetting phase shifts of nearly 90 degrees that net to near zero degrees.