

Formulae for the Memory-Challenged


General: $\frac{kT}{q} = 0.0256$ volts at room temperature (300° K).

$$R = \frac{\rho l}{A} \quad C = \frac{\epsilon A}{t}$$

Biasing: $I_C = h_{FE} I_B$

$$I_C = \frac{h_{FE} (V_{BB} - V_{BE} + R_{BB} I_{CBO})}{R_{BB} + (1 + h_{FE}) R_E} \quad I_{COPT} = \frac{V_{CC} - V_{CESAT}}{R_{DC} + (1 - \gamma) |Z_{AC}|}$$

Bipolar Transistor and Diode SS Models:

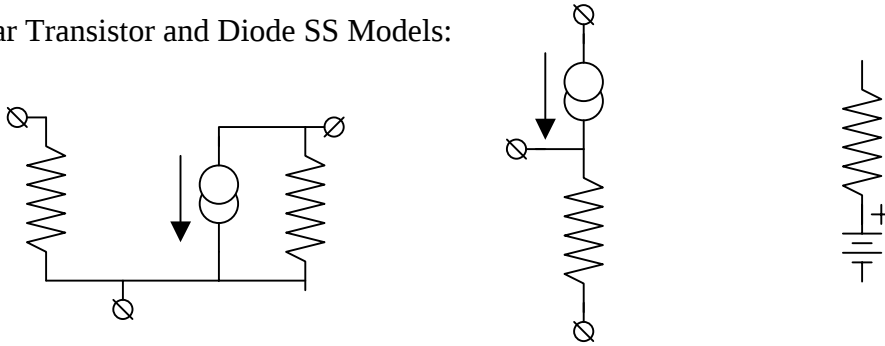

For BJTs: $r_e = \frac{kT}{qI_E}$, $g_m = \frac{I_C}{kT} = \frac{\alpha}{r_e}$, $r_\pi = r_b = (1 + h_{fe}) r_e$, $\alpha = \frac{h_{fe}}{1 + h_{fe}}$, $\beta \leftrightarrow h_{fe}$, and

$r_o = \frac{V_A + V_{CEQ}}{I_{CQ}}$. The full non-linear Shockley equation at constant V_{CE} and $I_C > 0$ is:

$$I_C = I'_s \exp\left(\frac{nqV_{BE}}{kT}\right) \text{ where } n \geq 1 \text{ and } I'_s \propto T^3 \exp\left(\frac{qV_G}{kT}\right).$$

Stage Type	Sign of Gain	Qual Gain	G(s)	Qual. Z_{in}	Z_{in}	Qual Z_{out}	Z_{out}
Common Emitter	-	high	$\frac{-\alpha Z_C}{r_e + Z_E}$	high	$R_{BB} \parallel [(1 + h_{fe})(r_e + Z_E)]$	high	Z_C
Common Base	+	high	$\frac{\alpha Z_C}{r_e + Z_1}$	low	$r_e + Z_1$	high	Z_C
Common Collector (Emitter Follower)	+	< 1	$\frac{Z_E}{r_e + Z_E}$	high	$R_{BB} \parallel [(1 + h_{fe})(r_e + Z_E)]$	low	$Z_E \parallel [r_e + Z_S / (1 + h_{fe})]$

Notes: 1.) Z_{BG} is the entire source impedance of the signal driving the base of the Common Collector stage.

2.) Z_1 is the impedance of any passive components in series with the input.

High frequency effects: parasitic capacitances

$$f_T = \frac{1}{2\pi r_e (C_\pi + C_\mu)} \quad \text{and} \quad f_\beta = \frac{1}{2\pi r_e C_\pi (1 + \beta)}$$

Equivalent input impedance at high frequencies of a CE or CC circuit exclusive of the Miller effect from C_{OB} and the base series resistance r_{bb} , is: $z_{tr}(s) \cong \frac{z_{tr}(0)}{1 + jf / f_\beta}$ and is equivalent to

an effective capacitance $C_{eff} = \frac{r_e C_\pi}{r_e + Z_E}$ across the low frequency input resistance $z_{tr}(0)$.

Widlar current sources (bipolar) have reduced output I_O from an emitter resistor R_E satisfying

$$\text{the equation: } I_O R_E = \frac{kT}{q} \ln \left(\frac{I_{REF}}{I_O} \right).$$


For long-channel MOSFETs:

$$I_{DS} = \frac{W}{L} \cdot K_N \cdot \begin{cases} 0 & \text{if } V_{GS} \leq V_{TH} \\ \left(V_{GS} - V_{TH} - \frac{(1+a)}{2} V_{DS} \right) V_{DS} & \text{if } V_{DS} \leq \frac{(V_{GS} - V_{TH})}{(1+a)} \\ \frac{(V_{GS} - V_{TH})^2}{2(1+a)} (1 + \lambda V_{DS}) & \text{if } V_{DS} \geq \frac{(V_{GS} - V_{TH})}{(1+a)} \end{cases}$$

$$I_D = \frac{W}{L} K' (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad \text{where } \lambda = 1/V_A \quad \text{in active operating mode.}$$

$$\text{MOSFET small signal model: } g_m \approx \frac{2I_{DQ}}{V_{OV}} \quad \text{and} \quad r_o = \frac{1 + \lambda V_{DSQ}}{\lambda I_{DQ}} = \frac{V_A + V_{DSQ}}{I_{DQ}}$$

“Overvoltage” is defined as: $V_{OV} \equiv |V_{GS} - V_{TH}|$ when the device is biased for operation above threshold.

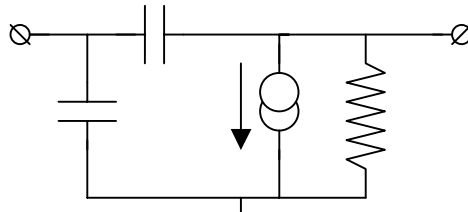

A diode with an abrupt junction operated with reverse voltage V_{REV} has capacitance:

$$C_D = \frac{C_0}{\sqrt{1 + V_{REV} / V_{BI}}}$$