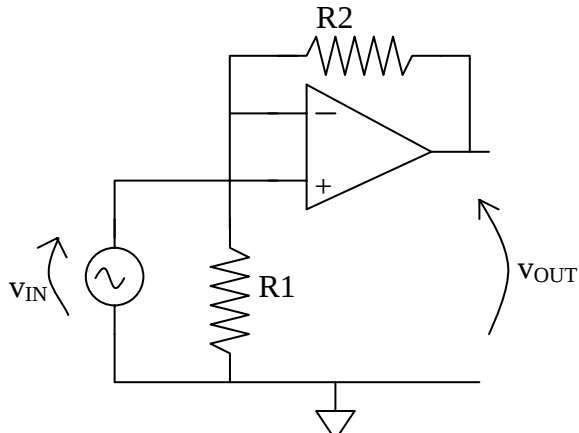



Some Basic Operational Amplifier Circuits Derived from an Ideal Model



Non-inverting Gain Block

$$\text{DC Gain: } G_0 = 1 + \frac{R_2}{R_1}$$

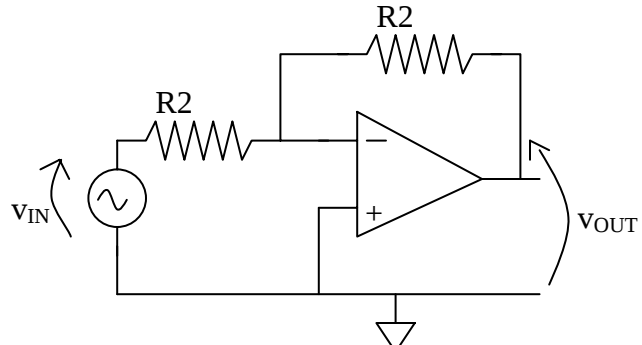
$$\text{Bandwidth: } f_C = f_{GBW} / G_0$$




Inverting Gain Block

$$\text{DC Gain: } G_0 = -\frac{R_2}{R_1}$$
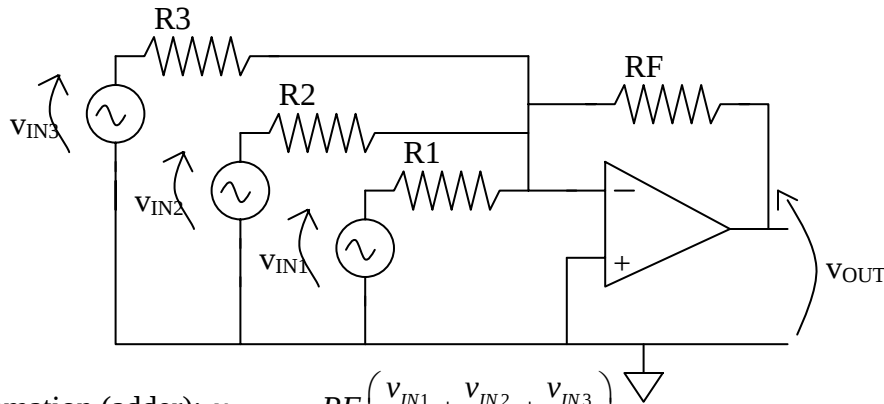
$$\text{Bandwidth: } f_C = f_{GBW} / (1 + G_0)$$



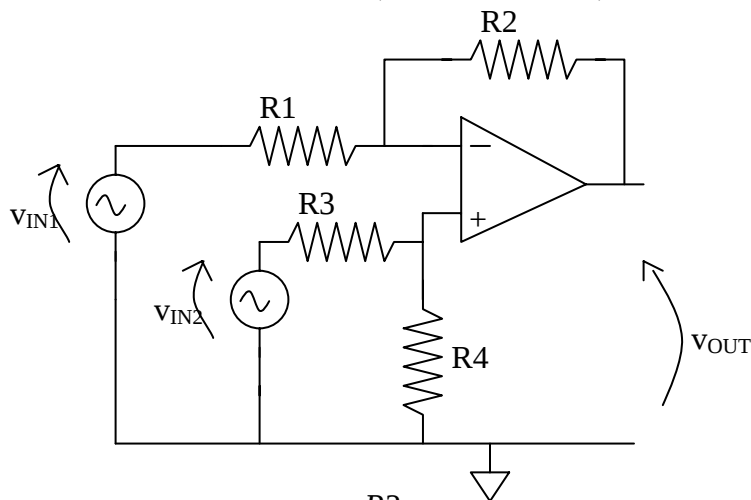
$$\text{Weighted summation (adder): } v_{OUT} = -R_F \left(\frac{v_{IN1}}{R_1} + \frac{v_{IN2}}{R_2} + \frac{v_{IN3}}{R_3} \right)$$



$$\text{Difference amplifier (subtraction): } v_{OUT} = \frac{R_2}{R_1} (v_{IN2} - v_{IN1}) \text{ if } R_1 \cdot R_4 = R_2 \cdot R_3$$

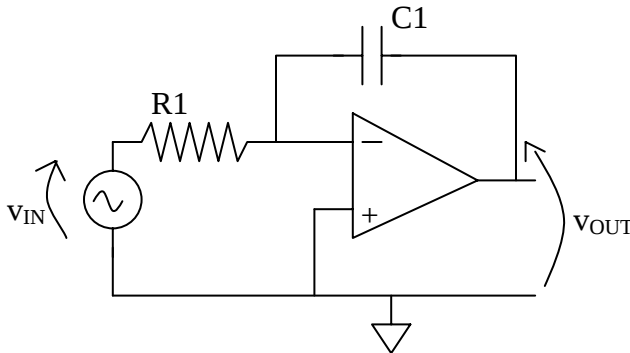
The accuracy of this differential amplifier is limited by resistor tolerances, temperature effects, and op-amp performance. More complicated circuits using multiple op-amps can do better.



Integrator: $v_{OUT} = -\frac{1}{R1 \cdot C1} \int_{-\infty}^t v_{IN}(t') dt'$


And $v_{OUT}(s) = \frac{-1}{sRC} v_{IN}(s)$

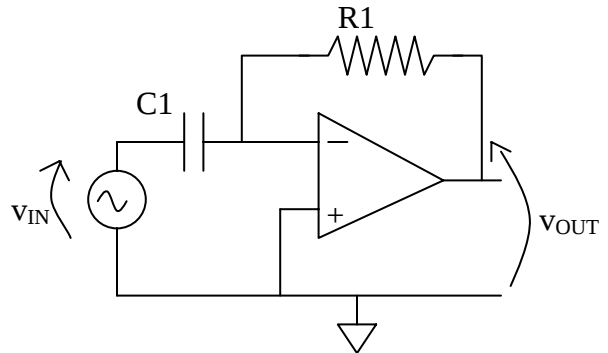With this circuit, DC conditions may require special care because the integral of a constant eventually becomes infinite.




Differentiator: $v_{OUT} = -R1 \cdot C1 \frac{dv_{IN}}{dt}$

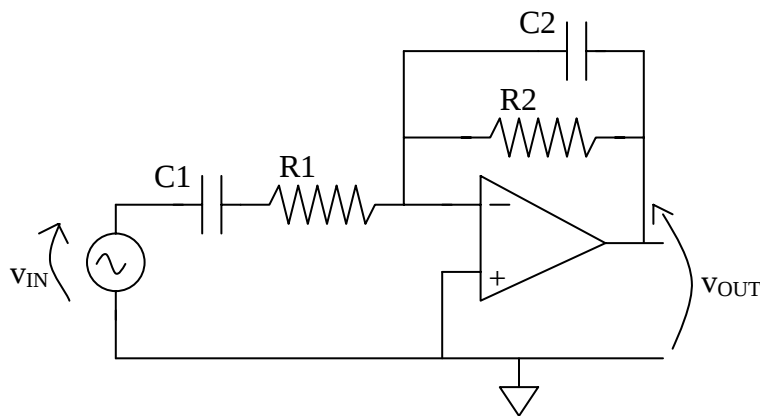NOTE: because of bandwidth limitations, this circuit does not usually work very well.



Filter with two simple poles (high-pass and low-pass):
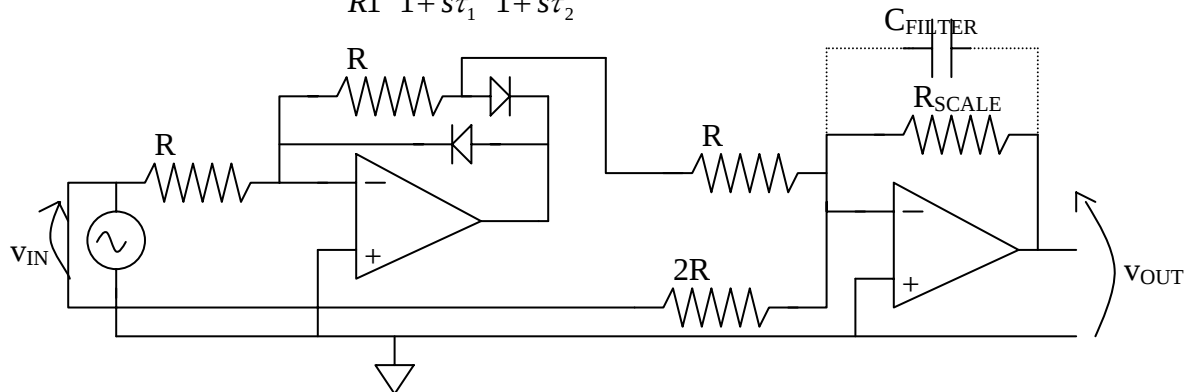
$$H(s) = -\frac{R2}{R1} \cdot \frac{s\tau_1}{1+s\tau_1} \cdot \frac{1}{1+s\tau_2} \text{ where } \tau_1 = R1 \cdot C1 \text{ and } \tau_2 = R2 \cdot C2$$



Precision rectifier for low voltages with optional filtering. $v_{OUT} = \frac{R_{SCALE}}{2R} |v_{IN}|$