

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROFS. IRIS BAHAR
SEPTEMBER 11, 2019
LECTURE 3: KARNAUGH MAPS & LOGIC MINIMIZATION

LECTURE SLIDES

- I will post lecture slides on the course webpage within 2 days of class
- Access the lecture slides from:
www.brown.edu/Departments/Engineering/Courses/Enl63/home.html
- Updated syllabus and other course materials are also available online

LABORATORY ASSIGNMENTS

- Lab kits and lab manuals are now ready for pickup
 - See George Worth in B&H325 for pickup (remember your \$60 --- check or cash)
- Lab manuals can also be found on the course webpage
- TA will start holding lab hours on Thursday
 - Schedule can be found on the course webpage
- We created a Piazza page as a discussion forum for issues/questions on lab assignments.
 - Join by going to: piazza.com/brown/fall2019/engn1630

LAB TUTORIAL

- Andrew Duncombe (one of our TAs) will be holding a tutorial session tomorrow (Thursday, Sept. 12) @ 5pm in the lab to go over the basics of building digital electronics
 - How to use a breadboard
 - How to wire up a breadboard
 - How to connect to a power source
 - Etc.
- Lab: B&H196

BOOLEAN AXIOMS

Axiom	Dual	Name
A1 $B = 0$ if $B \neq 1$	A1' $B = 1$ if $B \neq 0$	Binary field
A2 $\bar{0} = 1$	A2' $\bar{1} = 0$	NOT
A3 $0 \cdot 0 = 0$	A3' $1 + 1 = 1$	AND/OR
A4 $1 \cdot 1 = 1$	A4' $0 + 0 = 0$	AND/OR
A5 $0 \cdot 1 = 1 \cdot 0 = 0$	A5' $1 + 0 = 0 + 1 = 1$	AND/OR

Theorem	Dual	Name
T1 $B \cdot 1 = B$	T1' $B + 0 = B$	Identity
T2 $B \cdot 0 = 0$	T2' $B + 1 = 1$	Null Element
T3 $B \cdot B = B$	T3' $B + B = B$	Idempotency
T4 $\overline{\overline{B}} = B$		Involution
T5 $B \cdot \overline{B} = 0$	T5' $B + \overline{B} = 1$	Complements

BOOLEAN THEOREMS OF SEVERAL VARIABLES

Theorem	Dual	Name
T6 $B \cdot C = C \cdot B$	T6' $B + C = C + B$	Commutativity
T7 $(B \cdot C) \cdot D = B \cdot (C \cdot D)$	T7' $(B + C) + D = B + (C + D)$	Associativity
T8 $(B \cdot C) + B \cdot D = B \cdot (C + D)$	T8' $(B + C) \cdot (B + D) = B + (C \cdot D)$	Distributivity
T9 $B \cdot (B + C) = B$	T9' $B + (B \cdot C) = B$	Covering
T10 $(B \cdot C) + (B \cdot \overline{C}) = B$	T10' $(B + C) \cdot (B + \overline{C}) = B$	Combining
T11 $(B \cdot C) + (\overline{B} \cdot D) + (C \cdot D) = B \cdot C + \overline{B} \cdot D$	T11' $(B + C) \cdot (\overline{B} + D) \cdot (C + D) = (B + C) \cdot (\overline{B} + D)$	Consensus
T12 $\overline{B_0 \cdot B_1 \cdot B_2 \dots} = (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12' $\overline{B_0 + B_1 + B_2 \dots} = (\overline{B_0} \cdot \overline{B_1} \cdot \overline{B_2} \dots)$	De Morgan's Theorem

CANONICAL FORM

- Canonical form: a unique representation for a Boolean function
 - Given a fixed ordering of the input variables
 - Two equivalent functions have the same canonical form
 - Examples: truth table, canonical sum, canonical product

DEFINITIONS

- Literals x_i or x_i'
- Product Term $x_2 x_1'$
- Sum Term $x_2 + x_1' + x_0$
- Minterm** of n variables: A product of n variables in which every variable appears exactly once.
- Maxterm** of n variables: A sum of n variables in which every variable appears exactly once.

MINTERM AND MAXTERM

Id	a	b	c _{in}	carryout	
0	0	0	0	0	a+b+c
1	0	0	1	0	a+b+c'
2	0	1	0	0	a+b'+c
3	0	1	1	1	a' b c
4	1	0	0	0	a'+b+c
5	1	0	1	1	a b'c
6	1	1	0	1	a b c'
7	1	1	1	1	a b c

↑ minterm

↑ maxterm

Note that the literals are complemented for MAXTERMS

MINIMIZING A FUNCTION

- Note that a canonical representation of a function is not always the most compact way to represent a function
- To implement a function in hardware we want to minimize the number of literals and number of terms
- We can apply Boolean Theorems to minimize a function, but this can be cumbersome and lacks a visual understanding
- Instead, represent the function using Karnaugh maps...

REPRESENTING FUNCTIONS WITH KARNAUGH MAPS

Id	A	B	f(A, B)		A = 0	A = 1
0	0	0	m ₀	B = 0	0	$\overline{A}\overline{B}$
1	0	1	m ₁		2	$\overline{A}B$
2	1	0	m ₂	B = 1	1	$A\overline{B}$
3	1	1	m ₃		3	AB

- How do we represent $f(A,B) = A+B$ on the K-map

On the K-map:


Id	A	B	f(A, B)
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

$$f(A,B) = A + B$$

TWO VARIABLE K-MAPS

Id	a	b	f(a, b)
0	0	0	f(0, 0)
1	0	1	f(0, 1)
2	1	0	f(1, 0)
3	1	1	f(1, 1)

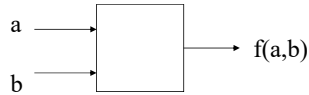2 variables means we have 2^2 entries and thus we have 2 to the 2^2 , or 2^4 possible functions for 2 bits, which is 16.




THREE VARIABLES K-MAPS

Id	a	b	c	f(a,b,c)
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	0
6	1	1	0	1
7	1	1	1	0

- What does the k-map look like?

CORRESPONDING K-MAP

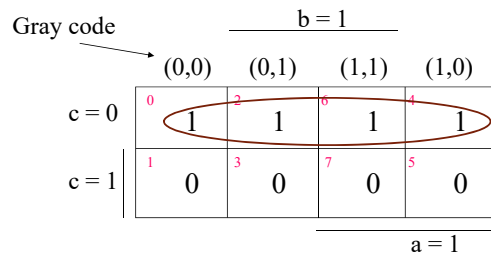

$$f(a,b,c) = c'$$

This is a minimum cover for this function

KARNAUGH MAPS (K-MAPS)

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y	AB			
C	00	01	11	10
0	1	0	0	0
1	1	0	0	0

Y	AB			
C	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

- Boolean expressions can be minimized by combining terms
- Karnaugh maps (K-maps) minimize equations graphically
- $PA + \bar{P}\bar{A} = P$

K-MAP

- Circle 1's in adjacent squares
- In the Boolean expression, include only the literals that are true for each square

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	0	0	0

$$y(A,B)=A'B'$$

MINTERM AND MAXTERM

Id	a	b	c _{in}	carryout
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

a+b+c

a+b+c'

a+b'+c

a'b'c

a'+b+c

a'b'c

a'bc'

abc

What does the K-map look like?

maxterm

minterm

ANOTHER 3-INPUT EXAMPLE

Id	a	b	c	f(a,b,c)
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	-
7	1	1	1	1

22

CORRESPONDING K-MAP

		b = 1			
		(0,0)	(0,1)	(1,1)	(1,0)
c = 0	0	0	1	-	1
c = 1	1	0	0	1	1

a = 1

$$f(a,b,c) = a + bc'$$

Adding the don't care term to the ON set allows for greater reduction in the functional representation (fewer literals and product terms)

YET ANOTHER EXAMPLE

Id	a	b	c	f(a,b,c,d)
0	0	0	0	1
1	0	0	1	1
2	0	1	0	-
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

24

CORRESPONDING K-MAP

	$b = 1$			
	(0,0)	(0,1)	(1,1)	(1,0)
$c = 0$	0 1	2 -	6 0	4 1
$c = 1$	1 1	3 0	7 0	5 1
	$a = 1$			

$f(a,b,c) = b'$

4-INPUT K-MAP

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

	Y			
	AB			
	00	01	11	10
00				
01				
11				
10				

4-INPUT K-MAP

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

	Y			
	AB			
	00	01	11	10
00	1	0	0	1
01	0	1	0	1
11	1	1	0	0
10	1	1	0	1

4-INPUT K-MAP

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		AB			
		00	01	11	10
CD	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

$$Y = \bar{A}C + \bar{A}BD + A\bar{B}\bar{C} + \bar{B}\bar{D}$$