


**BROWN**  
School of Engineering

## DIGITAL ELECTRONICS SYSTEM DESIGN


FALL 2019  
PROF. IRIS BAHAR  
SEPTEMBER 23, 2019  
LECTURE 6: COMBINATIONAL LOGIC BLOCKS
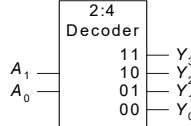
### DECODER: DEFINITION

- $N$  inputs,  $2^N$  outputs
- One-hot outputs: only one output HIGH at once



$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

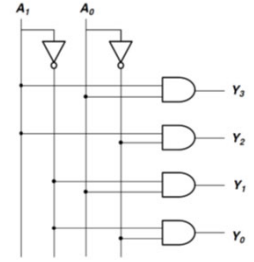


### LOGIC FUNCTIONS USING DECODERS

- $N:2^N$  decoder can be used to implement any function of  $N$  variables

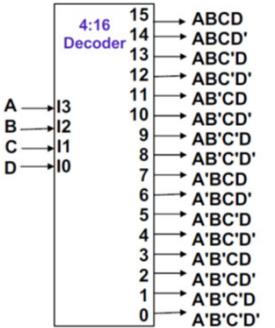
**How?**

- Connect variables to inputs
- Represent function using minterm canonical form



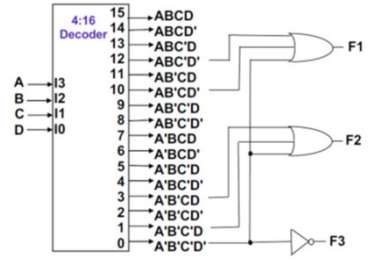
### LOGIC FUNCTIONS USING DECODERS

- $F1 = A'B'C'D' + AB'CD' + ABC'D'$
- $F2 = A'B'C' + A'B'CD$
- $F3 = A+B+C+D$




## DECODER WITH ENABLE

 

E	A <sub>1</sub>	A <sub>0</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

- X: don't care input
- Note that E, A<sub>0</sub>, A<sub>1</sub> = 0XX covers 000, 001, 010, 011

## DECODER WITH ENABLE

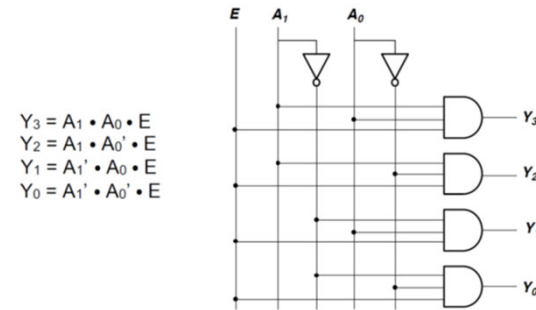


$$Y_3 = A_1 \cdot A_0 \cdot E$$

$$Y_2 = A_1 \cdot A_0' \cdot E$$

$$Y_1 = A_1' \cdot A_0 \cdot E$$

$$Y_0 = A_1' \cdot A_0' \cdot E$$


## ALTERNATIVE IMPLEMENTATIONS

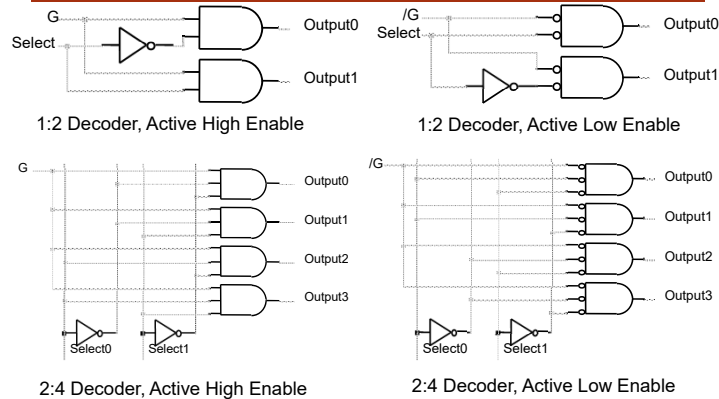
 
## ENCODERS

- Opposite of decoders
- Binary encoders:  $I_2^{n-1} \dots I_0$ 
  - $2^N$  inputs and N outputs
- Description:
  - At most one input  $I_i = 1$
  - $(y_{n-1}, \dots, y_0) = 1$  (according to the encoding for  $i$ ) if  $I_i = 1$  &  $En = 1$
  - $(y_{n-1}, \dots, y_0) = 0$  otherwise
  - $A=1$  if  $En = 1$  & one 1 s.t.  $I_i = 1$
  - $A=0$  otherwise


What happens if more than one input  $I_i = 1$ ?



## PRIORITY ENCODER

- Highest numbered inputs have priority when multiple inputs are asserted at the same time
- Example: 4-to-2 priority encoder

I3	I2	I1	I0	Y1	Y0	None
1	X	X	X	1	1	0
0	1	X	X	1	0	0
0	0	1	X	0	1	0
0	0	0	1	0	0	0
0	0	0	0	0	0	1

 


$$Y1 = I3 + I3'I2 = I3 + I2$$

$$Y0 = I3 + I3'I2'I1 = I3 + I2'I1$$


$$\text{None} = I3'I2'I1'I0'$$
 
## EXAMPLE: MICROPROCESSOR INTERRUPTS

- In order for devices to get service, they interrupt the microprocessor
- Most important requests are given priority



## SHIFTER

 


$$y_i = x_{i-1} \text{ if } En = 1, s = 1, \text{ and } d = L$$

$$= x_{i+1} \text{ if } En = 1, s = 1, \text{ and } d = R$$

$$= x_i \text{ if } En = 1, s = 0$$

$$= 0 \text{ if } En = 0$$

Can be implemented with a mux

 

## COMBINATIONAL BLOCK IN LABS

- Check your kits for chips that implement these combinational blocks
  - Decoder/demultiplexer
  - Multiplexor
  - Shift register
  - Comparator
- Use to your advantage

## TRANSISTORS AND BUILDING LOGIC GATES WITH CMOS TRANSISTORS

## FEATURE SIZE ( $\lambda$ VS. ABSOLUTE DIMENSIONS)

- Feature size: minimum distance between source and drain of transistor
- $\lambda$  rules:
  - If  $\lambda=45\text{nm}$  and  $L = 2\lambda$ , feature size 90nm
- Absolute dimensions:
  - e.g, 45nm library
  - Min. feature size = 50nm
  - $L_{\text{effective}} \approx 45\text{nm}$
- $\lambda$  rules can be more convenient than absolute dimensions since we don't need to update sizes for new technologies


 
 



FIG 2.6 Transistor dimensions

## THE INSIDE OF AN INTEGRATED CIRCUIT

 

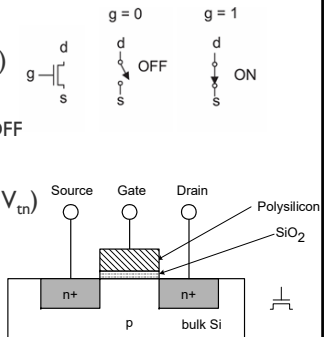
## NMOS TRANSISTOR

- $g=0$ : gate is at low voltage ( $V_{gs} < V_{tn}$ )
  - p-type body is at low voltage
  - source and drain junction diodes are OFF
  - transistor is OFF (no current flows)
- $g=1$ : gate is at a high voltage ( $V_{gs} \geq V_{tn}$ )
  - negative charge attracted to body
  - inverts a channel under gate to n-type
  - transistor is ON (current flows)
  - transistor acts as resistor




## PMOS TRANSISTOR

- g=0:** gate is at low voltage ( $|V_{gs}| > |V_{tp}|$ )
  - positive charge attracted to body
  - inverts channel under gate to p-type
  - transistor is **ON** (current flows)
- g=1:** gate is at a high voltage ( $|V_{gs}| \leq |V_{tp}|$ )
  - n-type body is at high voltage
  - Source and drain junctions are OFF
  - transistor is **OFF** (no current flows)

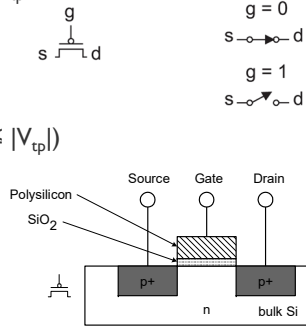


## THRESHOLD VOLTAGE CONCEPT

 

- Depletion region:** area devoid of mobile carriers (holes)
- Inversion layer:** n-channel region under oxide
- The value of  $V_{GS}$  where strong inversion occurs is called the threshold voltage,  $V_T$


## NMOS CUTOFF

- No channel
- $I_{ds} = 0$

 
 
## NMOS LINEAR

- Channel forms
- Current flows from d to s
  - $e^-$  from s to d
- $I_{ds}$  increases with  $V_{ds}, V_{gs}$
- Similar to linear resistor



## NMOS SATURATION

- Channel pinches off
- $I_{ds}$  independent of  $V_{ds}$
- We say current saturates
- Similar to current source

