

BROWN  
School of Engineering

## DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019  
PROF. IRIS BAHAR  
SEPTEMBER 30, 2019  
LECTURE 8: CMOS GATES & INTRODUCTION TO VERILOG

## CLARIFICATION ABOUT DEADLINES

- Labs are due in groups:
  - Group 1: labs 0-3 due by **Sunday, Oct. 6 (lab 1 & 2 both required)**
  - Group 2: labs 4-9 due by **Sunday, Nov. 17 (lab 9, and either 7 or 8 required)**
  - Group 3: labs A and B due by **Friday, Dec. 6**
  - Group 4: labs C and D due by **Thursday, Dec. 13 (one of lab B, C, D required)**
- The last week before the final exam can be used as a grace period:
  - *Up to one additional lab from group 1-3 can be checked off between Dec. 7-13*
  - Labs may be checked off earlier, but if completed after the group deadline, they will count as being checked off during exam week
  - *Only one lab a day credited in exam week*
- **Plan ahead! Don't wait until exam week to finish all your labs!**

## IBM STUDENT DESIGN WORKSHOP

**WHEN: October 12, 2019**

**TIME: 9:00am-5:00pm**

- Open to all students, but geared mostly toward engineering students in their junior year.
- IBM facilitators will guide students through design for tackling a current pressing problem (e.g., within the or for a course)





- Advanced registration is required. Please reserve your spot by *Thursday, Oct. 3* at <https://forms.gle/ynUg4rixsJbTy8Qj6>
- Email Elizabeth Austin or Jennifer Casasanto for additional questions.

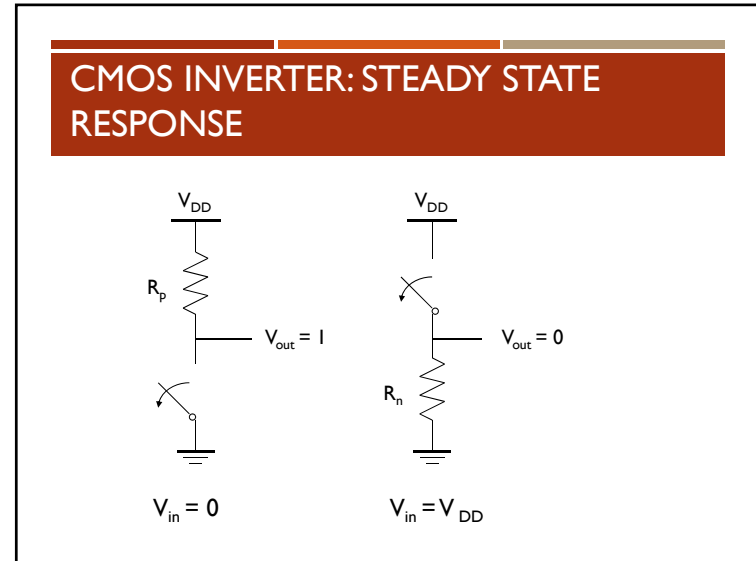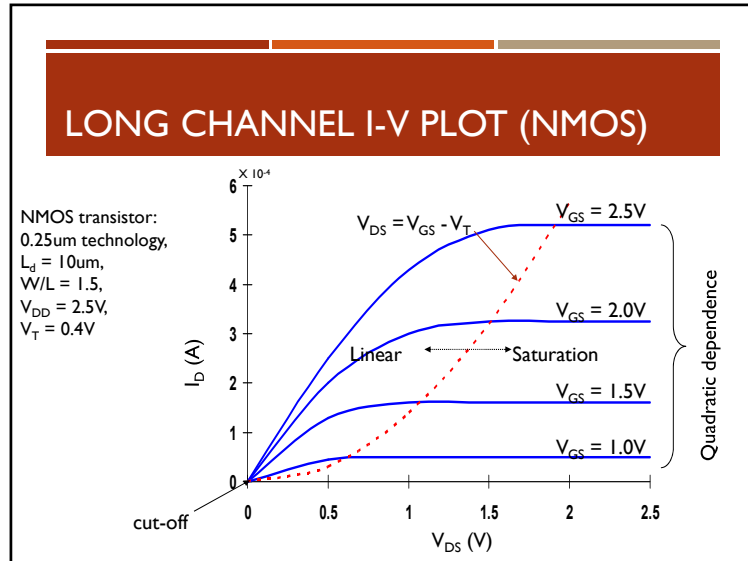
## NMOS I-V SUMMARY

- Shockley 1<sup>st</sup> order transistor models


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_{th} & \text{cutoff} \\ \beta \left( V_{gs} - V_{th} - V_{ds}/2 \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_{th})^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$



- ### CMOS PROPERTIES
- Full rail-to-rail swing → high noise margins
    - Logic levels independent of device sizes → *ratioless*
  - Always a path to  $V_{dd}$  or GND in steady state → less sensitive to noise
  - nearly zero steady-state input current
  - No direct path steady-state between power and ground
    - no static power dissipation
  - Propagation delay is a function of load capacitance and resistance of transistors

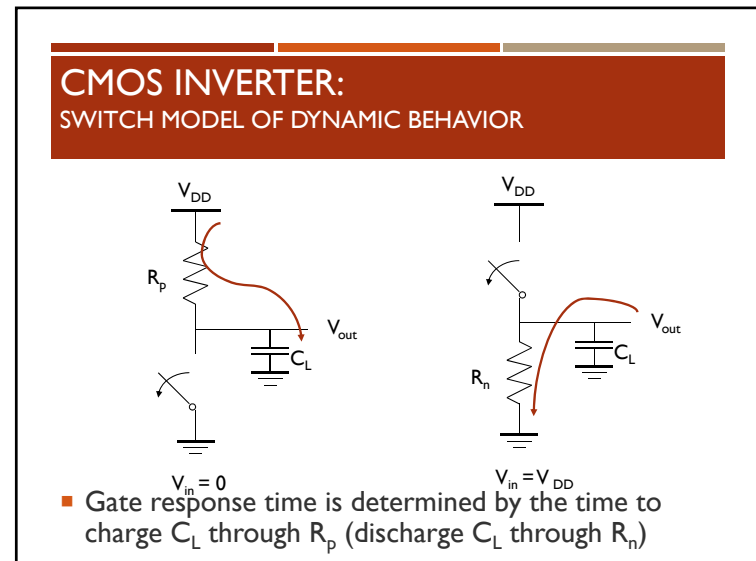

## CMOS INVERTER: DYNAMIC BEHAVIOR

 


- Transient, or dynamic, response determines the maximum speed at which a device can be operated.

$$t_{pHL} = f(R_n, C_L)$$
 
## STATIC COMPLEMENTARY CMOS

- Pull-up network (PUN) and pull-down network (PDN)




- PMOS transistors only
- pull-up: make a connection from  $V_{DD}$  to  $F$  when  $F(In_1, In_2, \dots, In_N) = 1$
- NMOS transistors only
- pull-down: make a connection from  $F$  to GND when  $F(In_1, In_2, \dots, In_N) = 0$


PUN and PDN are dual logic networks
 
## CONSTRUCTION OF PDN

- NMOS devices in series implement a NAND function



 - NMOS devices in parallel implement a NOR function



## DUAL PUN AND PDN

- PUN and PDN are dual networks


- DeMorgan's theorems

$$\overline{A + B} = \overline{A} \cdot \overline{B} \quad [!(A + B) = !A \cdot !B \text{ or } !(A | B) = !A \& !B]$$


$$\overline{A \cdot B} = \overline{A} + \overline{B} \quad [!(A \cdot B) = !A + !B \text{ or } !(A \& B) = !A | !B]$$

- a parallel connection of transistors in the PUN corresponds to a series connection of the PDN
- Complementary gate is naturally inverting (NAND, NOR, AOI, OAI)
- Number of transistors for an N-input logic gate is  $2N$

## CMOS NAND

 

## CMOS NOR

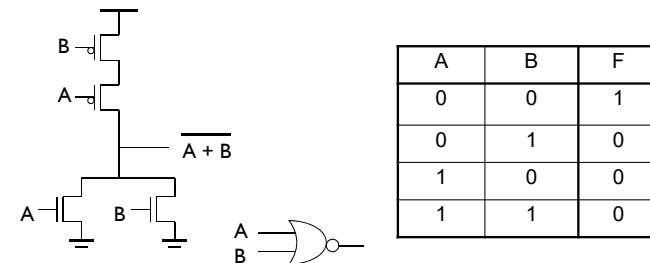


## PULL UP RESISTORS AND TRISTATE DRIVERS

- Lab 2 discusses use of pull-up resistors and tristate drivers
- Why use them?

## INTRODUCTION TO THE VERILOG HARDWARE DESCRIPTION LANGUAGE

## 2:4 DECODER WITH ENABLE

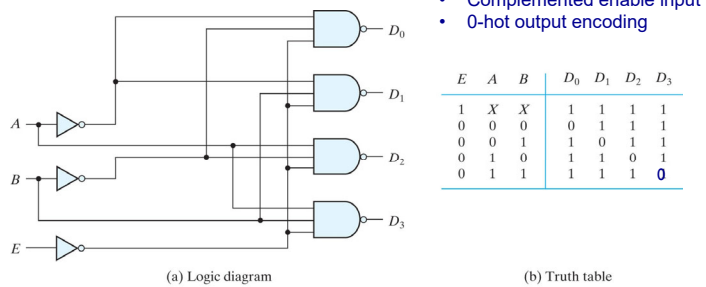

- Complemented enable input
- 0-hot output encoding

E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Copyright (c) 2011 Pearson Education, publishing as Prentice Hall

## 2:4 DECODER: STRUCTURAL

```
// Gate-level (structural) description of 2-to-4 decoder
module decoder_2x4_gates(D, A, B, enable_);
    output    [3:0] D;
    input     A, B, enable_;
    wire      A_not, B_not, enable_not;

    not G1(A_not, A);
    not G2(B_not, B);
    not G3(enable_not, enable_);
    nand G4(D[0], A_not, B_not, enable_not);
    nand G5(D[1], A_not, B, enable_not);
    nand G6(D[2], A, B_not, enable_not);
    nand G7(D[3], A, B, enable_not);
endmodule
```

multi-bit output

## 2:4 DECODER: BEHAVIORAL (DATAFLOW)

```
// Behavioral (dataflow) description of 2-to-4 decoder
module decoder_2x4_df(D, A, B, enable_);
    output    [3:0] D;
    input     A, B, enable_;

    assign D[0] = ~((~A) & (~B) & (~enable_));
    assign D[1] = ~((~A) & B & (~enable_));
    assign D[2] = ~(A & (~B) & (~enable_));
    assign D[3] = ~(A & B & (~enable_));
endmodule
```

left hand side must be a wire (or output)

## 2:4 DECODER: BEHAVIORAL 2 (DATAFLOW)

```
// Behavioral description of 2-to-4 decoder
// inputs A and B replaced with I[1:0]
module decoder_2x4_beh2(D, I, enable_);
    output    [3:0] D;
    input     [1:0] I;
    input     enable_;

    wire      [3:0] Di;

    assign Di = (I == 2'b11) ? 4'b0111:
                (I == 2'b10) ? 4'b1011:
                (I == 2'b01) ? 4'b1101: 4'b1110;

    assign D = (enable_ == 1'b0) ? Di : 4'b1111;
endmodule
```

conditional continuous assignment statement