



**BROWN**  
School of Engineering

## DIGITAL ELECTRONICS SYSTEM DESIGN

**FALL 2019**  
**PROF. IRIS BAHAR**  
OCTOBER 2, 2019  
LECTURE 9: MORE VERILOG & CMOS TRANSIENT BEHAVIOR


## MORE TUTORIALS FOR VERILOG

- On the course website you can find some useful links to additional Verilog examples
  - Example of a 3 bit counter
  - Blocking vs. non-blocking assignments within *always* blocks
  - State machine design for a Coke dispenser

## DATASHEETS FOR PARTS

- All parts provided for you in our kits come with datasheets
  - Pin layout in package
  - Schematic design
  - Specify operating conditions
  - Provide description of how to operate chip correctly to get desired output
- The datasheets can be downloaded from the course webpage (FullDataSheets-ENGNI630.zip)
  - Please feel free to refer to these datasheets to help answer some questions you have for the lab assignments.

## 2:4 DECODER WITH ENABLE

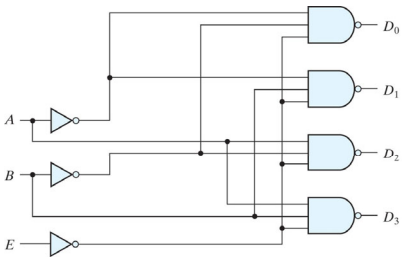

(a) Logic diagram

- Complemented enable input
- 0-hot output encoding

E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Copyright © 2013 Pearson Education, publishing as Prentice Hall

## 2:4 DECODER: STRUCTURAL

```
// Gate-level (structural) description of 2-to-4 decoder
module decoder_2x4_gates(D, A, B, enable_);
  output      [3:0] D;
  input       A, B, enable_;
  wire       A_not, B_not, enable_not;

  not G1(A_not, A);
  not G2(B_not, B);
  not G3(enable_not, enable_);
  nand G4(D[0], A_not, B_not, enable_not);
  nand G5(D[1], A_not, B, enable_not);
  nand G6(D[2], A, B_not, enable_not);
  nand G7(D[3], A, B, enable_not);
endmodule
```

multi-bit output

## 2:4 DECODER: BEHAVIORAL (DATAFLOW)

```
// Behavioral (dataflow) description of 2-to-4 decoder
module decoder_2x4_df(D, A, B, enable_);
  output      [3:0] D;
  input       A, B, enable_;

  assign D[0] = ~((~A) & (~B) & (~enable_));
  assign D[1] = ~((~A) & B & (~enable_));
  assign D[2] = ~(A & (~B) & (~enable_));
  assign D[3] = ~(A & B & (~enable_));

endmodule
```

left hand side must be a wire (or output)

## 2:4 DECODER: BEHAVIORAL 2 (DATAFLOW)

```
// Behavioral description of 2-to-4 decoder
// inputs A and B replaced with I[1:0]
module decoder_2x4_beh2(D, I, enable_);
  output      [3:0] D;
  input       [1:0] I;
  input       enable_;

  wire       [3:0] Di;

  assign Di = (I == 2'b11) ? 4'b0111:
             (I == 2'b10) ? 4'b1011:
             (I == 2'b01) ? 4'b1101: 4'b1110;

  assign D = (enable_ == 1'b0) ? Di : 4'b1111;
endmodule
```

conditional continuous assignment statement

## VERILOG: CONTINUOUS ASSIGNMENTS

- Drive values onto a net
- Left hand side must be a **wire**, (or output)
- Continuous assignments are always active
- The assignment expression is evaluated as soon as one of the right-hand side operands changes
- Operands on the right-hand side can be registers or wires

## VERILOG: PROCEDURAL ASSIGNMENTS

- Updates values of `reg` variables
- Value placed on a variable remains unchanged until another procedural assignment
- Not to be confused with continuous assignment (!) where the left-hand side is continuously driven

## VERILOG: INITIAL BLOCKS

- An `initial` block:
  - starts at time 0
  - executes exactly once during a simulation
  - executes independently of other blocks
  - `initial` is **not synthesizable** so should not be used except for testbenches or algorithm development
  - Everything within the block concurrently active
  - When all processes are done, the block expires

## VERILOG: INITIAL BLOCKS

```

module stimulus // testbench
reg a, b, m;

initial
  m = 1'b0; // single statement; does not need begin/end

initial
begin
  #5 a = 1'b1;
  #25 b = 1'b0;
end

initial
  #50 $finish;

endmodule

```

## VERILOG: ALWAYS

- An `always` block:
  - starts at time 0
  - executes statements continuously in a looping fashion, sequentially
  - executes independently of other blocks
- Keyword `always @`(sensitivity list)
  - Sensitivity list includes variables on right side of assignment statements inside block

## VERILOG: ALWAYS

```

module clock_gen // testbench
reg clock;

initial
  clock = 1'b0; // initialize clock at time zero

// Toggle clock every half-cycle (time period = 20)
always
  #10 clock = ~clock;

initial
  #1000 $finish;

endmodule

```

## VERILOG: ALWAYS

```

module pass_input(clock, in, out);
input  clock, in;
output reg out;

// Toggle clock every half-cycle
always @(clock)
begin
  out = in;
end

endmodule

```

## BLOCKING AND NON-BLOCKING ASSIGNMENTS

- Blocking assignments ( $X=A$ )
  - executed in the order they appear in a procedural block
  - completes the assignment before continuing on to next statement
- Non-blocking assignments ( $X<=A$ )
  - allow simultaneous scheduling
  - completes in zero time and doesn't change the value of the target until "end" is reached

## BLOCKING AND NON-BLOCKING ASSIGNMENTS

- Example: swap

```

always @(posedge CLK)
begin
  temp = B;
  B = A;
  A = temp;
end

```

```

always @(posedge CLK)
begin
  A <= B;
  B <= A;
end

```

## 2:4 DECODER: BEHAVIORAL 3

```

module decoder_2x4_beh3(D, I, enable_);
output      [3:0] D;
input       [1:0] I;
input       enable_;
reg         [3:0] Di;

always @(I)
begin
case (I)
2'b11: Di<=4'b0111;
2'b10: Di<=4'b1011;
2'b01: Di<=4'b1101;
default: Di<=4'b1110;
endcase
end
assign D = (enable_ == 1'b0) ? Di : 4'b1111;
endmodule
    
```

Annotations in the original image:

- Assigned in a procedural block: points to the `reg` declaration.
- Sensitivity list: points to the `@(I)` in the `always` block.
- Procedural block: points to the `begin` block.
- Non-blocking assignments: points to the assignment statements in the `case` block.

## 2:4 DECODER: TESTBENCH

```

`timescale 1 ns / 100 ps
module decoder_2x4_testbench;
wire      [3:0] D; // for instance outputs
reg       enable_, [1:0] I; // for instance inputs

decoder_2x4_beh3 M1(D, I, enable_); // instance to be tested
initial
begin
enable_ = 1'b1; // initialize inputs
I = 2'b0;
#4 enable_ = 1'b0;
#10 $finish; // end simulation
end

always
begin
#1 I = I + 1'b1;
end
endmodule
    
```

## NMOS I-V SUMMARY

- Shockley 1<sup>st</sup> order transistor models


$$I_{ds} = \begin{cases} 0 & V_{gs} < V_{th} & \text{cutoff} \\ \beta (V_{gs} - V_{th} - V_{ds}/2) V_{ds} & V_{gs} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_{th})^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

$$\beta = \mu C_{ox} \frac{W}{L}$$

where  $C_{ox}$  is the capacitance per unit area of  $SiO_2$
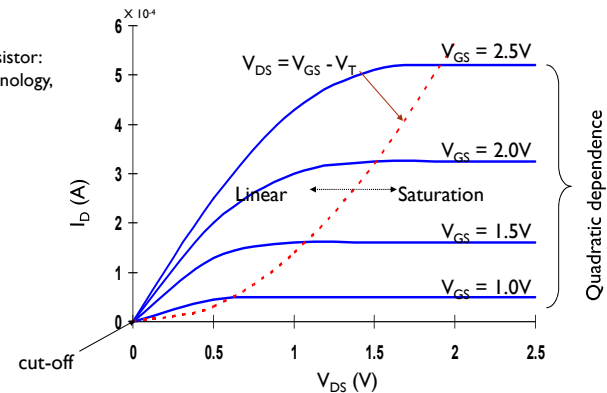
## LONG CHANNEL I-V PLOT (NMOS)

NMOS transistor:  
 0.25um technology,  
 $L_d = 10\mu m$ ,  
 $W/L = 1.5$ ,  
 $V_{DD} = 2.5V$ ,  
 $V_T = 0.4V$



## VOLTAGE TRANSFER CHARACTERISTICS

- What happens when input voltage is not “at rail”
- $V_{in} < V_{DD}$ , or  $V_{in} > Gnd$ ?
- If the transistor is ON, then voltage at output will change, but will not go to rail.


## TRANSFORMING PMOS I-V LINES

- Want common coordinate set  $V_{in}$ ,  $V_{out}$ , and  $I_{Dn}$


$$I_{Dsp} = -I_{Dsn}$$

$$V_{GSn} = V_{in}; V_{GSp} = V_{in} - V_{DD}$$

 
$$V_{DSn} = V_{out}; V_{Dsp} = V_{out} - V_{DD}$$




## CMOS INVERTER I-V CURVES

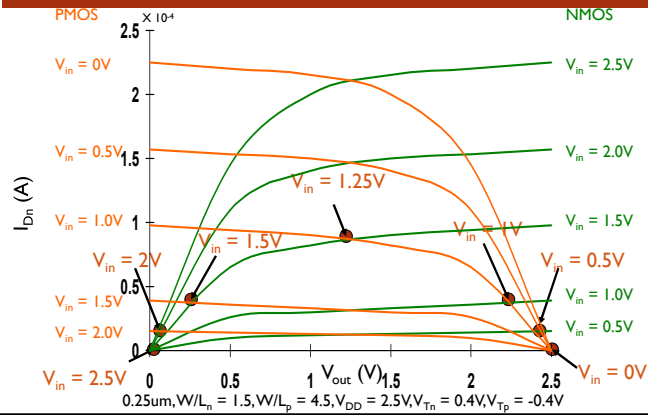

## CMOS INVERTER VTC

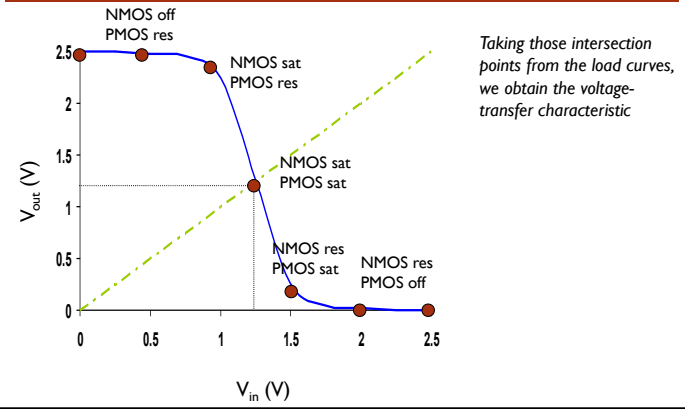
 
### CMOS INVERTER: SWITCH MODEL OF DYNAMIC BEHAVIOR



- Gate response time is determined by the time to charge  $C_L$  through  $R_p$  (discharge  $C_L$  through  $R_n$ )

### SWITCHING THRESHOLD

- Define  $V_M$  to be the point where  $V_{in} = V_{out}$  (both PMOS and NMOS in saturation since  $V_{DS} = V_{GS}$ )
- If  $V_M = V_{DD}/2$ , then this implies *symmetric rise/fall* behavior for the CMOS gate
- Recall at saturation,  $I_D = (k'/2)(W/L)(V_{GS} - V_{th})^2$ 
  - where  $k'_n = \mu_n C_{ox} = \mu_n \epsilon_{ox} / t_{ox}$
- Setting  $I_{Dp} = -I_{Dn}$ 


$$\frac{k'_n W_n}{2 L_n} (V_M - V_{tn})^2 = \frac{k'_p W_p}{2 L_p} (-V_M - V_{tp})^2$$
- Assuming  $V_{thN} = -V_{thP}$ 

$$\frac{W_p / L_p}{W_n / L_n} = \frac{k'_n}{k'_p} = \frac{\mu_n}{\mu_p}$$

### RELATIVE TRANSISTOR SIZING

- When designing static CMOS circuits, balance the driving strengths of the transistors by making the PMOS section wider than the NMOS section to
  - maximize the noise margins and
  - obtain symmetrical characteristics

### IMPACT OF UNMATCHED DRIVE STRENGTHS

 

● Skewing the  $\beta$  ratio will shift the switching threshold