

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR
OCTOBER 7, 2019
LECTURE 10: CMOS TRANSIENT BEHAVIOR

SCHEDULE THIS WEEK


- Jiwon Choe will be covering my lecture this Wednesday
 - Introduction to sequential logic
- McKenna Cisler will be holding a **Verilog tutorial** this THURSDAY from 5-7pm in the fishbowl
 - He will be swapping his usual Wednesday hours with Andrew

NMOS I-V SUMMARY

- Shockley 1st order transistor models

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_{th} & \text{cutoff} \\ \beta (V_{gs} - V_{th} - V_{ds}/2) V_{ds} & V_{gs} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_{th})^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$

 $\beta = \mu C_{ox} \frac{W}{L}$ where C_{ox} is the capacitance per unit area of SiO₂



SWITCHING THRESHOLD

- Define V_M to be the point where $V_{in} = V_{out}$ (both PMOS and NMOS in saturation since $V_{DS} = V_{GS}$)
- If $V_M = V_{DD}/2$, then this implies *symmetric rise/fall* behavior for the CMOS gate
- Recall at saturation, $I_D = (k'/2)(W/L)(V_{GS} - V_{th})^2$,


where $k'_n = \mu_n C_{ox} = \mu_n \epsilon_{ox} / t_{ox}$

- Setting $I_{Dp} = -I_{Dn}$ $\frac{k'_n W_n}{2 L_n} (V_M - V_{thn})^2 = \frac{k'_p W_p}{2 L_p} (V_M - V_{thp})^2$

- Assuming $V_{thn} = -V_{thp}$ $\frac{W_p/L_p}{W_n/L_n} = \frac{k'_n}{k'_p} = \frac{\mu_n}{\mu_p}$, if $L_p = L_n$, $W_p = W_n \cdot \frac{\mu_n}{\mu_p}$

MOS STRUCTURE RESISTANCE

 
- The simplest model assumes the transistor is a switch with an infinite "off" resistance and a finite "on" resistance R_{on}



- However R_{on} is nonlinear, time-varying, and dependent on the operation point of the transistor
- How can we determine an equivalent (constant and linear) resistance to use instead?

MOS STRUCTURE RESISTANCE

 
- Approximate R_{on} as the resistance found during linear operation
 - Simple to calculate but limited accuracy
- Instead use the average value of the resistances, R_{eq} , at the end-points of the transition (i.e., V_{DD} and $V_{DD}/2$)



$$R_{eq} \approx \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$

$$\approx \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}} + \frac{V_{DD}/2}{I_{DSAT}} \right)$$
 
$$\approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}}$$



EQUIVALENT MOS STRUCTURE RESISTANCE

$$R_{eq} = \frac{3}{4} \frac{V_{DD}}{I_{DSAT}}$$

where


$$I_{DSAT} = \frac{\mu C_{ox}}{2} \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

so,

$$R_{eq} = \frac{3}{2} \frac{L}{\mu C_{ox} W} \frac{V_{DD}}{(V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2}}$$

$$R_{eqNMOS} \propto \frac{L}{\mu_n W}, \quad R_{eqPMOS} \propto \frac{L}{\mu_p W}$$

 R_{eq} is essentially independent of V_{DD} as long as $V_{DD} \gg V_T + V_{DSAT}/2$



CMOS INVERTER: DYNAMIC BEHAVIOR

V_{DD}
 R_p
 R_n
 $V_{out} = 0$
 C_L
 $V_{in} = V_{DD}$

- Transient, or dynamic, response determines the maximum speed at which a device can be operated.

$t_{pHL} = f(R_n, C_L)$

SOURCES OF CAPACITANCE

- intrinsic MOS transistor capacitances
- extrinsic MOS transistor (fanout) capacitances
- wiring (interconnect) capacitance

SOURCES OF CAPACITANCE


- $C_L \approx C_{DB2} + C_{DB1} + C_{G4} + C_{G3}$

DELAY DEFINITIONS

input waveform
 V_{in}
 output waveform
 V_{out}
 Propagation delay
 $t_p = (t_{pHL} + t_{pLH})/2$
 signal slopes
 t_r
 t_f

INVERTER PROPAGATION DELAY

 - Propagation delay proportional to time-constant of network formed by ON resistor and the load capacitance.



$$t_{pHL} = f(R_n, C_L)$$


$$R_n = R_{eq} = \frac{3 V_{DD}}{4 I_{DSAT}}$$

$$C_L = C_{int} + C_{ext}$$

Want to have equal rise/fall delays
 → make $R_n = R_p$

MODELING PROPAGATION DELAY

 - Model circuit as first-order RC network



$$v_{out}(t) = (1 - e^{-t/\tau})V_{in}$$


where $\tau = RC$

Time to reach 50% point is
 $t = \ln(2) \tau = 0.69 \tau$


Time to reach 90% point is
 $t = \ln(9) \tau = 2.2 \tau$

$$t_p = (t_{pHL} + t_{pLH}) / 2 = 0.69 C_L (R_n + R_p) / 2$$

SWITCH DELAY MODEL

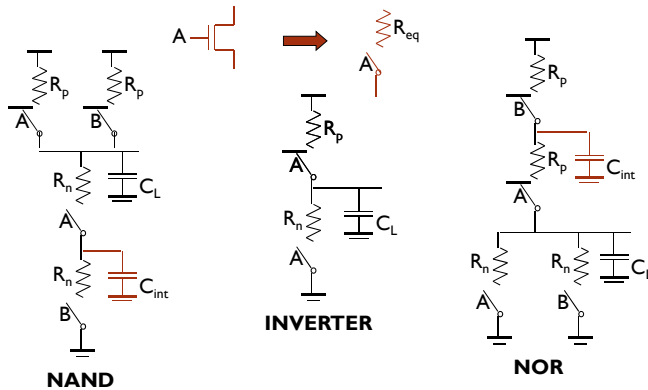

INPUT PATTERN EFFECTS ON DELAY

 

- Delay is dependent on the **pattern** of inputs
- 1st order approximation of delay:
 $t_p \approx 0.69 R_{eff} C_L$
- R_{eff} depends on the input pattern


INPUT PATTERN EFFECTS ON DELAY

- 0 → 1 transition on output: 2 possibilities
 - one input goes low: what is R_{eff} ?
 - delay is $0.69 R_p C_L$
 - both inputs go low: what is R_{eff} ?
 - delay is $0.69 R_p/2 C_L$ since 2 p-resistors on in parallel
- 1 → 0 transition on output: 1 possibility
 - both inputs go high
 - delay is $0.69 2R_n C_L$
- Adding transistors in series (without sizing) slows down the circuit

$\tau_p \approx 0.69 R_{eff} C_L$

TRANSISTOR SIZING

 - How should NMOS and PMOS devices be sized relative to an inverter with equal rise/fall times?



TRANSISTOR SIZING A COMPLEX GATE

- Size the shortest path first
- Numbers in **black** are relative to an inverter
- Numbers in **green** are relative to a minimum width device

OUT = $!(D + A \cdot (B + C))$

TRANSISTOR SIZING A COMPLEX GATE

- Alternate sizing:** size the longest path first

OUT = $!(D + A \cdot (B + C))$