


**BROWN**  
School of Engineering

## DIGITAL ELECTRONICS SYSTEM DESIGN


FALL 2019  
**PROF. IRIS BAHAR (TAUGHT BY JIWON CHOE)**  
 OCTOBER 9, 2019  
 LECTURE 11: SEQUENTIAL LOGIC

## COMBINATIONAL VS. SEQUENTIAL LOGIC

**Combinational Circuit**



**Sequential Circuit**

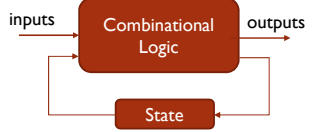



- **Combinational:**
  - Output depends only on current inputs
- **Sequential:**
  - Output depend on current inputs plus past history
  - Includes memory elements

## SEQUENTIAL CIRCUITS

- Outputs depend on inputs and state variables
- The state variables embody the past
  - Storage elements hold the state variables
- A clock periodically advances the circuit

## BISTABLE MEMORY STORAGE ELEMENT



- Fundamental building block of other state elements
- Two outputs,  $Q, \bar{Q}$
- No inputs

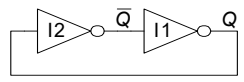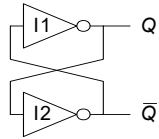- **What does the circuit do?**

  
## BISTABLE MEMORY ELEMENT

- Consider the two possible cases:
  - $Q = 0$ : then  $Q' = 1$  and  $Q = 0$  (consistent)
  - $Q = 1$ : then  $Q' = 0$  and  $Q = 1$  (consistent)
- Bistable circuit stores 1 bit of state in the state variable,  $Q$  (or  $Q'$ )
- But there are *no inputs to control the state*


 
## REVISIT NOR & NAND GATES

- Controlling inputs for NAND and NOR gates




- Implementing NOT with NAND/NOR using non-controlling inputs



 
## S-R (SET/RESET) LATCH

- Consider the four possible cases:
  - $S = 1, R = 0$
  - $S = 0, R = 1$
  - $S = 0, R = 0$
  - $S = 1, R = 1$



 
## S-R LATCH ANALYSIS

- $S = 1, R = 0$ : then  $Q = 1$  and  $\bar{Q} = 0$




 - $S = 0, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 1$



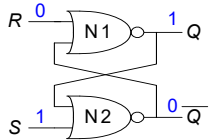
### S-R LATCH ANALYSIS

-  $S = 1, R = 0$ : then  $Q = 1$  and  $\bar{Q} = 0$



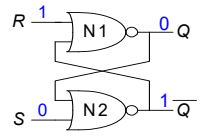
-  $S = 0, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 1$




### S-R LATCH ANALYSIS

-  $S = 0, R = 0$ : then  $Q = Q_{prev}$


$Q_{prev} = 0$

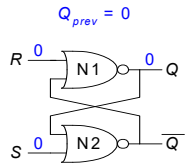

$Q_{prev} = 1$

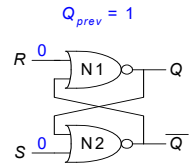


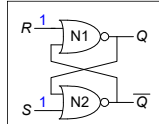-  $S = 1, R = 1$ : then  $Q = 0$  and  $\bar{Q} = 0$



### S-R LATCH AS MEMORY ELEMENT

■ Boolean expression for S-R latch:

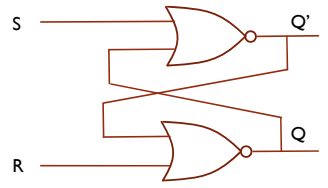

$Q' = (S + Q)'$

$Q_{next} = (R + Q)'$   
 $= (R + (S+Q)')'$   
 $= (R' \cdot (S+Q))'$   
 $= R' \cdot S + R' \cdot Q$


### S-R LATCH OPERATION

S	R	$R' \cdot S$	$R' \cdot Q$	$Q_{next}$
0	0	0	Q	Q
0	1	0	0	0
1	0	1	Q	1
1	1	0	0	0

- When  $S=0, R=0$ , latch holds its previous state
- When  $S=1, R=1$ , latch may become unstable
  - *What happens on a 11  $\rightarrow$  00 transition?*

 
## S-R LATCH SYMBOL

- SR stands for Set/Reset Latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S, R$  inputs
  - Set:** Make the output 1 ( $S = 1, R = 0, Q = 1$ )
  - Reset:** Make the output 0 ( $S = 0, R = 1, Q = 0$ )
- Must do something to avoid invalid state (when  $S = R = 1$ )**



 
## THE D LATCH

- D latch: builds on the S-R latch, where  $S$  and  $R$  cannot be both 1
  - Output "follows" input
- D latch captures input data (what to set) when certain condition holds (when to set)
- Operates in 2 modes:
  - Open (transparent): input flows through to output
  - Closed (opaque): output does not change



 
## D LATCH

- Clock enabled:  $Q$  output follows  $D$  input
- Clock disabled:  $Q$  output retains last state



## D LATCH


Clk	D	R	S	Q	Q'
1	1	0	1	1	0
1	0	1	0	0	1
0	X	0	0	$Q_{prev}$	$Q'_{prev}$

 

- Circuit guarantees  $R=S=1$  will never occur

 
## MULTI-BIT LATCH

- Simultaneously latch multiple bits
- A Latch may refer to a 1-bit latch or multi-bit latch




 
## CLOCK

- Clock:** An input to a sequential circuit that changes output and state value at a predetermined rate




- Triggering edge:** Transition of the clock (L→H or H→L) that captures input data
  - positive-edge or negative-edge
  - Clock period (cycle time): time between successive transitions in the same direction (L→H or H→L)
  - Clock frequency =  $1/\text{clock period}$

## D LATCH TIMING

  
 
## FLIP-FLOP

- Flip-flop: Samples input on triggering edge of clock
  - Rising edge → positive edge-triggered flip-flop
  - Falling edge → negative edge-triggered flip-flop
- D flip-flop: Two D latches back-to-back



## FLIP-FLOP MADE FROM D-LATCHES

D	Clk	Q
0		0
1		1
X	0	Q <sub>prev</sub>
X	1	Q <sub>prev</sub>

- Copies D to Q on the rising edge of the clock

## D FLIP-FLOP TIMING

## REGISTER

- Register: a collection of FFs operating off a common clock
- A single D flip-flop is a 1-bit register

## FLIP-FLOPS VS. LATCHES

- Why use a flip flop when it just takes twice as much logic?
- When would you want to use a flip-flop instead of a latch?