

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR
OCTOBER 16, 2019
LECTURE 12: CMOS TRANSIENT BEHAVIOR (CONTINUED)

ENGINEERING DESIGN THINKING SPEAKER YVONNE LIN


- Yvonne Lin (AB ENGN '00)
 - Founder, 4B Collective and the Femme Den
 - Thursday, Oct. 17, 12-1pm
 - B&H 190
 - Title: Design Engineering: Making Actual Stuff. Taking a product idea from inception to fruition
- Yvonne will speak about her path from Brown to the design world and what it took to get there
- How design works:** from idea to real life
- What is design engineering?** How is it different from traditional engineering
- Putting together a design portfolio** (to land a great job)



HOMEWORK PROBLEMS

- To give you practice on some of the concepts covered in class (and the labs), Jiwon has prepared a practice homework set
- You can find it on the course webpage
 - Look under *Handouts* and "Exam related materials from 2019"
- I am also including homework sets from past years prepared by Prof. Patterson.


CMOS INVERTER: DYNAMIC BEHAVIOR

 

- Transient, or dynamic, response determines the maximum speed at which a device can be operated.

$$t_{pHL} = f(R_n, C_L)$$


INPUT PATTERN EFFECTS ON DELAY

 

- Delay is dependent on the **pattern** of inputs
 - 1st order approximation of delay:
 $t_p \approx 0.69 R_{eff} C_L$
 - R_{eff} depends on the input pattern
- ➔ To get (more equal) rise/fall delays, we need to size transistors not just to compensate for differences in mobility, but also for differences in the topology.


TRANSISTOR SIZING

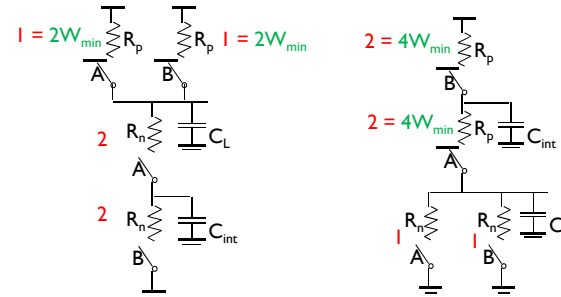- How should NMOS and PMOS devices be sized relative to an inverter with equal rise/fall times?
- Size for the worst case series path



WIRE DELAY MODELS

 
- Lumped C model
 - when only a single parasitic component (C, R, or L) is dominant the different fractions are lumped into a single circuit element



- good for short wires; pessimistic and inaccurate for long wires

WIRE DELAY MODELS, CON'T

 
- Lumped RC model
 - total resistance and capacitance are lumped into a single R, C respectively
 - good for short wires; pessimistic and inaccurate for long wires
- Distributed RC model
 - circuit parasitics are **distributed** along the length, L, of the wire
 - c and r are the capacitance and resistance per unit length



- Delay is determined using the Elmore delay equation:

$$\tau_{Di} = \sum_{k=1}^N C_k r_{ik}$$

CHAIN NETWORK ELMORE DELAY

 


- A typical wire is a chain network with (simplified) Elmore delay of

$$\tau_{DN} = \sum c_i r_{ij} = \sum c_i \sum r_j$$

- Where $\sum r_j = r_1 + r_2 + \dots + r_i$

CHAIN NETWORK ELMORE DELAY

 


$$\tau_{Di} = c_1 r_1 + c_2 (r_1 + r_2) + \dots + c_i (r_1 + r_2 + \dots + r_i)$$

Elmore delay equation $\tau_{DN} = \sum c_i r_{ii} = \sum c_i \sum r_j$

If all resistors are equal size,

$$\tau_{Di} = c_1 r_{eq} + 2c_2 r_{eq} + 3c_3 r_{eq} + \dots + ic_i r_{eq}$$

FANIN CONSIDERATIONS

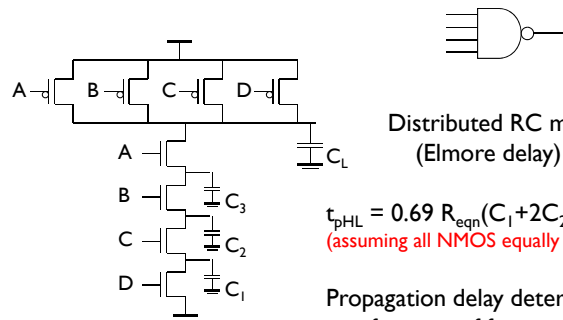


Distributed RC model (Elmore delay)

$$\tau_{pHL} = 0.69 R_{eqn} (C_1 + 2C_2 + 3C_3 + 4C_4)$$

(assuming all NMOS equally sized)

Propagation delay deteriorates rapidly as a function of fanin: **quadratically** in the worst case.

τ_p AS A FUNCTION OF FANIN


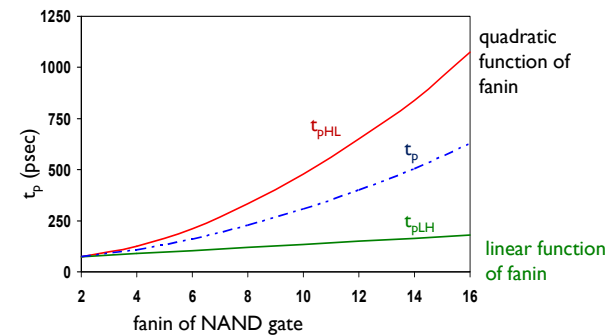


- Gates with a fan-in greater than 4 should be avoided.

SEQUENTIAL LOGIC

D LATCH


Clk	D	R	S	Q	Q'
1	1	0	1	1	0
1	0	1	0	0	1
0	X	0	0	Q _{prev}	Q' _{prev}

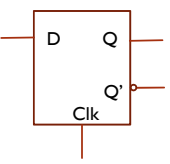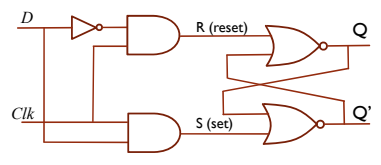
- Circuit guarantees R=S=1 will never occur

FLIP-FLOP

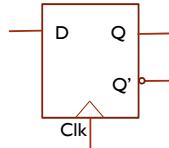- Flip-flop: Samples input on triggering edge of clock
 - Rising edge → *positive edge-triggered* flip-flop
 - Falling edge → *negative edge-triggered* flip-flop
- D flip-flop: Two D latches back-to-back





FLIP-FLOP MADE FROM D-LATCHES

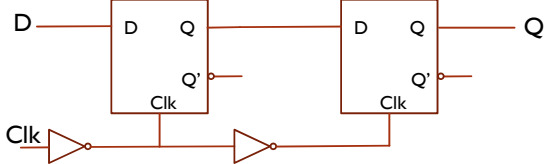


D	Clk	Q
0		0
1		1
X	0	Q _{prev}
X	1	Q _{prev}

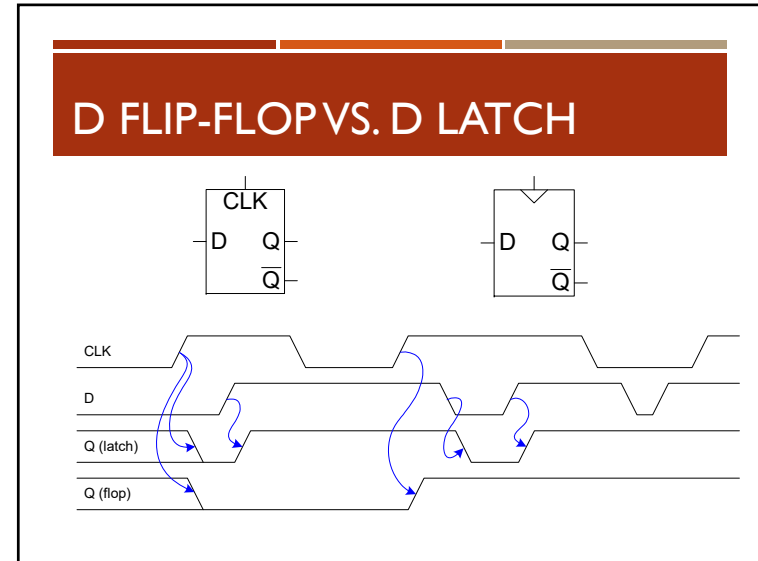 
- Copies D to Q on the *rising edge* of the clock



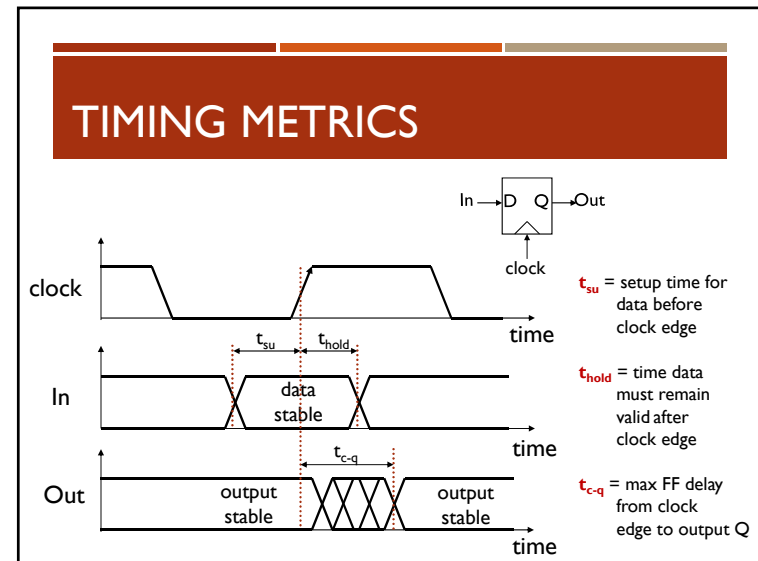
- ### FLIP-FLOPS VS. LATCHES
- Why use a flip flop when it just takes twice as much logic?
 - When would you want to use a flip-flop instead of a latch?



SYSTEM TIMING CONSTRAINTS

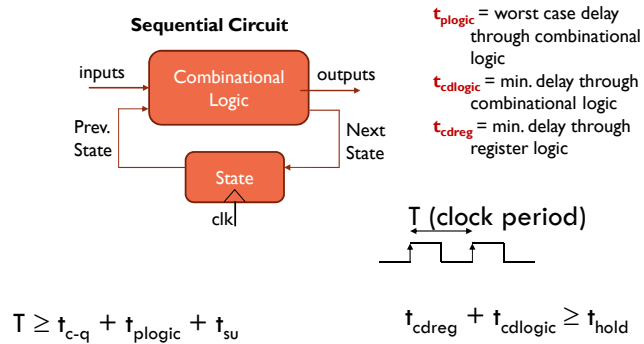



LATCH RACE PROBLEM

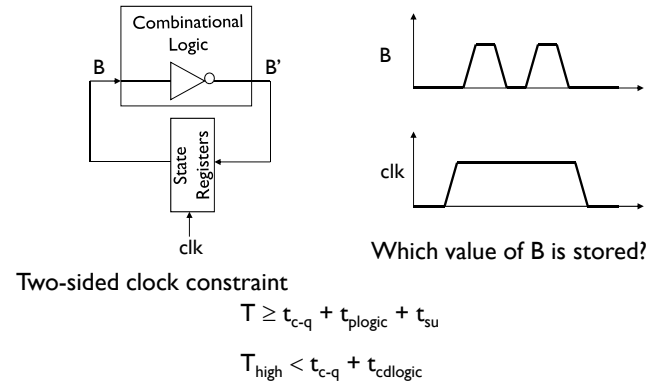

PASS TRANSISTOR LOGIC


NMOS TRANSISTORS IN SERIES/PARALLEL

  - So far we have assumed that primary inputs are only allowed to drive gate terminals of MOS transistors.
- Now assume primary inputs can drive both gate and source/drain terminals
- NMOS switch closes when the gate input is high




- Remember - NMOS transistors pass a strong 0 but a weak 1

PASS TRANSISTOR (PT) LOGIC

 


- Gate is static – a low-impedance path exists to both supply rails under all circumstances
- N transistors instead of 2N
- No static power consumption
- Bidirectional (versus non-directional)

VTC OF PASS TRANSISTOR AND GATE

 

- Pure PT logic is not regenerative: signal gradually degrades after passing through a number of PTs
- ➔ fix with static CMOS inverter insertion

NMOS ONLY PT DRIVING AN INVERTER

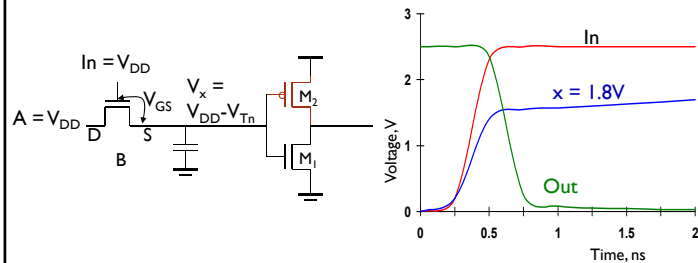

- V_x does not pull up to V_{DD} , but $V_{DD} - V_{Tn}$
- Threshold voltage drop causes static power dissipation (M_2 may be weakly conducting forming a path from V_{DD} to GND)