

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR (GIVEN BY JIWON CHOE)
NOVEMBER 4, 2019
LECTURE 16: A/D CONVERTERS AND OP AMPS

1

ANNOUNCEMENTS

- McKenna is changing his Friday lab hours to 11am-1pm


2

ENGN 1630 LABS 7, 8: ANALOG TO DIGITAL CONVERTERS

- Interface to the “real” world involves analog signals,
 - Inputs derived from sensors (temperature, flow, position, velocity, acceleration, magnetic field,....)
 - Outputs generated to control devices (motors, engines, valves, heaters, lights,.....)
- Wide range of voltage and current values and their variations in time → specialized analog circuit techniques (not the domain of this course!)
- A/D and D/A conversion: Translate between a limited voltage range contained within the $[0, V_{DD}]$ range of the digital circuit, and the set of all 2^n n -bit binary numbers (for some value of n)

3

A/D AND D/A CONVERSION

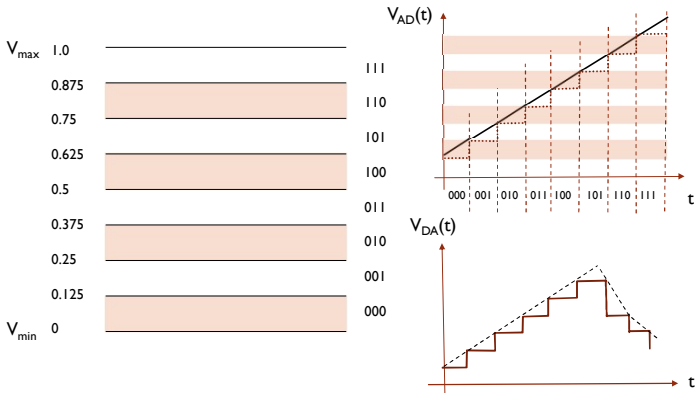

The figure illustrates the conversion between analog and digital signals. On the left, a vertical axis shows voltage levels from V_{min} (0) to V_{max} (1.0) in increments of 0.125. These levels are mapped to 3-bit binary numbers: 000 (0), 001 (0.125), 010 (0.25), 011 (0.375), 100 (0.5), 101 (0.625), 110 (0.75), and 111 (0.875). The top graph shows an analog signal $V_{AD}(t)$ as a straight line that steps up at each digital level. The bottom graph shows the digital output $V_{DA}(t)$ as a staircase function that follows the analog signal's path.

4


IDEAL OP-AMP (OPERATIONAL AMPLIFIER)

Model for a general-purpose component that solves the loading problem (among other things!)

Has a very large input resistance, small output resistance, and amplifies any difference between the voltages at the two input terminals

Power supply connections generally NOT shown on circuit schematics

 Analysis with negative feedback: assume $V_{(+)} = V_{(-)}$ and no current flow into or out of the input terminals. Output sources or sinks any current necessary to achieve these conditions.




5

5

REAL OP-AMP

 
- First attempt to model the non-ideal behavior of actual op-amps
- Incorporates a dependent voltage source and two resistors
- Enables a more detailed analysis of op-amp circuits, such as the voltage follower



6

6


OP-AMP OPEN LOOP (= COMPARATOR)

 

7

UNITY-GAIN BUFFER (VOLTAGE FOLLOWER)

 - Output voltage follows the input voltage (gain = 1)
- Very high input resistance
- Very low output resistance
- Effectively isolates the behavior of the "upstream" and "downstream" circuit functions




8

8

ANALOG INVERTER

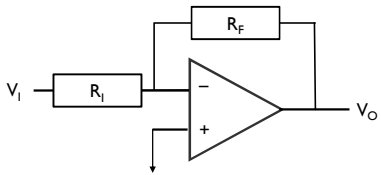- Output voltage follows the input voltage but with the opposite sign (gain = -1)



$$V_{(-)} \cong V_{(+)} = 0$$

$$\frac{V_I}{R_I} = \frac{0 - V_O}{R_F}$$


$$V_O = -\left(\frac{R_F}{R_I}\right) V_I$$

9

9

SUMMING AMPLIFIER

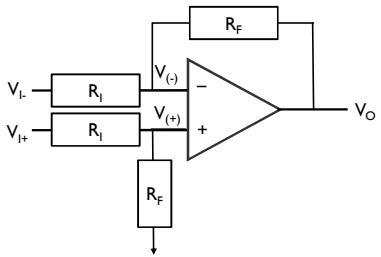- Output voltage follows the sum of two input voltages, one taken with the opposite sign



$$V_{(-)} \cong V_{(+)} = \frac{R_F}{R_I + R_F} V_{I+}$$

$$\frac{V_{I-} - V_{(-)}}{R_I} = \frac{V_{(-)} - V_O}{R_F}$$


$$V_O = ?$$

10

10

INTEGRATOR

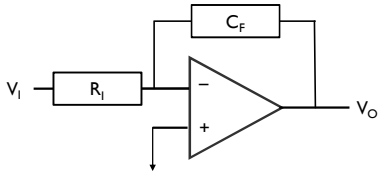- Output voltage is the time integral of the input voltage, with the opposite sign, and with a scale factor



$$V_{(-)} \cong V_{(+)} = 0$$

$$\frac{V_I}{R_I} = C_F \frac{d}{dt} (0 - V_O)$$


$$V_O = -\left(\frac{1}{R_I C_F}\right) \int V_I dt$$

11

11

COMPARATOR

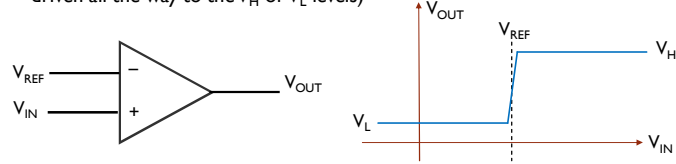- Fundamental interface between the analog and digital domains
- Component with analog inputs (arbitrary voltages) and a digital output (two defined levels, "low" and "high").
- In your kits, LM 311
- Basically a high-gain amplifier intended to be used in saturation (its output driven all the way to the V_H or V_L levels)



12

12

COMPARATOR: 1-BIT A/D CONVERTER

- Set the reference voltage at 1/2 of the analog signal range
- Operate the comparator with the same voltage supply as the digital logic
- Output is 0 for voltage below threshold, 1 for voltage above threshold

13

N-BIT PARALLEL (FLASH) A/D CONVERTER ($2^N - 1$ COMPARATORS)

3-bit flash converter example

14

FLASH CONVERTER TRADE-OFFS

- Large number of comparators plus adder network or other logic stages (chip area increasing with 2^N)
- Comparator offset voltage must be less than 1/2 the LSB interval, which becomes challenging for 1 mV level and less
- Comparator offset matching
- Resolution up to 10 bits
- Highest speed (one clock cycle)

15

SAMPLING

Voltage or current signals, which are continuous functions of time, have to be sampled in order to be represented digitally.

Sampling introduces ambiguity: what happens in between sample points?

If the maximum frequency present in the signal is f , the sample rate F_s must be greater than $2f$.

All frequencies greater than $F_s/2$ appear aliased in the interval $[0, F_s/2]$. To get rid of the confusion, signals must be band-limited (by low-pass filtering) to less than $F_s/2$ before the sampling operation.

16

SAMPLE AND HOLD (S/H)

- Clock signal C determines sampling instants
- Capacitor stores the sampled voltage between C pulses
- Unity-gain amplifiers buffer the sampling capacitor from input and output circuits
- Input side (or prior circuits) must band-limit the signal to less than half the sampling frequency
- Output presents a piece-wise constant signal to the A/D converter

https://en.wikipedia.org/wiki/Sample_and_hold

17

SUB-RANGING A/D CONVERTER

- One of many techniques for trading off conversion time and circuit cost
- 2 lower resolution flash A/D converters operating at half the rate
- D/A converter requires 8-bit accuracy in this example

*phi_N = CLOCK PHASE

<https://www.maximintegrated.com/en/app-notes/index.mvp/id/810>

18

SUCCESSIVE APPROXIMATION A/D CONVERTER

SAR = 1000
 If ANALOG less than DIGITAL, SAR = 0100
 else SAR = 1100
 If ANALOG less than DIGITAL, SAR = X010
 else SAR = X110
 etc.

Successive approximation register (SAR)

19

DUAL-SLOPE A/D CONVERTER

20