


BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR (GIVEN BY JIWON CHOE)
 NOVEMBER 6, 2019
 LECTURE 17: BINARY ADDITION

SUMMING AMPLIFIER

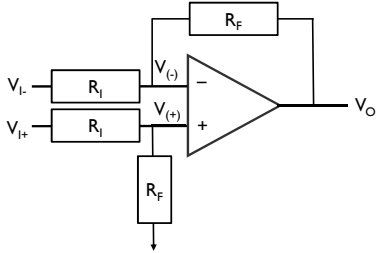- Output voltage follows the sum of two input voltages, one taken with the opposite sign



$$V_{(-)} \cong V_{(+)} = \frac{R_F}{R_I + R_F} V_{I+}$$


$$\frac{V_{I-} - V_{(-)}}{R_I} = \frac{V_{(-)} - V_O}{R_F}$$

$$V_O = ?$$

2

INTEGRATOR

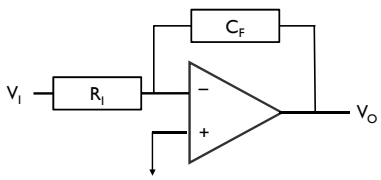- Output voltage is the time integral of the input voltage, with the opposite sign, and with a scale factor




$$V_{(-)} \cong V_{(+)} = 0$$

$$\frac{V_I}{R_I} = C_F \frac{d}{dt} (0 - V_O)$$

$$V_O = -\left(\frac{1}{R_I C_F}\right) \int V_I dt$$

3

DUAL-SLOPE A/D CONVERTER

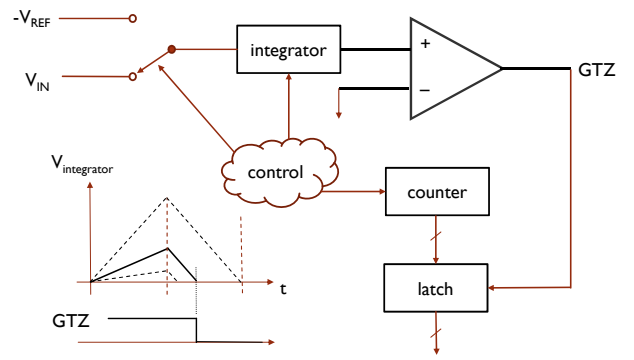


$-V_{REF}$

V_{IN}

$V_{integrator}$

GTZ

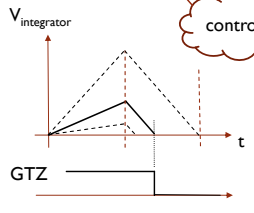


integrator

control


counter

latch


R-2R LADDER D/A CONVERTER

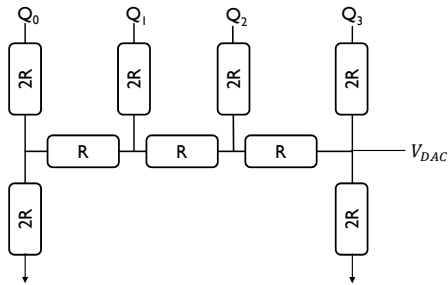


R-2R LADDER D/A CONVERTER

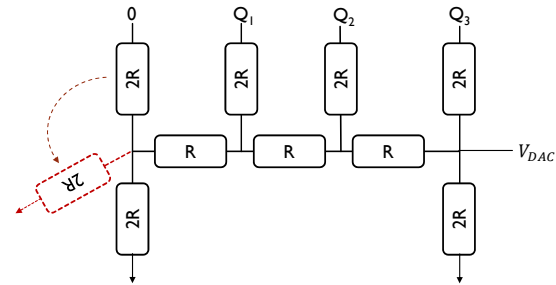

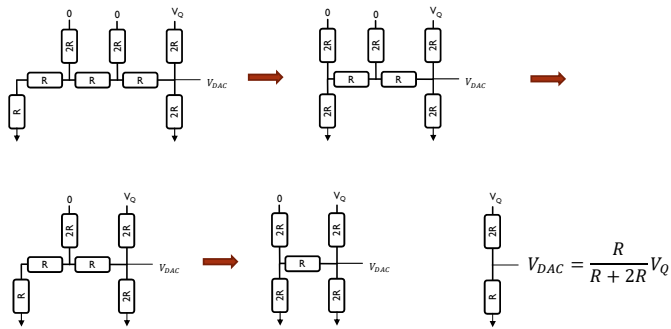R-2R LADDER ANALYSIS BY SUPERPOSITION AND SERIES PARALLEL REDUCTION



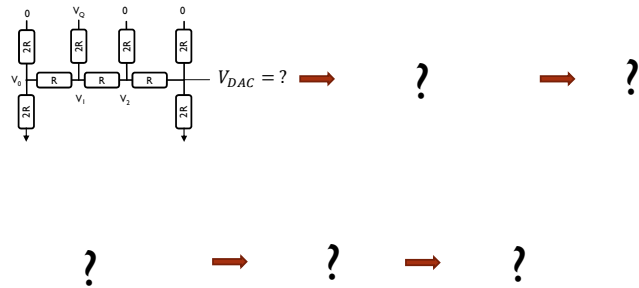R-2R LADDER ANALYSIS BY SUPERPOSITION AND SERIES PARALLEL REDUCTION



BINARY ADDITION

UNSIGNED BINARY NUMBERS

- For the binary number $b_{n-1}b_{n-2}\dots b_1b_0.b_{-1}b_{-2}\dots b_{-m}$ the decimal number is:

Example: $D = \sum_{i=-m}^{n-1} b_i 2^i$
 $101.001_2 = ?$

$5 + 2^{-3} = 5.125$

BINARY ADDITION

- Addition is an essential operation for all kinds of computing
- We need to understand how to do this for binary numbers
- We need to understand how to do this for positive and negative numbers
- We need to understand how to implement this efficiently in hardware


$$\begin{array}{r} 5 \\ + 7 \\ \hline 12 \end{array}$$

Carry Sum

$$\begin{array}{r} 1\ 1\ 1 \leftarrow \text{Carry bits} \\ + 1\ 1\ 1 \\ \hline 1\ 1\ 0\ 0 \end{array}$$

Carryout Sums

HALF ADDER

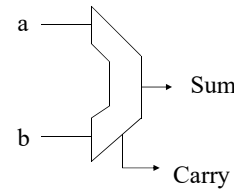

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

FULL ADDER

Id	a	b	c_{in}	carry	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

▪ How do you express sum and carry as Boolean functions?

THE FULL ADDER

BUILDING A BINARY ADDER

				← Carry bits
	1	1	1	
	1	0	1	5 (A)
+	1	1	1	7 (B)
	1	1	0	12 (S)
	1	1	0	

↑ Carryout
↑ Sums

- Inputs & outputs for the i^{th} bit position
 - Inputs: A_i , B_i , and C_i (carry-in)
 - Outputs: S_i (sum) and C_{i+1} (carry out)
- Carry out of a bit position is the carry in for the next bit position

THE RIPPLE CARRY ADDER

- The carry out of one stage ripples to the carry in of the next

WHAT ABOUT NEGATIVE NUMBERS?

- So far we have just considered unsigned numbers when converting from base 10 to binary.
- What about negative numbers and how do we add two signed numbers in binary?
- 3 ways of representing signed numbers:
 - Signed magnitude
 - 1's complement
 - 2's complement

SIGNED MAGNITUDE

- The Most Significant Bit (MSB) is the sign bit: 0 → positive, 1 → negative
- The rest of the bits define the magnitude
- Need to know how many bits are available to represent a number!
- Example: $(2)_{10} = (0010)_2 = (0\ 010)_{S\&M}$
 $(-2)_{10} = (1010)_2 = (1\ 010)_{S\&M}$
- Makes adding and subtracting a pain
 - Can't just add them regularly
- Also, two representations for zero (+0 and -0)

SIGNED MAGNITUDE ADDITION

$$\begin{array}{r}
 (1)_{10} \rightarrow 0001 \\
 + (5)_{10} \rightarrow +0101 \\
 \hline
 (6)_{10} \quad 0110 \quad \text{(both positive, so a positive result)} \\
 \\
 (-2)_{10} \rightarrow 1010 \\
 + (-4)_{10} \rightarrow +1100 \\
 \hline
 (-6)_{10} \quad 1110 \quad \text{(both negative, so keep the negative sign)} \\
 \\
 (4)_{10} \rightarrow 0100 \quad \text{(larger number - smaller number)} \\
 + (-3)_{10} \rightarrow +1011 \quad \text{(keep the sign of the larger number)} \\
 \hline
 (1)_{10} \quad 0001 \quad \text{(signs are different } \rightarrow \text{ subtract smaller from larger number, keep sign of larger number)}
 \end{array}$$

- Need a comparator to supplement adder/subtractor

1'S COMPLEMENT

- To negate a number, complement (invert, flip) each bit
- Example: $(4)_{10} = (0100)_2 = (0100)_{1's\ comp}$
 $(-4)_{10} = (1011)_{1's\ comp}$
- Like sign and magnitude, the high bit indicates the sign of the number
- What about adding and subtracting?

1'S COMPLEMENT ADD/SUBTRACT

$$\begin{array}{r}
 \begin{array}{l}
 (-2)_{10} \rightarrow 1101 \\
 + (-4)_{10} \rightarrow + 1011 \\
 \hline
 (-6)_{10}
 \end{array}
 \qquad
 \begin{array}{l}
 11000 \\
 + 1 \\
 \hline
 1001
 \end{array}
 \begin{array}{l}
 \text{-- not right, } (-6)_{10} = (1001)_{1\text{'s comp}} \\
 \rightarrow \text{add } C_{\text{out}} \text{ back to LSB} \\
 \text{-- now it works}
 \end{array}
 \end{array}$$

$$\begin{array}{r}
 \begin{array}{l}
 (4)_{10} \rightarrow 0100 \\
 + (-3)_{10} \rightarrow + 1100 \\
 \hline
 (1)_{10}
 \end{array}
 \qquad
 \begin{array}{l}
 10000 \\
 + 1 \\
 \hline
 0001
 \end{array}
 \begin{array}{l}
 \text{-- not right, add } C_{\text{out}} \text{ back to LSB} \\
 \text{-- now it works}
 \end{array}
 \end{array}$$

- Better than sign and magnitude (can subtract by adding the negative)
- But requires 2 addition operations (need to conditionally add C_{out})