

**DIGITAL ELECTRONICS
SYSTEM DESIGN**

FALL 2019
PROF. IRIS BAHAR
NOVEMBER 11, 2019
LECTURE 18: ADDING SIGNED NUMBERS & MINIMIZING
DELAY

SEMINAR SPEAKER THIS TUESDAY

Hannah Chung
Co-founder & Head of Design of Sproutel
Tuesday, November 12
B&H 190, 12-1pm




From Mechanical Engineering to Designer --- The Sproutel Story

Hannah will share her story of finding her voice as a designer and engineer as she pursues her passion for designing for good in healthcare

UPDATES TO LAB HOURS THIS WEEK

- Monica has to cancel her lab hours Tuesday 1-4pm. She will schedule makeup hours later this week. Stay tuned.


HALF ADDER

 

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

FULL ADDER

 


Truth Table

Id	a	b	c_{in}	carry	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1


- How do you express sum and carry as Boolean functions?

BUILDING A BINARY ADDER

 

- Inputs & outputs for the i^{th} bit position
 - Inputs: A_i , B_i , and C_i (carry-in)
 - Outputs: S_i (sum) and C_{i+1} (carry out)
- Carry out of a bit position is the carry in for the next bit position

THE RIPPLE CARRY ADDER

 

- The carry out of one stage ripples to the carry in of the next

WHAT ABOUT NEGATIVE NUMBERS?

- So far we have just considered unsigned numbers when converting from base 10 to binary.
- What about negative numbers and how do we add two signed numbers in binary?
- 3 ways of representing signed numbers:
 - Signed magnitude
 - 1's complement
 - 2's complement

SIGNED MAGNITUDE

- The Most Significant Bit (MSB) is the **sign bit**: 0 → positive, 1 → negative
- The rest of the bits define the **magnitude**
- Need to *know how many bits are available* to represent a number!
- Example: $(2)_{10} = (0010)_2 = (0\ 010)_{S\&M}$
 $(-2)_{10} = (1\ 010)_{S\&M}$
- Makes adding and subtracting a pain
 - Can't just add them regularly
- Also, two representations for zero (+0 and -0)

SIGNED MAGNITUDE ADDITION

$$\begin{array}{r}
 (1)_{10} \rightarrow 0001 \\
 + (5)_{10} \rightarrow +0101 \\
 \hline
 (6)_{10} \quad 0110 \text{ (both positive, so a positive result)} \\
 \\
 (-2)_{10} \rightarrow 1010 \\
 + (-4)_{10} \rightarrow +1100 \\
 \hline
 (-6)_{10} \quad 1110 \text{ (both negative, so keep the negative sign)} \\
 \\
 (4)_{10} \rightarrow 0100 \text{ (larger number - smaller number)} \\
 + (-3)_{10} \rightarrow +1011 \text{ (keep the sign of the larger number)} \\
 \hline
 (1)_{10} \quad 0001 \text{ (signs are different } \rightarrow \text{ subtract smaller from larger number, keep sign of larger number)}
 \end{array}$$

- Need a comparator to supplement adder/subtractor

1'S COMPLEMENT


- To negate a number, complement (invert, flip) each bit
- Example: $(4)_{10} = (0100)_2 = (0100)_{1's\ comp}$
 $(-4)_{10} = (1011)_{1's\ comp}$
- Like sign and magnitude, the high bit indicates the sign of the number
- What about adding and subtracting?

1'S COMPLEMENT ADD/SUBTRACT

$$\begin{array}{r}
 (-2)_{10} \rightarrow 1101 \\
 + (-4)_{10} \rightarrow +1011 \\
 \hline
 (-6)_{10} \quad 11000 \text{ -- not right, } (-6)_{10} = (1001)_{1's\ comp} \\
 \quad \quad \quad + 1 \rightarrow \text{add } C_{out} \text{ back to LSB} \\
 \quad \quad \quad \hline
 \quad \quad \quad 1001 \text{ -- now it works} \\
 \\
 (4)_{10} \rightarrow 0100 \\
 + (-3)_{10} \rightarrow +1100 \\
 \hline
 (1)_{10} \quad 10000 \text{ -- not right, add } C_{out} \text{ back to LSB} \\
 \quad \quad \quad + 1 \\
 \quad \quad \quad \hline
 \quad \quad \quad 0001 \text{ -- now it works}
 \end{array}$$

- Better than sign and magnitude (can subtract by adding the negative)
- But requires 2 addition operations (need to conditionally add C_{out})

ANOTHER ENCODING FOR BINARY

 

2'S COMPLEMENT REPRESENTATION

- MSB has weight -2^{n-1}
- Range of an n-bit number is -2^{n-1} through $2^{n-1}-1$
 - Smallest negative number (-2^{n-1}) has no positive counterpart

-2^2	-2^1	-2^0	
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	-4
1	0	1	-3
1	1	0	-2
1	1	1	-1

2'S COMPLEMENT

- To negate in 2's complement, complement (flip) each bit and then add 1
- Example: Represent $(-5)_{10}$ in 2's complement using 4 bits

$$\begin{array}{r} (5)_{10} = (0101)_{2's\ comp} \quad 1010 \\ + \quad 1 \\ \hline 1011 \end{array} \rightarrow (-5)_{10} = (1011)_{2's\ comp}$$
- Like sign and magnitude, the MSB indicates the sign of the number
- Sign extension: Pad the high bits with the value of the MSB

Example: $(-6)_{10} = (1010)_2 = (111010)_2$
- Range: for n bits: $[-2^{n-1}, (2^{n-1}-1)] \rightarrow 1$ more neg. than pos. number

2'S COMPLEMENT ADDITION

- Add numbers as you would for unsigned addition
- Examples with 4 bits:

$$\begin{array}{r} 4 \rightarrow 0100 \\ - 4 \rightarrow + 1100 \quad (\text{subtract by negating } 2^{nd} \text{ number \& adding}) \\ \hline 0 \rightarrow +0000 \quad (\text{ignore carry out since signs were different}) \end{array}$$

$$\begin{array}{r} 5 \rightarrow 0101 \\ + 6 \rightarrow + 0110 \\ \hline 11 \quad 1011 \quad \text{-- overflow (two positives, got a negative)} \end{array}$$
- 2's complement has one representation for 0 and arithmetic is easier
- It's the most commonly used negative number representation

SIGNED BINARY NUMBERS

Table 1.3
Signed Binary Numbers

Decimal	Signed-2's Complement	Signed-1's Complement	Signed Magnitude
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0001	0001	0001
+0	0000	0000	0000
-0	—	1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
-8	1000	—	—

Copyright © 2012 Pearson Education, publishing as Prentice Hall

GRAY CODES

- Represent decimal numbers 0-8 in binary such that only bit changes value as you count up/down
- Why would such an encoding be advantageous?

Decimal	Gray code
0	0000
1	0001
2	0011
3	0010
4	0110
5	0111
6	0101
7	0100
8	1100
9	1101

2'S COMPLEMENT SUBTRACTION


- Negate second operand and add:

$$\begin{array}{r} 01101000 \quad (104) \\ - 00010001 \quad (17) \\ \hline \end{array}$$

$$\begin{array}{r} 01101000 \quad (104) \\ - 11101111 \quad (-17) \\ \hline 01010111 \quad (87) \end{array}$$


A 64-BIT ADDER/SUBTRACTOR

 - Ripple Carry Adder (RCA) built out of 64 Full Adders
- Subtraction – complement all subtrahend bits (xor gates) and set low order carry-in
- RCA
 - Simple logic, so low (area) cost
 - Slow: $O(N)$ for N bits and lots of glitching



INVERTER PROPAGATION DELAY

 - Propagation delay is proportional to the time-constant of the network formed by the pull-down resistor and the load capacitance.



$$t_{pHL} = f(R_n, C_L)$$


$$R_n = R_{eq} = \frac{3 V_{DD}}{4 I_{DSAT}}$$

$$C_L = C_{int} + C_{ext} + C_{wire}$$

Want to have equal rise/fall delays
 → Make $R_n = R_p$

MODELING PROPAGATION DELAY

 - Model circuit as first-order RC network



$$v_{out}(t) = (1 - e^{-t/\tau})V_{in}$$

$$\text{where } \tau = RC$$

$$\text{Time to reach 50\% point is } t = \ln(2) \tau = 0.69 \tau$$

$$\text{Time to reach 90\% point is } t = \ln(9) \tau = 2.2 \tau$$


$$t_p = (t_{pHL} + t_{pLH}) / 2 = 0.69 C_L (R_n + R_p) / 2$$

HOW CAN WE IMPROVE PERFORMANCE?

- Reduce R_n, R_p
 - Increase W/L ratio of the transistor
 - most powerful and effective performance optimization tool for designer
 - But what happens to the intrinsic capacitance with larger W/L?
- Reduce C_L
 - Keep drain diffusions small
 - Limit interconnect capacitance
 - Limit fanout
- Increase V_{DD}
 - Trade off energy for performance
 - Increase V_{DD} above a certain level yields minimal improvements
 - Reliability concerns enforce an upper bound on V_{DD}

NMOS/PMOS RATIO

- So far we have sized the PMOS and NMOS so that the R_{eq} values match (i.e., $\beta = (W/L_p)/(W/L_n) = W_p/W_n = 2$ to 2.8)
 - Symmetric VTC
 - Equal high-to-low and low-to-high propagation delays
- If speed is the only concern, **reduce** the width of the PMOS device!
 - Widening the PMOS degrades the t_{pHL} due to larger intrinsic capacitance
- What does this imply if we want to minimize delay for an inverter?

 

NMOS/PMOS RATIO

- We define propagation delay as:

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69 C_L \left(\frac{R_{eqn} + R_{eqp} / \beta}{2} \right)$$

- And define

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_W$$

$$C_L \approx (1 + \beta)(C_{dn1} + C_{gn2}) + C_W$$

- So we have

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_W)(R_{eqn} + R_{eqp} / \beta)$$

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_W)R_{eqn} \left(1 + \frac{r}{\beta} \right), \quad \text{where } r = \frac{R_{eqp}}{R_{eqn}}$$

- Now, optimize t_p with respect to β ...

NMOS/PMOS RATIO

- Given the equation for t_p :

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_W)R_{eqn} \left(1 + \frac{r}{\beta} \right)$$

- Minimize t_p as a function of β ...


- Compute the optimal value of β by setting $\partial t_p / \partial \beta = 0$

$$\beta_{opt} = \sqrt{r \left(1 + \frac{C_W}{C_{dn1} + C_{gn2}} \right)}$$

Where $r = R_{eqp} / R_{eqn}$ = resistance ratio for identically sized PMOS, NMOS

$$\beta_{opt} = \sqrt{r} \quad \text{when } C_W \text{ is negligible}$$

PMOS/NMOS RATIO EFFECTS

 

$$\beta = (W/L_p)/(W/L_n)$$

β of 2.4 gives symmetrical response

β of 1.6 to 1.9 gives optimal performance

DEVICE SIZING FOR PERFORMANCE

- Divide capacitive load, C_L , into

- C_{int} : intrinsic \rightarrow diffusion

- C_{ext} : extrinsic \rightarrow fanout (gate-channel cap and wiring)

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$

- $t_{p0} = 0.69 R_{eq} C_{int}$ is the intrinsic (unloaded) delay of the gate

- Widening both PMOS and NMOS by a factor S reduces R_{eq} by an identical factor ($R_{eq} = R_{ref}/S$), but raises the intrinsic capacitance by the same factor ($C_{int} = S C_{iref}$)

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(S C_{iref})) = t_{p0} (1 + C_{ext}/(S C_{iref}))$$

DEVICE SIZING FOR PERFORMANCE

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0}(1 + C_{ext}/(SC_{iref}))$$

What can we conclude from this?

- t_{p0} is independent of the sizing of the gate; *with no load the drive of the gate is totally offset by the increased capacitance*
- Any S sufficiently larger than (C_{ext}/C_{int}) yields the best performance gains with least area impact

SIZING IMPACTS ON DELAY

