


BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR
NOVEMBER 13, 2019
LECTURE 19: FANOUT SIZING

NMOS/PMOS RATIO

- So far we have sized the PMOS and NMOS so that the R_{eq} values match (i.e., $\beta = (W/L_p)/(W/L_n) = W_p/W_n = 2$ to 2.8)
 - Symmetric VTC
 - Equal high-to-low and low-to-high propagation delays
- If speed is the only concern, **reduce** the width of the PMOS device!
 - Widening the PMOS degrades the t_{pHL} due to larger intrinsic capacitance
- What does this imply if we want to minimize delay for an inverter?

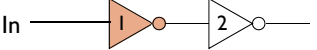

NMOS/PMOS RATIO

- We define propagation delay as:

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 0.69C_L \left(\frac{R_{eqn} + R_{eqp} / \beta}{2} \right)$$
- And define

$$C_L = (C_{dp1} + C_{dn1}) + (C_{gp2} + C_{gn2}) + C_w$$

$$C_L \approx (1 + \beta)(C_{dn1} + C_{gn2}) + C_w$$
- So we have

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_w)(R_{eqn} + R_{eqp} / \beta)$$

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_w)R_{eqn} \left(1 + \frac{r}{\beta} \right), \quad \text{where } r = \frac{R_{eqp}}{R_{eqn}}$$
- Now, optimize t_p with respect to β ...

NMOS/PMOS RATIO

- Given the equation for t_p :

$$t_p = 0.345((1 + \beta)(C_{dn1} + C_{gn2}) + C_w)R_{eqn} \left(1 + \frac{r}{\beta} \right)$$
- Minimize t_p as a function of β ...
- Compute the optimal value of β by setting $\partial t_p / \partial \beta = 0$

$$\beta_{opt} = \sqrt{r \left(1 + \frac{C_w}{C_{dn1} + C_{gn2}} \right)}$$

Where $r = R_{eqp}/R_{eqn}$ = resistance ratio for identically sized PMOS, NMOS

$$\beta_{opt} = \sqrt{r} \quad \text{when } C_w \text{ is negligible}$$

PMOS/NMOS RATIO EFFECTS

$\beta = (W/L_p)/(W/L_n)$

β of 2.4 gives symmetrical response

β of 1.6 to 1.9 gives optimal performance

DEVICE SIZING FOR PERFORMANCE

- Divide capacitive load, C_L , into
 - C_{int} : intrinsic \rightarrow diffusion
 - C_{ext} : extrinsic \rightarrow fanout (gate-channel cap and wiring)

$$t_p = 0.69 R_{eq} C_{int} (1 + C_{ext}/C_{int}) = t_{p0} (1 + C_{ext}/C_{int})$$

- $t_{p0} = 0.69 R_{eq} C_{int}$ is the intrinsic (unloaded) delay of the gate
- Widening both PMOS and NMOS by a factor S reduces R_{eq} by an identical factor ($R_{eq} = R_{ref}/S$), but raises the intrinsic capacitance by the same factor ($C_{int} = SC_{iref}$)

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0}(1 + C_{ext}/(SC_{iref}))$$

DEVICE SIZING FOR PERFORMANCE

$$t_p = 0.69 R_{ref} C_{iref} (1 + C_{ext}/(SC_{iref})) = t_{p0}(1 + C_{ext}/(SC_{iref}))$$

What can we conclude from this?

- t_{p0} is independent of the sizing of the gate; with no load the drive of the gate is totally offset by the increased capacitance
- Any S sufficiently larger than (C_{ext}/C_{int}) yields the best performance gains with least area impact

IMPACT OF FANOUT ON DELAY

$$t_p = t_{p0} (1 + C_{ext}/C_{int})$$

- Extrinsic capacitance, C_{ext} , is a function of the gates being driven by the gate under question (i.e. the fanout)
 - larger fanout \rightarrow larger external load.
- Re-express the intrinsic capacitance (C_{int}) in terms of input gate capacitance:


$$C_{int} = \gamma C_g, \quad \text{where } \gamma \approx 1$$

$$t_p = t_{p0} (1 + C_{ext}/\gamma C_g) = t_{p0} (1 + f/\gamma)$$

$$f = C_{ext}/C_g \text{ is the effective fanout}$$

INVERTER CHAIN

 - Goal is to minimize the delay through an inverter chain



- The delay of the j^{th} inverter stage is

$$t_{p,j} = t_{p0} (1 + C_{g,j+1}/(\gamma C_{g,j})) = t_{p0} (1 + f_j / \gamma)$$

$$\text{and } t_p = t_{p,1} + t_{p,2} + \dots + t_{p,N}$$

$$\text{so } t_p = \sum t_{p,j} = t_{p0} \sum (1 + C_{g,j+1}/(\gamma C_{g,j}))$$

- If C_L and $C_{g,1}$ are given, we have 2 different optimizations
 - How should the inverters be sized to minimize delay?
 - What is the optimal number of inverters to minimize the delay?

SIZING THE INVERTERS IN THE CHAIN

- After a bit of calculus, we find that for minimum delay:

$$C_{g,j+1}/C_{g,j} = C_{g,j}/C_{g,j-1} \text{ for } j=2 \dots N$$

- What does this imply?

- All gates have the same effective fanout, f
- Each gate should be scaled up by the same factor w.r.t. its preceding gate

- What is the effective fanout for a gate given C_L and $C_{g,1}$?

- With a bit of algebra and inductive reasoning we find that:


$$f = \sqrt[N]{C_L / C_{g,1}} = \sqrt[N]{F}$$

- $F = C_L / C_{g,1}$ is the overall effective fanout

- What is the minimum delay through the chain?

$$t_p = N t_{p0} (1 + \sqrt[N]{F} / \gamma)$$

EXAMPLE: INVERTER CHAIN SIZING

 

- $C_L / C_{g,1}$ has to be evenly distributed over $N = 3$ inverters

$$F = C_L / C_{g,1} = 8 / 1$$

$$f = \sqrt[3]{8} = 2$$

- Assuming L remains unchanged for all inverters, f is obtained by adjusting W relative to the previous stage (i.e., scale up by factor of 2 relative to the previous gate).

OPTIMAL NUMBER OF INVERTERS

- What is the optimal value for N given F ? (where $F = f^N$)

- if the number of stages is too large, the intrinsic delay of the stages dominates
- if the number of stages is too small, the effective fan-out of each stage dominates


$$t_p = N t_{p0} (1 + \sqrt[N]{F} / \gamma)$$

$$\partial t_p / \partial N = \gamma + \sqrt[N]{F} - \frac{\sqrt[N]{F} \ln F}{N} = 0$$

$$\rightarrow f = e^{(1+\gamma/f)}$$


- For $\gamma = 0$ (ignoring self-loading) $N = \ln(F)$ and the effective-fan out (tapering factor) becomes $f = e = 2.718$
- For $\gamma = 1$ (the typical case) the optimum effective fan-out can be solved numerically and turns out to be close to 3.6

OPTIMUM EFFECTIVE FANOUT

 

- Too many stages has a substantial negative impact on delay
 - Choosing f slightly larger than optimum has little effect on delay and reduces the number of stages (and area).
 - Common practice to use $f = 4$ (for $\gamma = 1$)
- ➔ Fanout of 4 (FO4) rule of thumb delay metric is based on this result

FULL ADDER

 


Truth Table


Id	a	b	c_{in}	carry	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

- How do you express sum and carry as Boolean functions?

THE FULL ADDER

 


BUILDING A BINARY ADDER

 

- Inputs & outputs for the i^{th} bit position
 - Inputs: A_i , B_i , and C_i (carry-in)
 - Outputs: S_i (sum) and C_{i+1} (carry out)
- Carry out of a bit position is the carry in for the next bit position

THE RIPPLE CARRY ADDER

 

- The carry out of one stage ripples to the carry in of the next

2'S COMPLEMENT SUBTRACTION


- Negate second operand and add:

$$\begin{array}{r} 01101000 \quad (104) \\ - 00010001 \quad (17) \\ \hline \end{array}$$


$$\begin{array}{r} 01101000 \quad (104) \\ - 11101111 \quad (-17) \\ \hline 01010111 \quad (87) \end{array}$$

A 64-BIT ADDER/SUBTRACTOR

 - Ripple Carry Adder (RCA) built out of 64 Full Adders
- Subtraction – complement all subtrahend bits (xor gates) and set low order carry-in
- RCA
 - Simple logic, so low (area) cost
 - Slow: $O(N)$ for N bits and lots of glitching



GLITCHING IN A RIPPLE CARRY ADDER

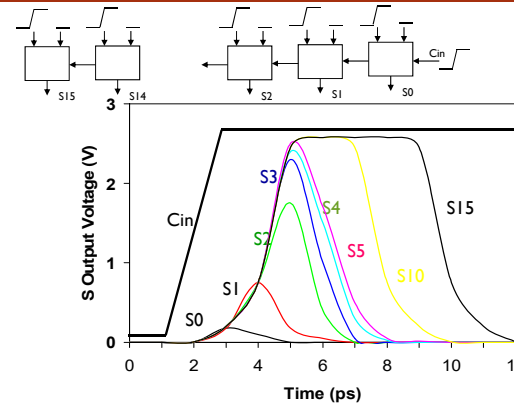

FAST CARRY CHAIN DESIGN

- The key to fast addition is a low latency carry network
- What matters is whether in a given position a carry is
 - generated $G_i = A_i \& B_i = A_i B_i$
 - propagated $P_i = A_i \oplus B_i$
 - annihilated (killed) $K_i = !A_i \& !B_i$
- Giving a carry recurrence of

$$C_{i+1} = G_i + P_i C_i$$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$


$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$


CARRY OUT LOGIC FOR 4-BIT ADDER

- P_i s and G_i s are computed at time 0
- $$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$
 
$$= \underbrace{G_3 + P_3(G_2 + P_2(G_1 + P_1 G_0))}_{G_{3:0} : \text{carry generation from bits 3-0}} + \underbrace{(P_3 P_2 P_1 P_0)}_{P_{3:0} : \text{carry propagation from bits 3-0}} C_0$$



 32-BIT CARRY LOOKAHEAD ADDER WITH 4-BIT RIPPLE CARRY ADDERS



- Carry out logic gets more complicated beyond 4 bits
- CLAs are often implemented as 4-bit modules and instantiated in a hierarchical way to realize wider adders