

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN


FALL 2019
PROF. IRIS BAHAR
NOVEMBER 25, 2019
LECTURE 22: MEMORY DESIGN

LAB HOURS THIS WEEK

- Eren will not be holding lab hours this Tuesday evening.
- Monica still has hours on Wednesday from 11am-1pm (unless no one is planning to show up...)

MEMORY DEFINITIONS

 - Size (Kbytes, Mbytes, Gbytes, Tbytes)
- Timing parameters
 - Read Access – delay between read request and the data available
 - Write Access – delay between write request and writing data to memory
 - (Read or Write) Cycle – min. time required between read/writes



MEMORY DEFINITIONS


- Function – functionality, nature of the storage mechanism
 - static and dynamic; volatile and nonvolatile
- Access pattern – random, serial, content addressable
- Input-output architecture – number of data input and output ports (multi-ported memories)
- Application – embedded, secondary, tertiary

MEMORY DEFINITIONS

| RWM | | NVRWM | ROM |
|-----------------------------|-----------------------|--------|--------------------------------|
| Random Access | Non-Random Access | EPROM | Mask-programmed |
| SRAM (cache, register file) | FIFO, LIFO | EEPROM | Electrically-programmed (PROM) |
| DRAM (main memory) | Shift Register CAM | FLASH | |

- Read-Only Memories (ROM)**
 - Truly read-only
 - Written in the factory, and never written after installation
 - Mostly read and rarely written
 - Much faster to read than write
 - Non-volatile, e.g., flash memory
- Random Access Memory (RAM)**
 - Read and write any location at similar speeds
 - Volatile: loses contents when powered off
 - SRAM, DRAM


EXAMPLE ROM IMPLEMENTATION

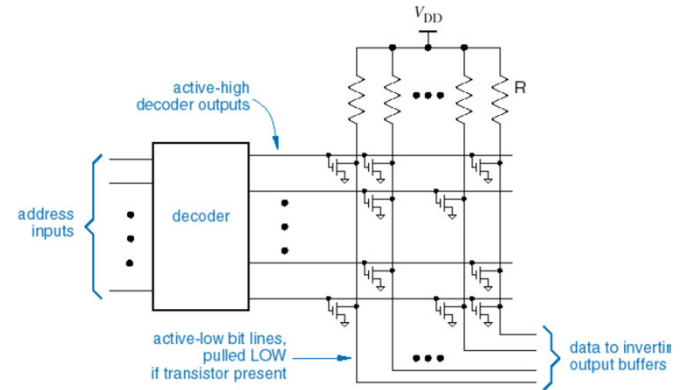

APPLICATIONS OF ROM

- Program storage**
 - e.g., Boot code for personal computers, application storage for embedded systems
- Data storage**
 - e.g., Configuration information, music players
- Combinational logic functions**
 - Lookup tables
 - Address inputs = function inputs
 - Data outputs = function outputs

USING ROMS FOR COMBINATIONAL LOGIC

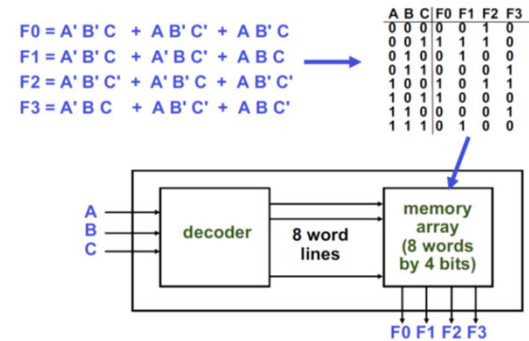


ROM AS A "RANDOM-LOGIC" CIRCUIT


- ROM advantages
 - Design time is short
 - Can implement any function of n inputs
- ROM disadvantages
 - Size doubles for each additional input
 - Cannot exploit logic minimization (e.g., don't cares)

READ ONLY MEMORIES (ROMS)

 
- A memory that can only be read and never altered
 - Programs for fixed applications that, once developed and debugged, never need to be changed (only read)
 - Fixing the contents at manufacturing time leads to small and fast implementations.



MOS OR ROM CELL ARRAY

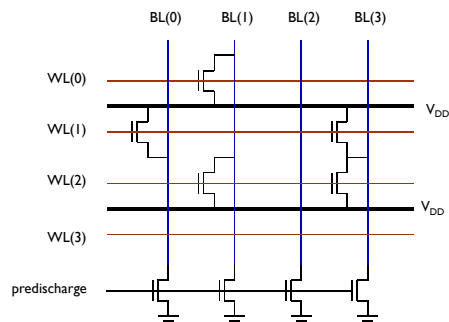


PRECHARGED MOS NOR ROM

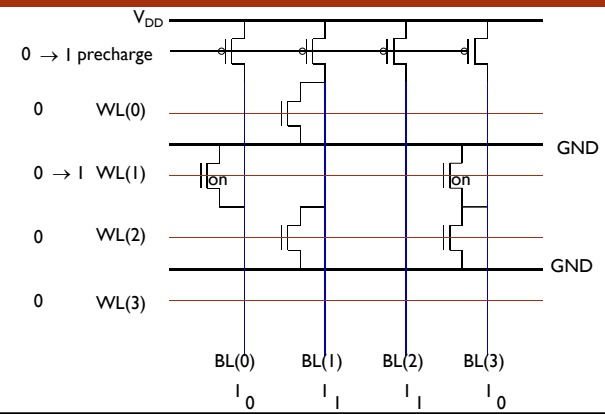

A TYPICAL MEMORY HIERARCHY

 - By taking advantage of the principle of locality, we can:
 - present the user with as much memory as is available in the cheapest technology
 - at the speed offered by the fastest technology.




| | | | | | |
|----------------------|---------|------|--------|-------|---------|
| Speed (ns): | .1's | 1's | 10's | 100's | 1,000's |
| Size (bytes): | 100's | KB's | 10KB's | MB's | TB's |
| Cost: | highest | | | | lowest |


READ/WRITE MEMORIES (RAMS)





- Static – SRAM**
 - data is stored as long as voltage supply is enabled
 - large cells (6 FETs/cell) → fewer bits/chip
 - fast → used where speed is important (e.g., caches)
- Dynamic – DRAM**
 - periodic refresh required (every 1 to 4 ms)
 - small cells (1 to 3 FETs/cell) → more bits/chip
 - slower → used for main memories

1-DIMENSIONAL MEMORY ARCHITECTURE

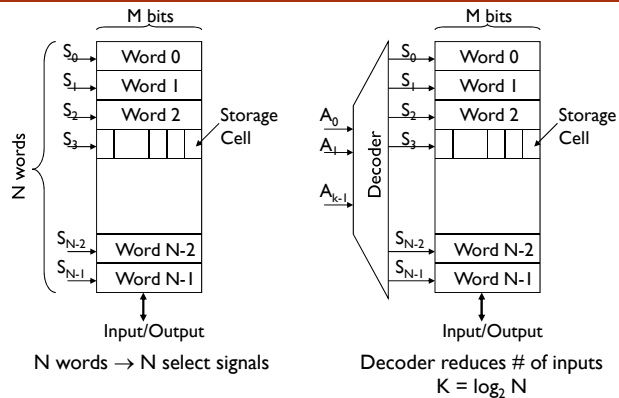

2D MEMORY ARCHITECTURE

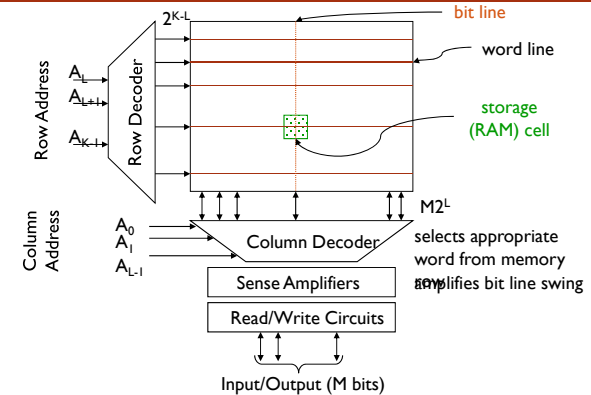

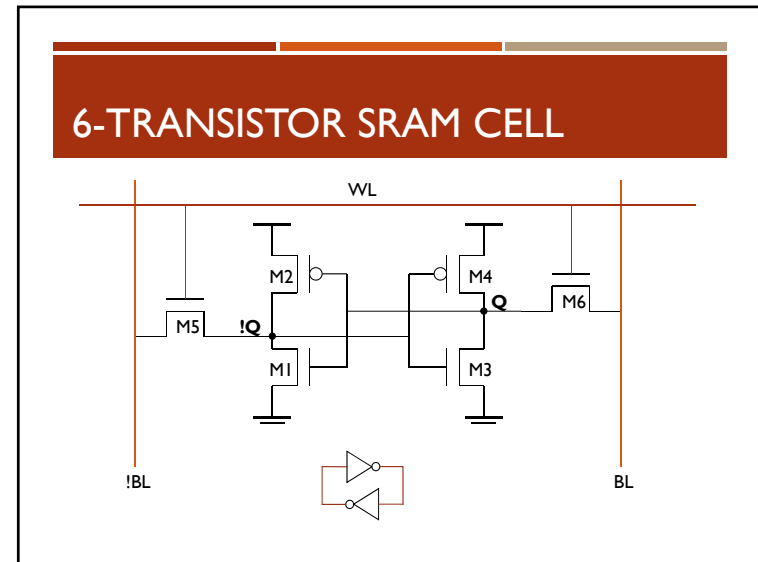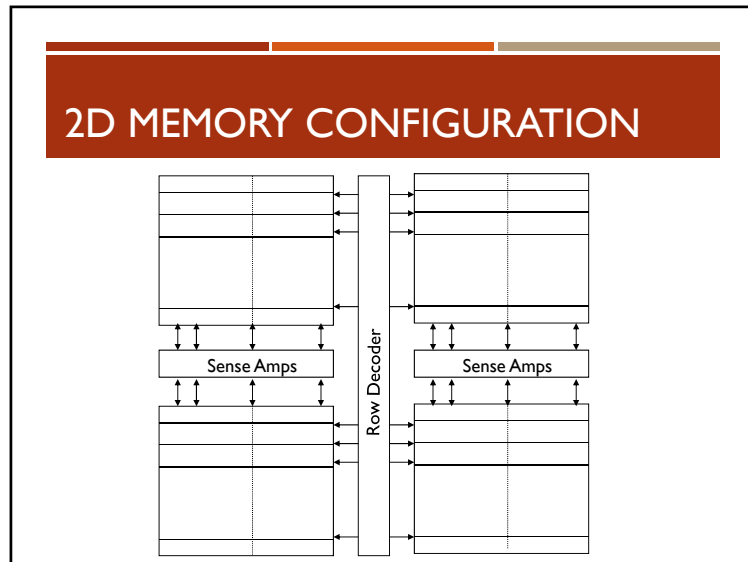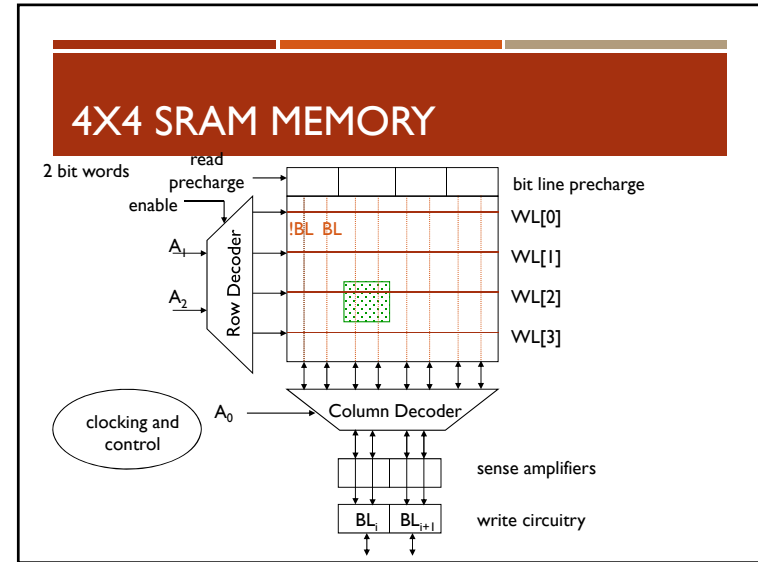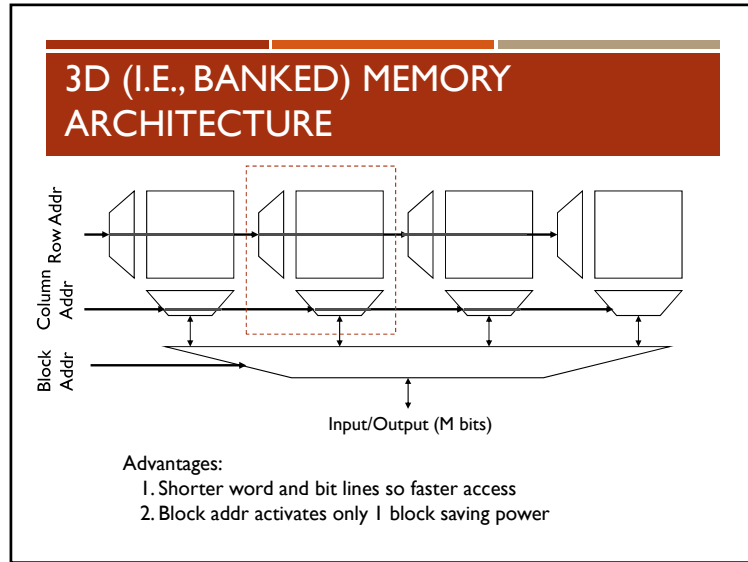

SRAM WRITE

- Drive on bit line high, the other low (depending on the desired write value)
- Then enable the word line (WL)
- Bit lines overpower cell with new value

