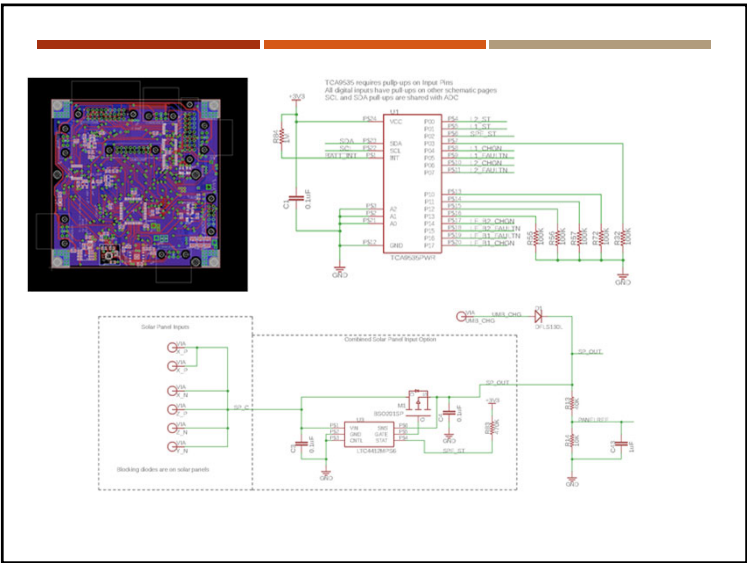

BROWN
School of Engineering

DIGITAL ELECTRONICS SYSTEM DESIGN

FALL 2019
PROF. IRIS BAHAR
DECEMBER 4, 2019
LECTURE 24: DYNAMIC MEMORY DESIGN



Sundays 1PM
Barus and Holley 190*
bse@brown.edu

LAB PRINTOUT AND RETURN


- Lab 2 has been graded.
 - Jiwon should have sent you an email with comments. Please get back to her with corrections (if needed).
- Lab 9 has been graded (by Prof. Patterson)
 - Those who require to resubmit, please redo, print out, and give directly to Prof. Patterson for fast turn around.
- Schematic requirement (for lab 1, 5, 7, 8, or A)
 - Print out your schematic and BOM for grading
 - This is due by Friday (but please complete sooner, if possible)

COURSE EVALUATIONS


- Course evaluation forms are now available
- Please access using Banner self service
- Filling out this form provides me with important feedback about your experience with this course.
- Comments are confidential
- Available to me only after grades have been submitted.

- Thanks!

SRAM ARCHITECTURE

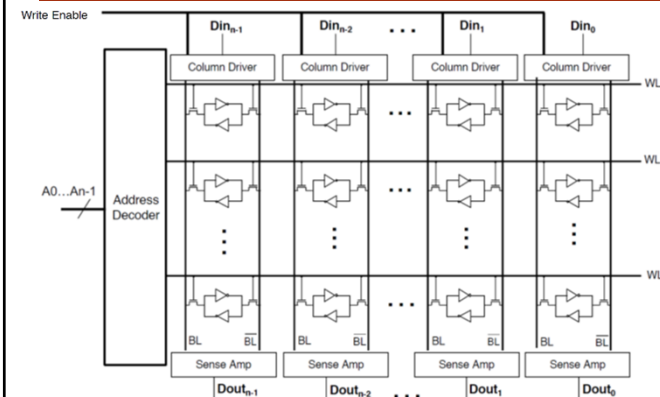

SENSE AMPLIFIERS

 

- Amplification: resolves data with small bit line swings
- Delay reduction: compensates for the limited drive capability of the memory cell

$$t_p = (C * \Delta V) / I_{av}$$


Annotations: C is labeled 'large', ΔV is labeled 'small' and 'make ΔV as small as possible', and I_{av} is labeled 'small'.

- Power reduction: eliminates a large part of the power dissipation

$$P = \frac{1}{2} C * V_{DD} * \Delta V * f$$


Annotation: ΔV is labeled 'make ΔV as small as possible'.

PULSED WORD LINE FEEDBACK

 


- Dummy column
 - height set to 10% of a regular column and its cells are tied to a fixed value
 - capacitance is only 10% of a regular column

PULSED WORD LINE TIMING




 


- Dummy bit lines have reached full swing and trigger pulse shut off when regular bit lines reach 10% swing

LATCH BASED SENSE AMPLIFIER

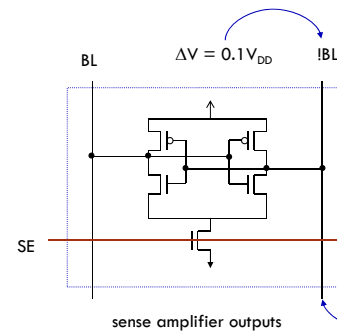


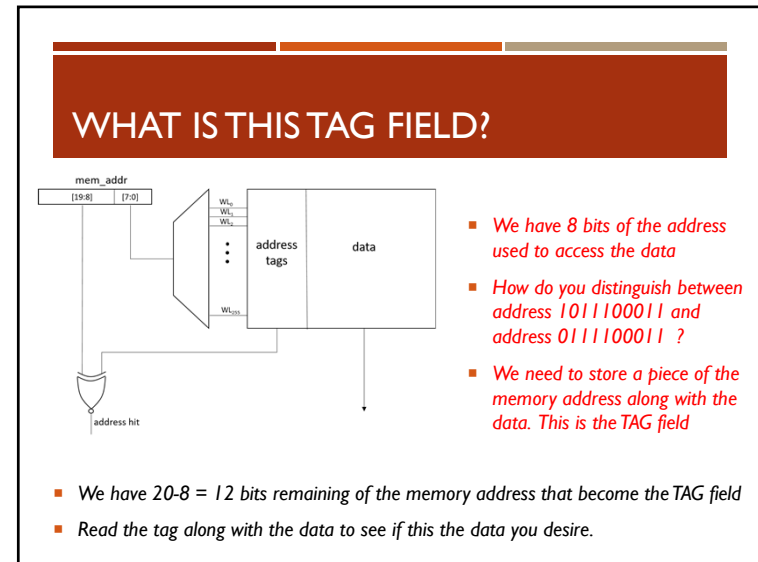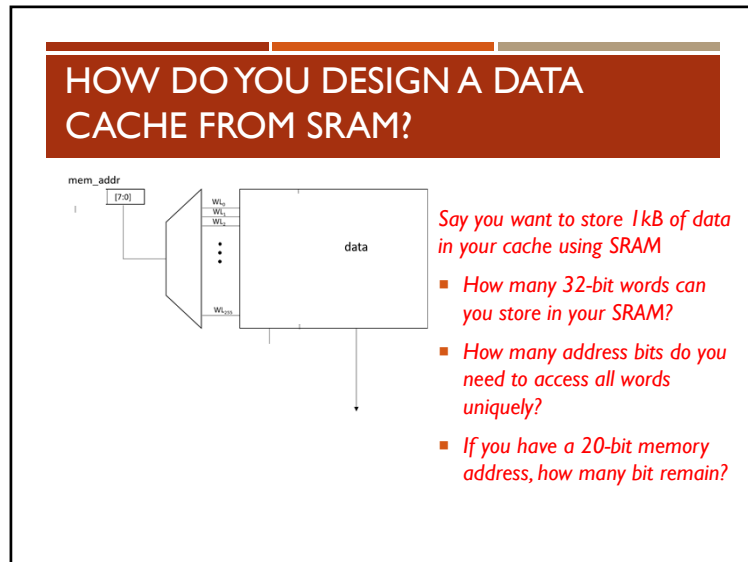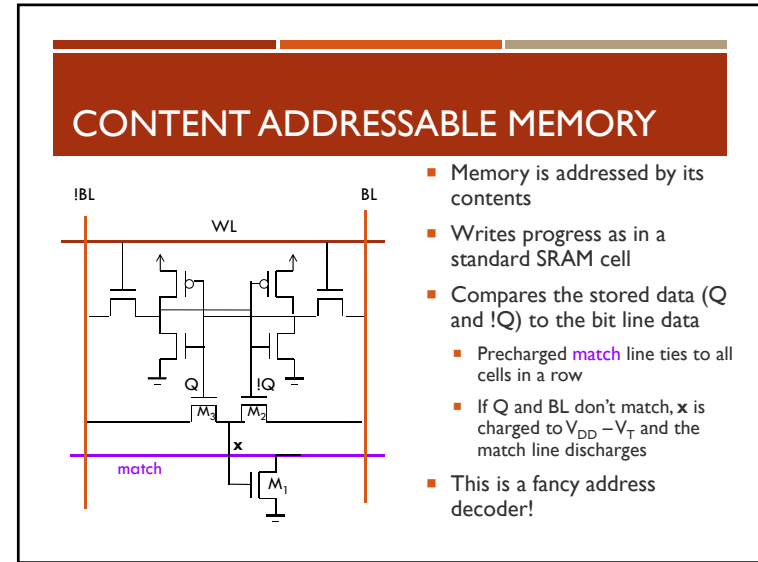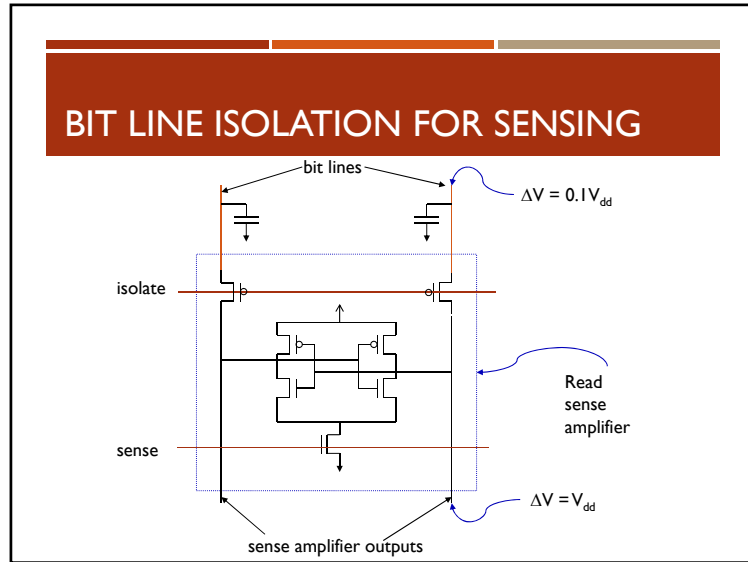- When SRAM cell is read, SE=0 (disabling amplifier)
- After short read period, SE=1, turning on cross-coupled inverters



FIELD PROGRAMMABLE GATE ARRAY (FPGA)

 - FPGAs are chips containing configurable logic blocks (CLBs) and programmable interconnect
- Each CLB contains a reprogrammable LookUp Table (LUT) and Flip-Flops for storage.
- The CPLDs you have been using in your labs are scaled back version of FPGAs (10^3 vs. 10^5 logic blocks and less memory)




MODERN FPGAS

- Modern FPGAs contain many additional specialized blocks:
 - Internal memory (Block RAM)
 - Memory controllers
 - Clock multipliers/dividers
 - Digital signal processing (DSP) units for fast arithmetic
 - Bus interfaces
 - Simple processors (e.g., ARM)


LOOKUP TABLES

 - A Lookup Table is a logic function generator made up of memory that essentially stores the truth table of a function.
- An n-input LUT can implement any function consisting of n inputs
 - 2^{2^n} different functions possible, so for n=4, 16,536 different functions



The connectivity of a single LUT6 block in a Xilinx Spartan-6 FPGA.

LOOKUP TABLE

 

- How do you program a 3-input LUT for this function?
- This is a 1-bit wide memory with 2^3 address lines

LUT MEMORY CELLS

- It is convenient to program the FPGA and then retain that programming even when disconnected from power (i.e., using non-volatile memory).
- One way to do this is with flash-memory based FPGAs

 


Fig. 2: A floating-gate transistor used in flash memory

FLOATING GATE TRANSISTOR

- Gate is electrically isolated, creating a floating node.
- A number of inputs are deposited above the floating gate and are electrically isolated from it.
- Since the floating gate is completely surrounded by a highly resistive material, the charge remains unchanged.