

1. (a)  $P < Q$  only

		$P_1 P_0$			
		00	01	11	10
$Q_1 Q_0$	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

Handwritten annotations: A red circle '1' is around the cell (01, 00). A red circle '2' is around the cell (10, 11). A green circle '3' is around the bottom-right corner of the 1s in the 11 and 10 rows.

$$\text{out} = \bar{P}_1 \bar{P}_0 Q_0 + \bar{P}_0 Q_1 Q_0 + \bar{P}_1 Q_1$$

①, ②, ③ are the prime implicants and the essential prime implicants.

(b)  $P < Q$  w/  $P = Q$  don't care

		$P_1 P_0$			
		00	01	11	10
$Q_1 Q_0$	00	X	0	0	0
	01	1	X	0	0
	11	1	1	X	1
	10	1	1	0	X

Handwritten annotations: A red circle '3' is around the cell (00, 00). A red circle '1' is around the cell (10, 11). A blue circle '2' is around the bottom-left corner of the 1s in the 01 and 10 rows. A green circle '4' is around the bottom-right corner of the 1s in the 11 and 10 rows. A red circle '5' is around the cell (10, 10).

①, ②, ③, ④, ⑤ are prime implicants.

possible solutions: (any of the three are correct)

Ⓐ if  $\text{out} = Q_1 Q_0 + \bar{P}_1 \bar{P}_0 + \bar{P}_1 Q_1$

①, ②, ④ are the essential prime implicants.

Ⓑ if  $\text{out} = Q_1 Q_0 + \bar{P}_1 Q_0 + \bar{P}_1 Q_1$


①, ③, ④ are the essential prime implicants.

Ⓒ if  $\text{out} = \bar{P}_1 Q_0 + \bar{P}_1 Q_1 + \bar{P}_0 Q_1$

③, ④, ⑤ are the essential prime implicants.

2. (a)  $F = WX + \bar{W}\bar{Y} + X\bar{Y}$

		XY			
		00	01	11	10
W	0	1			1
	1			1	1

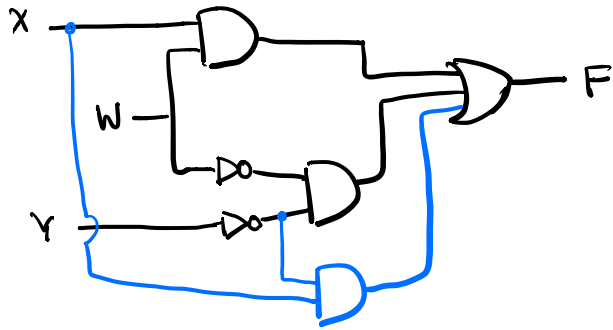

There is a potential timing hazard when  $X=1, Y=0$ , and  $W$  switches from  $1 \rightarrow 0$ .  
 need to add the blue term to remove hazards.

(b)  $F = W\bar{X}\bar{Y} + X\bar{Y}Z + XY + W\bar{Y}Z$

		XY			
		00	01	11	10
WZ	00	0	0	1	0
	01	0	0	1	1
	11	1	0	1	1
	10	1	0	1	0

There is a potential timing hazard when  $W=1, Y=0, Z=1$ , and  $X$  switches from  $1 \rightarrow 0$ .  
 Need to add the blue term to remove hazards.

(c)  $F = WY + \bar{W}\bar{Z} + X\bar{Y}Z + \bar{W}X\bar{Y} + WXZ + Y\bar{Z}$

		XY			
		00	01	11	10
WZ	00	1	1	1	1
	01	0	0	0	1
	11	0	1	1	1
	10	0	1	1	0

There are multiple timing hazards in this circuit:


- ① when  $X=1, Y=0, W=0$ , and  $Z$  switches from  $1 \rightarrow 0$ .
- ② when  $X=1, W=1, Z=1$ , and  $Y$  switches from  $1 \rightarrow 0$ .
- ③ when  $Y=1, Z=0$ , ( $X$  can be anything) and  $W$  switches from  $1 \rightarrow 0$

Need to add all blue terms to remove all three timing hazards.


3. (a) When  $T$  is low, the  $T$  flip-flop stores the value  $Q$ .  
 When  $T$  is high, the  $T$  flip-flop toggles the value of  $Q$  at every positive clock edge.

(b)  $Q_{next} = \overline{T}Q + T\overline{Q} = T \oplus Q$  ( $\oplus$ : XOR)


	T	
	0	1
Q	0	1
	1	0

 


T-flip flop:

 

4.

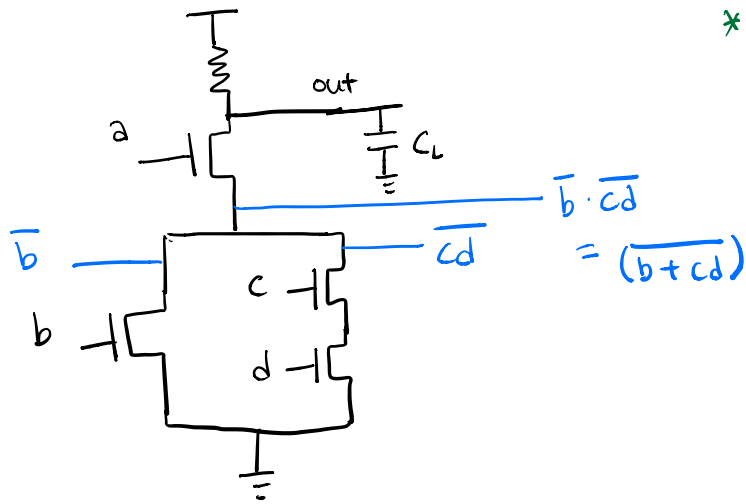

\*Note: NMOS transistor

 

when  $g=0$  ( $V_{gs} < V_{th}$ )  
no current flows,  
when  $g=1$  ( $V_{gs} \geq V_{th}$ )  
current flows.

- (a) current will flow when  $a=1$  AND ( $b=1$  OR  $cd=1$ )  
(out=0 when current flows, otherwise 1)

$$\text{out} = \overline{a(b+cd)}$$

- (b) \*Note: 1st order approximation  $t_{PHL} = 0.69 R_n \cdot C_L$  ← total resistance to drain  
\*Note: resistance of NMOS  $R_n \propto \frac{L}{\mu_n W}$   
 $t_{PHL}$  depends on total resistance to drain.  
resistance of gates depends on  $L/W$ .

longest path in given circuit — when  $a=c=d=1$

$$t_{PHL} = \alpha \frac{L_{min}}{W_{min}} = \alpha \left( \frac{L_a}{W_a} + \frac{L_c}{W_c} + \frac{L_d}{W_d} \right)$$

↑  
 $t_{PHL}$  for min. size inverter

Note: need to reduce resistance/gate but cannot reduce length beyond minimum size  
⇒ increase width

assuming gates  $a, c, d$  are same size.

$$L_a = L_c = L_d = 50 \text{ nm}, \quad W_a = W_c = W_d = 450 \text{ nm}$$


when  $a=b=1$ .

$$t_{PHL} = \alpha \frac{L_{min}}{W_{min}} = \alpha \left( \frac{L_a}{W_a} + \frac{L_b}{W_b} \right) = \alpha \left( \frac{L_{min}}{3W_{min}} + \frac{L_b}{W_b} \right)$$

$$L_b = 50 \text{ nm}, \quad W_b = 225 \text{ nm}$$

(c) fully - complementary CMOS gate

\*Note: PMOS transistor

 


when  $g$  is high ( $|V_{gs}| < |V_{th}|$ )

no current flows.

when  $g$  is low ( $|V_{gs}| \geq |V_{th}|$ )

Current flows.

 

$$t_{pHL} = 0.69 R_p \cdot C_L$$

$$R_p \propto \frac{L}{\mu_p W}$$

$$\frac{L}{\mu_p W} = \frac{2.5L}{\mu_n W}$$

worst - case path:  $c = b = 0$

$$t_{pHL} = \alpha \frac{L_{min}}{W_{min}}$$

$$t_{pHL} \text{ (for this circuit)} = \alpha \cdot 2.5 \cdot \left( \frac{L_b}{W_b} + \frac{L_c}{W_c} \right) = \alpha \frac{L_{min}}{W_{min}}$$

$$\frac{L_b}{W_b} + \frac{L_c}{W_c} = \frac{1}{2.5} \times \frac{L_{min}}{W_{min}}$$

assuming PMOS gates  $b, c$  are the same size,

$$\underline{L_b = L_c = 50 \text{ nm}, \quad W_b = W_c = 2 \cdot 2.5 \cdot W_{min} = 750 \text{ nm}}$$

PMOS gate  $d$  should be the same size as PMOS gate  $c$  (for  $b=d=0$ )

$$\underline{L_d = 50 \text{ nm}, \quad W_d = 750 \text{ nm}}$$

$$\text{if } a=0 \text{ — } t_{pHL} = \alpha \cdot 2.5 \cdot \frac{L_a}{W_a} = \alpha \cdot \frac{L_{min}}{W_{min}}$$

$$\frac{L_a}{W_a} = \frac{L_{min}}{2.5 W_{min}}$$

$$\underline{L_a = 50 \text{ nm}, \quad W_a = 375 \text{ nm}}$$

(d)  $(a, b, c, d) = (1, 0, 1, 1)$  causes worst-case fall delay.

$t_{pHL} \propto R_n$ . where  $R_n$  is the effective drain resistance.

$(a, b, c, d) = (1, 0, 1, 1)$  is when the drain path has highest resistance.

(e)  $R_{min} = 5 \text{ k}\Omega = K \frac{L_{min}}{W_{min}}$   
 (constant including  $\mu_n$ )

$C_L = 50 \text{ fF} (= 50 \times 10^{-15} \text{ F})$

worst-case  $t_{pHL} = 0.69 \cdot (R_a + R_c + R_d) \cdot C_L$

$R_a = R_c = R_d$   
 $= K \cdot \frac{L_{min}}{3W_{min}}$


$= 0.69 \cdot (3 \times \frac{5}{3} \times 10^3 \Omega) \cdot 50 \times 10^{-15} \text{ F}$

$= \frac{5}{3} \text{ k}\Omega$

$= 172.5 \times 10^{-12} \text{ seconds}$

$(1 \text{ f} \approx 1 \text{ second} / \Omega)$

(f) pull-down path — NMOS circuit

 

$W_a = W_c = W_d = 3 W_{min}$   
 $W_b = 1.5 W_{min}$


$C_{int1}$  — connected to source of c and drain of d.

$C_{int1} = 3 \cdot C_{dmin} + 3 C_{dmin} = 6 \cdot C_{dmin} = 3 \text{ fF}$

$C_{int2}$  — connected to source of a and drain of b, c

$C_{int2} = 3 C_{dmin} + 1.5 C_{dmin} + 3 C_{dmin} = 7.5 C_{dmin} = 3.75 \text{ fF}$

(g)

 

(using input vector  
from part (c),  
transistor b is off)

$$\begin{aligned} t_{PHL} &= 0.69 \cdot \left( 3 \text{ fF} \times \frac{5}{3} \text{ k}\Omega + 3.75 \text{ fF} \times \frac{10}{3} \text{ k}\Omega + 50 \text{ fF} \times \frac{15}{3} \text{ k}\Omega \right) \\ &= 0.69 \times (5 + 12.5 + 250) \times 10^{-15} \times 10^3 \text{ seconds} \\ &= \underline{184.575 \times 10^{-12} \text{ seconds}} \end{aligned}$$