

1. A 2-bit “comparator” circuit receives two 2-bit numbers, $P = P_1P_0$, and $Q = Q_1Q_0$. The comparator circuit produces a 1 if and only if $P < Q$.
 - a. Using a K-map, design a minimum sum-of-products circuit for this 2-bit comparator. Identify all the prime implicants and essential prime implicants.
 - b. How would you answer for part (a) of this question if the output can be either 0 or 1 when $P = Q$?


2. For each of the following logic expressions, use a K-map to find all potential timing hazards in the corresponding two-level AND-OR circuit, and design a hazard-free circuit that realizes the same logic function.
 - a. $F = WX + W'Y'$
 - b. $F = WX'Y' + XY'Z + XY$
 - c. $F = WY + W'Z' + XY'Z$

3. The table below summarizes the behavior of a *T flip-flop*.

T	Clk	Q	Q _{next}
0	X	X	Q
1	Positive edge	0	1
1	Positive edge	1	0

- a. Describe in words the behavior of this device.
- b. Find a Boolean expression for this device’s output.
- c. Using a D flip-flop and a minimum number of additional logic gates, design the T flip-flop.

 4. Consider the following NMOS gate with pull-up resistor:



(a) What Boolean function does this gate implement?

(b) Assume a minimum transistor has $W_{min}=150\text{nm}$ and $L_{min}=50\text{nm}$. Size the NMOS devices for the gate such that as a first order approximation, the t_{pHL} delay of the gate is the same as the t_{pHL} delay of a minimum sized inverter. Size the **longest path first** and write the transistor sizes (W and L) next to each transistor. Show your calculations below, if needed.

(c) Now consider designing the complex gate as a static, fully-complementary CMOS gate. Draw the transistor-level representation of the full gate and size the PMOS devices in terms of W_{min} such that rise time is approximately the same as fall time (for worst case paths). Assume that the mobility of the NMOS device is $2.5\times$ greater than the PMOS (i.e., $\mu_n = 2.5\mu_p$)

- (d) What input vector {a,b,c,d} produces a worst case fall delay t_{pHL} ? Explain your reasoning.
- (e) If the resistance of a minimum sized NMOS is $R_{min}=5K\Omega$, and the output load is $C_L=50fF$, what is the approximate *worst case fall delay*, t_{pHL} , for the gate to reach the 50% point (ignoring effects of intrinsic capacitance on internal nodes)? Show your calculations.
- (f) Now add source/drain intrinsic capacitance to all *internal* nodes in the pull-down path (ignore any additional capacitance at the output node). Assume that each source/drain connected to a node contributes a capacitance of $C_d=x \cdot C_{dmin}$ to the total node capacitance, where x is the width of the transistor relative to a *minimum sized transistor* and $C_{dmin} = 0.5fF$. Show your calculations for all the internal node capacitances and draw the capacitances with values on the diagram above.
- (g) Given the additional internal capacitances from part (e), draw the equivalent RC network and re-calculate the worst case fall delay t_{pHL} for the gate using the Elmore delay model, assuming the same input vector from part (c). Explain your reasoning. Recall that the Elmore delay equation is:

$$t_p = \sum_{i=0}^N c_i r_{ij} = \sum_{i=0}^N c_i \sum_{j=0}^i r_j$$