

EN1600

**Design and Implementation of
VLSI Systems
Fall 2016**

Lecture 10: Performance Optimization for Complex CMOS Gates

Reading: Chapter 4, sections 4.4-4.5 October 12, 2016
Weste & Harris Prof. R. Iris Bahar


 **BROWN**

© 2016 R.I. Bahar
Portions of these slides taken from Professors
J. Rabaei, J. Irwin, V. Narayanan, and S. Reda

BROWN


Transistor sizing for a complex gate

OUT = $!(D + A \cdot (B + C))$

 

Which one is better?


Does it even matter?

 

BROWN

Transistor sizing for a complex gate

OUT = $!(D + A \cdot (B + C))$

 


- Total $W_p=24$
- Worst case path resistance:
 - $R_{p_{eff}} = \beta(1/8 + 1/8 + 1/4)$
 $= 2 \times (1/2) = 1$
 (same as for an inverter)
- Shortest path resistance:
 - $R_{p_{eff}} = \beta(1/4 + 1/4)$
 $= 2 \times (1/2) = 1$
- Best case pull up resistance:
 - $R_{p_{eff}} = \beta [((1/8 + 1/8) || (1/4)) + 1/4]$
 $= \beta [1/8 + 1/4] = 3/8$
 (approx. more than twice as fast as worst case)

BROWN

Transistor sizing for a complex gate

OUT = $!(D + A \cdot (B + C))$

 


- Total $W_p=21$ (less area, intrinsic cap)
- Worst case path resistance:
 - $R_{p_{eff}} = \beta(1/6 + 1/6 + 1/6)$
 $= 2 \times (1/2) = 1$
 (same as for an inverter)
- Shortest path resistance:
 - $R_{p_{eff}} = \beta(1/3 + 1/6)$
 $= 2 \times (1/2) = 1$
- Best case pull up resistance:
 - $R_{p_{eff}} = \beta [((1/6 + 1/6) || (1/3)) + 1/6]$
 $= \beta [1/6 + 1/6] = 1/3$
 (even better than shortest path first sizing!)
 Creates larger disparity in delays as a function of inputs

Homework #3

- Available on line later today
- Due Friday, October 21 by 5pm
- After today's lecture, you should be able to complete all but the last problem (on dynamic logic)
- Monday's lecture will finish covering dynamic logic

Chain network Elmore delay

 


- A typical wire is a chain network with (simplified) Elmore delay of

$$\tau_{DN} = \sum c_i r_{ii} = \sum c_i \sum_{j=i}^N r_j$$

- Where $\sum_{j=i}^N r_j = r_i + r_{i+1} + \dots + r_N$

Chain Network Elmore Delay

 

Elmore delay equation $\tau_{DN} = \sum c_i r_{ii} = \sum c_i \sum_{j=i}^N r_j$

If all resistors are equal size,


$$\tau_{Di} = c_1 r_{eq} + 2c_2 r_{eq} + 3c_3 r_{eq} + \dots + ic_i r_{eq}$$

Uses for the Elmore Delay Model

- Modeling the delay of a wire
- Modeling the delay of a series of pass transistors

➡ Modeling the delay of a pull-up and pull-down networks

Fanin considerations

 


Distributed RC model (Elmore delay)


$$t_{pHL} = 0.69 R_{eqn}(C_1 + 2C_2 + 3C_3 + 4C_L)$$

(assuming all NMOS equally sized)

 Propagation delay deteriorates rapidly as a function of fanin: **quadratically** in the worst case.



RC tree definitions

 

- RC tree characteristics
 - Unique path from source to any node
 - Single input (source), no loops
 - All caps have connection to GND
- Path resistance:

$$r_{ii} = \sum r_i \Rightarrow (r_i \in [\text{path}(s \rightarrow i)])$$
- Shared path resistance:

$$r_{ik} = \sum_{j=1}^N r_j \Rightarrow (r_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$
- A typical wire is a tree network with Elmore delay of:


$$\tau_{Di} = \sum_{k=1}^N C_k r_{ik}$$

Multiply each capacitance C_k by the shared resistance from source to k and source to i

Fast complex gates: techniques #0, #1

- Transistor sizing (i.e., scaling up all transistor in gate)
 - as long as fan-out capacitance dominates
- Progressive sizing

Distributed RC line

 

$M1 > M2 > M3 > \dots > MN$

(the FET closest to the **output** should be the smallest)

Can reduce delay by more than 20%; decreasing gains as technology shrinks

Fast complex gates: technique #2

- Input re-ordering
 - when not all inputs arrive at the same time

critical path

delay determined by time to discharge C_L , C_1 and C_2

critical path

delay determined by time to discharge C_L

Sizing and ordering effects

Example:

Progressive sizing in pull-down chain gives up to a 23% improvement.

Input ordering saves 6%

critical path A – 23%

critical path D – 17%

Fast complex gates: technique #3

- Alternative logic structures

$F = ABCDEFGH$

Fast complex gates: technique #4

- Isolating fan-in from fan-out using buffer insertion

- Real lesson:** optimizing the propagation delay of a gate in isolation is misguided

Technique #5 : Logical Effort

- The optimum effective fan-out for a chain of N inverters driving a load C_L is $f = \sqrt[N]{C_L / C_{in}}$
 - Set N such that the fan-out per stage is around 4, whenever possible (FO4)
- Can we generalize this approach (logical effort) to any gate?
 - The inverter equation is $t_p = t_{p0} (1 + C_{ext} / \gamma C_g) = t_{p0} (1 + f / \gamma)$ we can generalize it to...

$$t_p = t_{p0} (p + g f / \gamma)$$

 - t_{p0} is the intrinsic delay of an inverter
 - f is the effective fan-out (C_{ext} / C_g) – also called the **electrical effort**
 - p is the ratio of the intrinsic delay of the gate relative to a simple inverter (a function of the gate topology and layout style): **parasitic delay**
 - g is the **logical effort**

Intrinsic delay term, p

- The more involved the structure of the complex gate, the higher the intrinsic delay compared to an inverter

Gate Type	P
Inverter	1
n-input NAND	n
n-input NOR	n
n-way mux	$2n$
XOR, XNOR	$n 2^{n-1}$

Ignoring second order effects such as internal node capacitances

Logical effort term, g

- g represents the fact that, for a given load, complex gates have to work harder than an inverter to produce a similar (speed) response
 - complex gates have higher input capacitance $\rightarrow$ worse output current

Gate Type	g (for 1 to 4 input gates)			
	1	2	3	4
Inverter	1			
NAND		4/3	5/3	$(n+2)/3$
NOR		5/3	7/3	$(2n+1)/3$
mux		2	2	2
XOR		4	12	

Delay as a function of fanout

- The slope of the line is the logical effort of the gate (g)
- The y-axis intercept is the intrinsic delay (t_{p0})
- What are 2 ways to reduce delay?
 - Adjust the effective fanout (by scaling up transistor sizes)
 - Choose a gate with a different logical effort

Gate effort: $h = fg$

Path delay of logic gate network

- Total path delay through a combinational logic block

$$t_p = \sum t_{p,i} = t_{p0} \sum (p_i + (f_i g_i)/\gamma)$$
- Using the same analysis as for the inverter we find that **each stage should bear the same gate effort**

$$f_1 g_1 = f_2 g_2 = \dots = f_N g_N \quad \text{or}$$

$$g_1 C_{\text{ext},1} / C_{g,1} = g_2 C_{\text{ext},2} / C_{g,2} = \dots = g_N C_L / C_{g,N}$$
- Optimize the path delay through the logic network

How do we optimally size gates a, b, and c?

Path delay (equation derivation)

- The path logical effort, $G = \prod g_i$
- Path effective fanout (path electrical effort) is $F = C_L / C_{g1}$ [1]
- The branching effort accounts for fan-out to other gates in the network: $b = (C_{\text{on-path}} + C_{\text{off-path}}) / C_{\text{on-path}}$
- The path branching effort is then $B = \prod b_i$
...and the **total path effort** is then $H = GFB$ [1]
- The gate effort that minimizes path delay is $h = \sqrt[4]{H}$
- So, the minimum delay through the path is

$$D = t_{p0} \left(\sum_{j=1}^N p_j + \frac{N(\sqrt[4]{H})}{\gamma} \right)$$

[1] Note the textbook swaps the definitions of F, H and f_i, h

Path delay of logic gate network (cont.)

- For gate i in the chain, its size is determined by $h = f_i g_i b_i$

- For this network what do we need to compute h ?
 - $F = C_L / C_{g1} = 5$
 - $G = 1 \times 5/3 \times 5/3 \times 1 = 25/9$
 - $B = 1$ (no branching)
 - $H = GFB = 125/9$, so the optimal stage effort is $h = \sqrt[4]{H} = 1.93$
 - Fanout factors are computed as $f_i = h / (g_i b_i)$. Since $b_i = 1$ we have:

$$f_1 = h / g_1 = 1.93, \quad f_2 = 1.93 / (5/3) = 1.16,$$

$$f_3 = 1.93 / (5/3) = 1.16, \quad f_4 = 1.93$$


Path delay of logic gate network (cont.)

- Given f_i for each gate i in the chain, what is the final sizing?

- $f_1 = 1.93, f_2 = 1.16, f_3 = 1.16, f_4 = 1.93$
- So the gate sizes are (working from outputs to inputs):
 - c: $f_4 = C_{\text{ext},4} / C_{g,4} = C_L / C_{g,4} = 1.93 \rightarrow C_{g,4} = 5 / 1.93 = 2.59$
 - b: $f_3 = C_{\text{ext},3} / C_{g,3} = C_{g,4} / C_{g,3} = 1.16 \rightarrow C_{g,3} = 2.59 / 1.16 = 2.23$
 - a: $f_2 = C_{\text{ext},2} / C_{g,2} = C_{g,3} / C_{g,2} = 1.16 \rightarrow C_{g,2} = 2.23 / 1.16 = 1.93$
 - g₁: $f_1 = C_{\text{ext},1} / C_{g,1} = C_{g,2} / C_{g,1} = 1.93 \rightarrow C_{g,1} = 1.93 / 1.93 = 1.00$

Path delay of logic gate network (cont.)

 - So what are the actually scaling sizes of the gates?



- Consider again the intrinsic capacitance values we calculated
 - $c_{g,4}=5/1.93=2.56$, $c_{g,3}=2.59/1.16=2.23$, $c_{g,2}=2.23/1.16=1.93$, $c_{g,1}=1.93/1.93=1.00$
 - These are relative to a *minimum sized inverter*, so we need to adjust to the gate type:
 - $c_{g,4} = 2.56 \rightarrow$ gate c is 2.56X size of minimum sized inverter, so $S_c = 2.56$ since gate c is an inverter as well.
 - $c_{g,3} = 2.23 \rightarrow$ gate b is 2.23X size of minimum sized nor. Minimum sized nor is 5/3 as big as min sized inv so $S_b = 2.23 \times 3/5 = 1.34$ (i.e., NOR is 1.34X size of minimum sized NOR)
 - $c_{g,2} = 1.93 \rightarrow$ gate a is 1.93X size of minimum sized NAND3. Minimum sized nand3 is 5/3 as big as min sized nand so $S_a = 1.93 \times 3/5 = 1.16$ (i.e. NAND is 1.16X size of minimum sized NAND3)