

EN1600
Design and Implementation of
VLSI Systems
Fall 2016


Lecture 22: Datapath Logic

Reading: Chapter 11, sections 11.8, 11.9 November 28, 2016
 Chapter 1, section 1.10 Prof. R. Iris Bahar

Weste & Harris


 **BROWN**

© 2016 R.I. Bahar
 Portions of these slides taken from Professors
 J. Rabaey, J. Irwin, V. Narayanan, and S. Reda


 **BROWN**

What's coming up?


- Remaining lectures:
 - Datapath Logic
 - Design for reliability, low power circuits, emerging topics...
 - Process technologies beyond bulk CMOS
- Final exam: **Wednesday, November 30 (in class)**
- Project status report: **Wednesday, December 7, 5pm**
- Final Presentations: **Tuesday, December 13, 9am-noon**
- Final Reports due by: **Thursday, December 15, 5pm**
 - Include slides, proposal, progress reports in appendix

 **BROWN**


A Programmable Binary Shifter

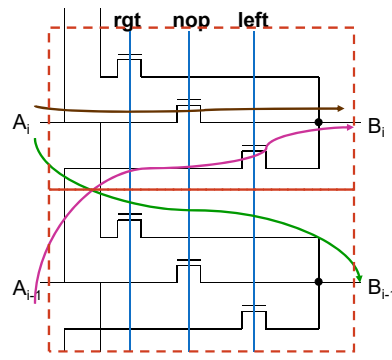

A_i	A_{i-1}	rgt	nop	left	B_i	B_{i-1}
A_1	A_0	0	1	0	A_1	A_0
A_1	A_0	1	0	0	0	A_1
A_1	A_0	0	0	1	A_0	0

 **BROWN**

4-bit Barrel Shifter

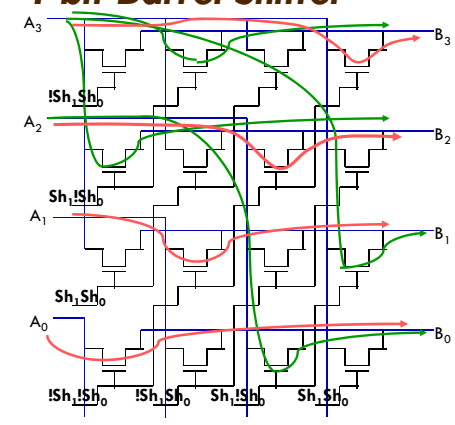

Example:





$!Sh_1!Sh_0 = 1$
 $B_3B_2B_1B_0 = A_3A_2A_1A_0$

$!Sh_1Sh_0 = 1$
 $B_3B_2B_1B_0 = A_3A_3A_2A_1$

$Sh_1!Sh_0 = 1$
 $B_3B_2B_1B_0 = A_3A_3A_3A_2$

$Sh_1Sh_0 = 1$
 $B_3B_2B_1B_0 = A_3A_3A_3A_3$

Area dominated by wiring

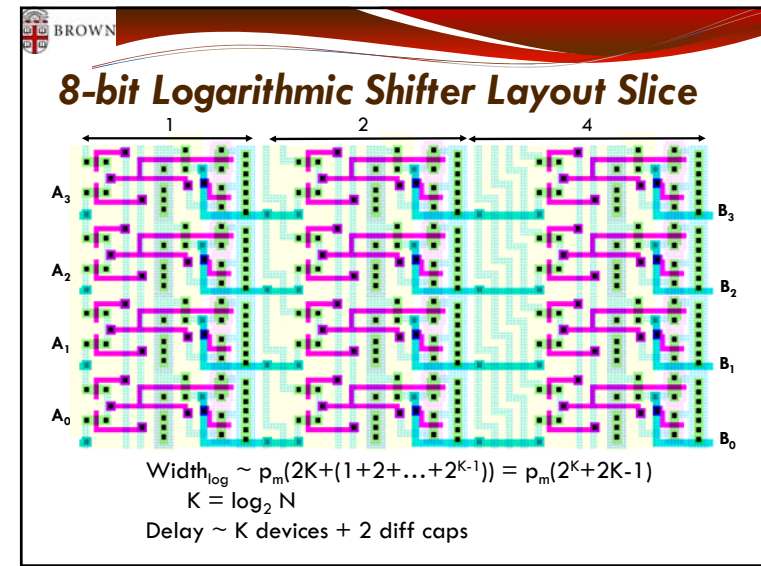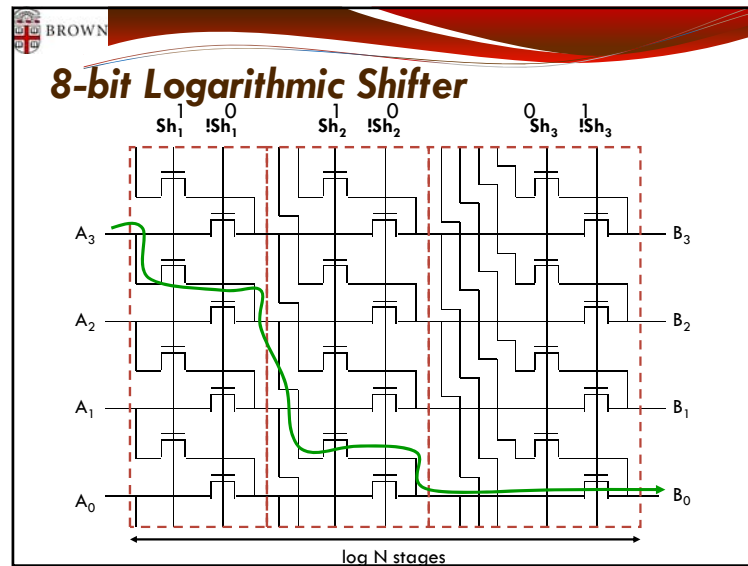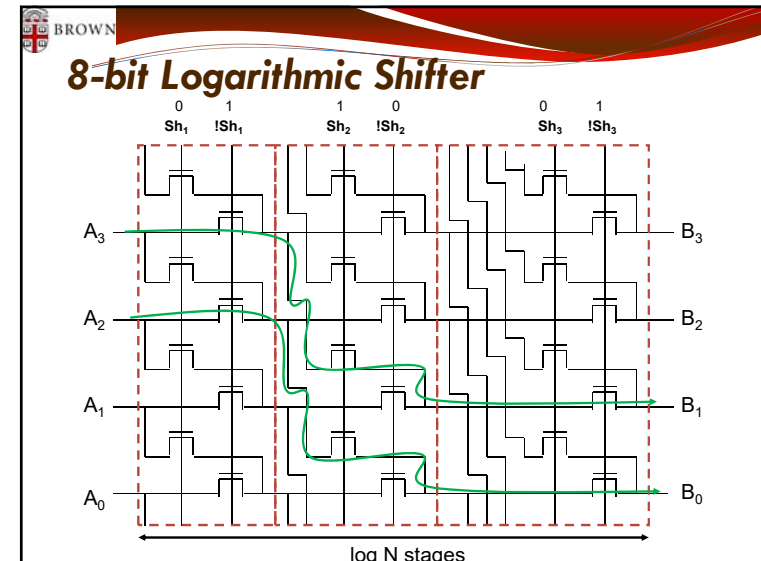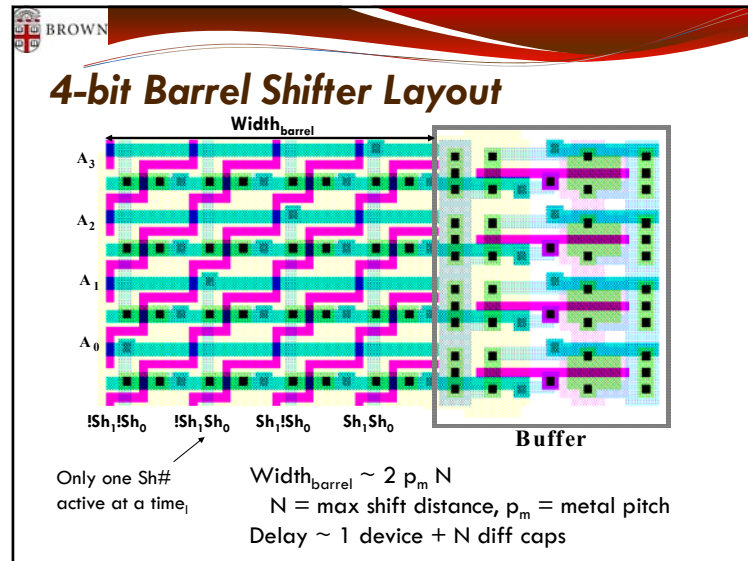

A. 1's and 0's detectors

- 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)

Is there a better/faster way?

Domino Zero Detector

B. Equality comparator

- Check if each bit is equal (XNOR, aka equality gate)
- 1's detect on bitwise equality

Where have you seen this function before?

9-T CAM cell

- Writes progress as in a standard SRAM cell
- Compares the stored data (Q and !Q) to the bit line data
 - Precharged match line ties to all cells in a row
 - If Q and BL match, x is discharged through M_2 or M_3 and thus M_1 is OFF keeping the match line high
 - Else if Q and BL don't match, x is charged to $V_{DD} - V_T$ and the match line discharges

